

**A**

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 54B01**

B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2019

Fourth Semester

Biomedical Engineering

15UBM401-ANALOG AND DIGITAL INTEGRATED CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Output impedance of an ideal op-amp is \_\_\_\_\_. CO1- R  
(a) Infinity                      (b) Zero                      (c) One                      (d) Undefined
- If the feedback/input resistor ratio of a feedback amplifier is 4.6 with 1.7 V applied to the non inverting input, what is the output voltage value? CO1- R  
(a) 7.82 V                      (b) 8.27 V                      (c) 9.25 V                      (d) 9.52
- Op-amp used as high and low pass filter circuits employ \_\_\_\_\_ configuration. CO2- R  
(a) Non-Inverting                      (b) Comparator                      (c) Open-loop                      (d) Inverting
- In successive approximation ADC technique n-bit conversion requires \_\_\_\_\_ clock period. CO2- R  
(a) n                      (b) n-1                      (c)  $2^n$                       (d)  $2^{n-1}$
- An astable multivibrator is also known as \_\_\_\_\_. CO3- R  
(a) One-Shot Multivibrator                      (b) Free-Running Multivibrator  
(c) Bistable Multivibrator                      (d) Monostable Multivibrator

6. The accurate and stable time delays are produced by\_\_\_\_\_. CO3- R  
 (a) Schmitt trigger (b) PLL (c) VCO (d) 555 Timer
7. The gate required to build a half adder are \_\_\_\_\_. CO4- R  
 (a) EX-OR gate and NOR gate (b) EX-OR gate and AND gate  
 (c) EX-OR gate and OR gate (d) Four NAND gates
8. Encoder is a combinational circuit that usually contains \_\_\_\_\_. CO4- R  
 (a)  $2^n$  inputs and n outputs (b) n inputs and  $2^n$  outputs  
 (c)  $2^n$  inputs and 1 output (d) 1 inputs and  $2^n$  output
9. The output Q of JK flip flop is 1. It changes to 0 when a clock pulse is applied. The input J & K are respectively. CO5- R  
 (a) 1 & X (b) X & 1 (c) 0 & X (d) X & 0
10. State diagram of D flip flop consists of \_\_\_\_\_ number of states. CO5- R  
 (a) 2 (b) 4 (c) 8 (d) 10

PART – B (5 x 2= 10 Marks)

11. Define CMRR of an op-amp. CO1 R
12. Differentiate Schmitt trigger and comparator. CO2 R
13. List the application of analog multiplier. CO3 R
14. Prove that  $ABC + ABC' + AB'C + A'BC = AB + AC + BC$  CO4 R
15. Compare volatile and non-volatile memory. CO5 R

PART – C (5 x 16= 80 Marks)

16. (a) With neat sketch explain the operation of an instrumentation CO1- App (16)  
 amplifier.

Or

- (b) (i) Elucidate in detail about the AC characteristics of op-amp. CO1- App (8)  
 (ii) In operational amplifier If  $R_1 = 10K\Omega$  and  $R_f = 100\Omega$  , CO1- App (8)  
 $V_i=1V$ . A load of  $25K\Omega$  is connected to the output terminal.  
 Calculate  
 (a)  $i_1$  (b)  $V_0$  (c)  $i_L$  (d) total current  $i_0$  into the output pin.

17. (a) Design a second order active Low pass filter for a cutoff frequency of 5KHZ. CO2- Ana (16)
- Or
- (b) Describe in detail about the following Digital to Analog converters. (i) R-2R ladder (ii) Weighted Resistor types. CO2- Ana (16)
18. (a) Explain the block diagram of PLL and derive the expression for Lock range and capture range. CO3- Ana (16)
- Or
- (b) With a neat functional diagram, explain the operation of VCO. Also derive an expression for  $f_0$ . CO3- Ana (16)
19. (a) (i) Simplify the following function  
 $F(A,B,C,D) = \sum m(0,1,2,4,6,9,12,14)$  using K-Map method and implement the minimal expression using only NAND gates. CO4- Ana (12)
- (ii) Design a full Subtractor using only NAND gates. CO4- Ana (4)
- Or
- (b) (i) Reduce the following equation using Quine McCluskey method.  
 $F(A,B,C,D) = \sum m(0,1,3,4,5,7,10,13,14,15)$  CO4- Ana (12)
- (ii) Convert the Boolean expressions to canonical form  
 $A'C + A'B + AB'C + BC$  CO4- Ana (4)
20. (a) Explain the various methods by which a shift register shifts data out of a register. CO5- U (16)
- Or
- (b) Design a 3-bit binary synchronous counter using JK Flip-flops. CO5- U (16)

