

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52B08

B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2019

Second Semester

Biomedical Engineering

15UBM208 - ELECTRICAL CIRCUITS ANALYSIS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. Six light bulbs are connected in parallel across 110 V. Each bulb is related at 75 W. How much current flows through each bulb? CO1- R
(a) 0.682A (b) 0.7 A (c) 75 A (d) 110 A
2. Mesh analysis is based on CO1- R
(a) Kirchhoff's current law (b) Kirchhoff's voltage law (c) Source (d) Load
3. Superposition theorem is valid only for CO2- R
(a) Linear circuits (b) Non-linear circuits
(c) Both linear and non-linear (d) Neither of the two
4. Maximum power is transferred when load impedance is CO2- R
(a) Equal to source impedance (b) Equal to half of the source impedance
(c) Equal to zero (d) None of the above
5. What is the total reactance of a series RLC circuit at resonance? CO3- R
(a) Equal to X_L (b) Equal to X_C (c) Equal to R (d) Zero
6. Mutual inductance is a property associated with CO3- R
(a) Only one coil (b) Two or more coils
(c) Two or more coils with magnetic coupling (d) None of the above

7. The transient response occurs CO4- R
 (a) Only in resistive circuits (b) Only in inductive circuits
 (c) Only in capacitive circuits (d) Both in (b) and (c)
8. The time constant of a series RL circuit is CO4- R
 (a) LR (b) L/R (c) R/L (d) 0
9. The resultant voltage in a closed balanced delta circuit is given by CO5- R
 (a) Three times the phase voltage (b) $\sqrt{3}$ times the phase voltage
 (c) Zero (d) one
10. In a three-phase system, the volt-ampere rating is given by CO5- R
 (a) $3 V_L I_L$ (b) $\sqrt{3} V_L I_L$ (c) $V_L I_L$ (d) P_L

PART – B (5 x 2= 10 Marks)

11. State the Ohm's law and give their limitations. CO1- R
12. In a circuit contains $V=50$ volts, $R_{th} =25 \Omega$. Determine the value of load resistance when the load resistance draws maximum powers also find the value of P_{Max} CO2- R
13. Define the dot rule for coupled circuits. CO3- R
14. What is meant by forces and free response? CO4- R
15. Distinguish between the balanced and unbalanced star connection load. CO5- R

PART – C (5 x 16= 80 Marks)

16. (a) Determine the current delivered by the source in the circuit shown in Figure 1. CO1 App (16)

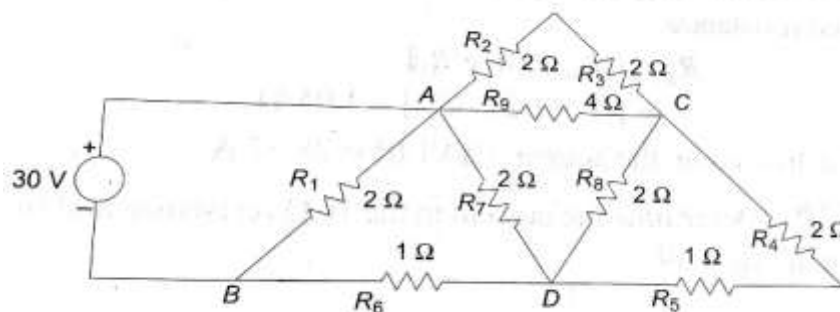


Figure 1

Or

- (b) Determine the mesh current $I_1, I_2,$ and I_3 in the circuit shown in Figure 2. CO1 App (16)

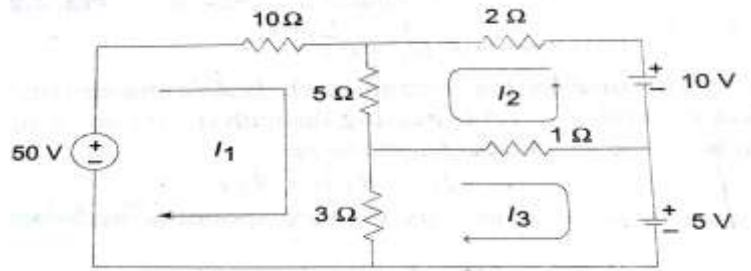


Figure 2

17. (a) Verify the reciprocity theorem for the network shown in Figure 3 CO2- App (16)

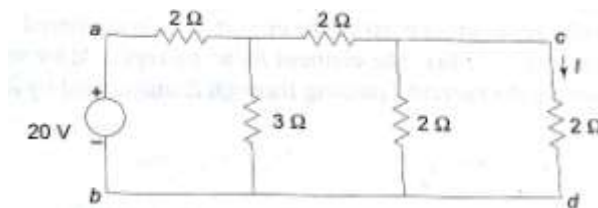


Figure 3

Or

- (b) Determine the current flowing through the 5Ω resistor in the circuit shown in Figure 4 by using Norton's theorem. CO2- App (16)

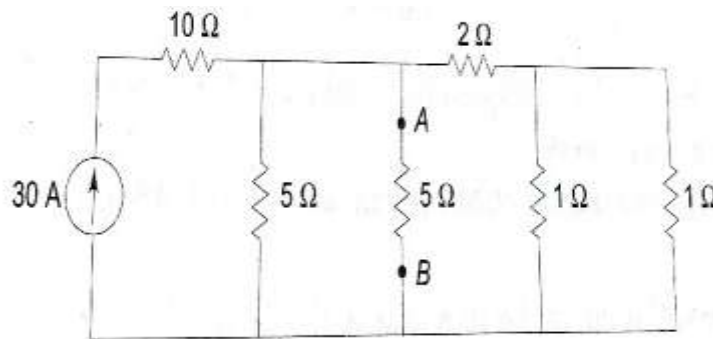


Figure 4

18. (a) (i) Two coupled coils of inductance $L_1 = 0.5$ H and $L_2 = 8$ H and $K = 0.5$ are connected in, CO3- Ana (8)
- Series aiding mode
 - Series opposing mode
 - Parallel aiding mode
 - Parallel opposing mode
- Calculate equivalent inductance of each case
- (ii) Derive the resonant frequency of a series RLC circuit. CO3- Ana (8)

Or

- (b) Determine the half power frequencies Bandwidth, the quality factor of a coil for the series circuit consisting of $R=10\ \Omega$, $L=0.1\ \text{H}$ and $C=10\ \mu\text{F}$. CO3- Ana (16)
19. (a) Derive and determine the DC response of an RL Series circuit and also find the voltage across the resistance and Inductance of the DC response. CO4- U (16)

Or

- (b) In an RLC series circuit contains $R=20\ \Omega$, $L=0.05\ \text{H}$, and $C=20\ \mu\text{F}$ with the $100\ \text{V}$ source when the switch is closed at $t=0$. Find the transient current. CO4- U (16)
20. (a) A three-phase balanced delta-connected load of $(4+j8)\ \Omega$ is connected across a $400\ \text{V}$, 3phase balanced supply. Determine the phase currents and line currents. Assume the phase sequence to be RYB. Also, calculate the power drawn by the load. CO5- U (16)

Or

- (b) A $400\ \text{V}$, three -phase supply feeds an unbalanced three-wire, star connected load. The Branch Impedances of The Load are $Z_R = (4+j8)\ \Omega$, $Z_y = (3+j4)\ \Omega$ and $Z_B = (15+j20)\ \Omega$. Find the line currents and voltage across each phase impedance. Assume the RYB phase sequence. CO5- U (16)