

B

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53B05

B.E./B.Tech. DEGREE EXAMINATION, APRIL 2019

Third Semester

Biomedical Engineering

15UBM305- SEMICONDUCTOR DEVICES AND CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. The diffused impurities with _____ valence electrons are called donor atoms. CO1-R
(a) 4 (b) 3 (c) 5 (d) 0
2. If $I_B = 1$ mA, $\beta = 50$ for a transistor, I_E is _____. CO1-App
(a) 51 mA (b) 50 mA (c) 101 mA (d) 49 mA
3. Which of the following equipment can check the condition of a transistor? CO2-U
(a) Current tracer (b) Digital display meter (DDM)
(c) Ohmmeter (VOM) (d) All of the above
4. g_m of MOSFET is controlled by _____. CO2- R
(a) Drain-source voltage (b) Gate-source voltage (c) Drain current (d) Gate current
5. The approximate current gain of CE transistor amplifier is _____. CO3- R
(a) h_{ie} (b) $-h_{ie}$ (c) $-h_{fe}$ (d) h_{fe}
6. The main feature of a large-signal amplifier is the circuit's _____. CO3- U
(a) power efficiency (b) maximum power limitations
(c) impedance matching to the output device (d) All of the above
7. Oscillator is similar to _____. CO4- R
(a) Rectifier (b) Amplifier (c) D.C source (d) A.C source

8. Which of the following improvements is (are) a result of the negative feedback in a circuit? CO4- R
- (a) Lower output impedance (b) Reduced noise
(c) More linear operation (d) All of the above
9. Bistable multivibrator is _____ in any state. CO5- R
- (a) Stable (b) Unstable (c) Saturated (d) Independent
10. Which of the following equipment can check the condition of a transistor? CO5- U
- (a) Current tracer (b) Digital display meter (DDM)
(c) Ohmmeter (VOM) (d) All of the above

PART – B (5 x 3= 15Marks) (5 Out of 7)

11. Define drift current? CO1- R
12. BJT as a current controlled device – Justify CO1- E
13. Why do we choose Q point at the center of the load line? CO2- E
14. Compare the operations of Class A and Class B amplifiers. CO3- Ana
15. Point out the advantages of negative feedback. CO4- Ana
16. State and explain Barkhausen criterion for oscillation. CO4- U
17. What is meant by hysteresis voltage in a Schmitt trigger? CO5- Ana

PART – C (5 x 15= 75 Marks)

18. (a) Illustrate the operation of a zener diode and discuss its V-I characteristics. Also discuss zener diode as a voltage regulator CO1- U (15)
- Or
- (b) Compare the operation of voltage divider bias circuits, base bias circuits and Emitter bias circuits. CO1- Ana (15)
19. (a) With neat diagram explain the operation of MOSFET in Enhancement mode and derive its current equations CO2-U (15)
- Or
- (b) Explain the working and characteristics of SCR and its applications CO2-U (15)

20. (a) Determine the h-parameters from transistor characteristics. CO3- App (15)
Or
(b) Find the input impedance, output impedance, voltage and current gain for CE amplifier CO3- Ana (15)
21. (a) Explain the concept of negative feedback in amplifier. Derive the expressions for voltage gain, input impedance and output impedance CO4-U (15)
Or
(b) Draw the circuit of Hartley oscillator and explain its working. Also derive the expressions for frequency of oscillation for starting of oscillation. CO4-U (15)
22. (a) Write the operation of collector coupled monostable multivibrator with neat circuit diagram and draw the various waveforms. CO5-U (15)
Or
(b) Illustrate the construction, equivalent circuit and operation of UJT and also explain the characteristics of UJT. CO5-U (15)

