

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code : 53404

B.E./B.Tech. DEGREE EXAMINATION, APRIL 2019

Third Semester

Electronics and Communication Engineering

15UEC304-ELECTRONIC CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

- When a BJT is used as an amplifier, it operates in CO1- R
(a) Active region (b) Cutoff region (c) Saturation region (d) All the above
- The darlington pair consists of the following two stages CO2- App
(a) CE and CC (b) Both CE (c) both CC (d) CE and CB
- The cutoff frequency that occurs when the common emitter current gain value drops to 0.707 of its low frequency value is called as CO3- U
(a) Alpha frequency (b) Beta frequency (c) Gamma frequency (d) Bandwidth
- Class AB operation is often used in power amplifiers in order to CO4-R
(a) Get maximum efficiency (b) remove even harmonics
(c) Overcome cross-over distortion (d) reduce collector dissipation
- In a Common emitter amplifier, the un-bypassed emitter resistor provides CO5- R
(a) voltage-shunt feedback (b) current-series feedback
(c) negative-voltage feedback (d) positive-current feedback

PART – B (5 x 3= 15Marks)

- Define: Stability factor. CO1-R
- State Miller's theorem. CO2-U
- Sketch the frequency response of an amplifier with a bypassed emitter resistor. CO3-App
- What is mean by second order harmonic distortion? CO4-U

10. An amplifier has a mid-band gain of 125 and a bandwidth of 250kHz. Calculate the new bandwidth and gain, if 4% of negative feedback is introduced. CO5- R

PART – C (5 x 16= 80Marks)

11. (a) Design the CE amplifier circuit with fixed bias configuration and explain it in detail. CO1-App (16)
- Or
- (b) Discuss the various techniques of stabilization of Q-point in a transistor. CO1- U (16)
12. (a) Draw the small signal equivalent model of a CE amplifier circuit and analyze the circuit to obtain the various parameters. CO2- U (16)
- Or
- (b) Draw the circuit of an emitter coupled differential amplifier and explain its operation. Analyze the circuit and obtain its transfer characteristics. CO2- U (16)
13. (a) Analyze the high frequency equivalent circuit of a FET amplifier. CO3-U (16)
- Or
- (b) Find the Midband gain A_m and upper 3dB frequency f_h of CS amplifier fed with a signal source having an internal resistance $R_{sig}=100\text{ K}\Omega$. The amplifier has $R_G = 4.7\text{M}\Omega$, $R_D = R_L = 15\text{K}\Omega$, $g_m = 1\text{mA/V}$, $r_0 = 150\text{K}\Omega$, $C_{gs} = 1\text{pF}$ and $C_{gd} = 0.4\text{ pF}$. CO3-App (16)
14. (a) Derive an expression for the theoretical maximum conversion efficiency of class B power amplifier. Also distinguish between class A, class B and class C amplifiers. CO4 U (16)
- Or
- (b) Draw the circuit diagram and explain the operation of class B push pull amplifier. Also discuss its merits. CO4 U (16)
15. (a) State and explain Nyquist criterion for stability in feedback amplifier. Also Obtain the frequency response of a current series feedback amplifier and explain the same. CO5- U (16)
- Or
- (b) Discuss and analyze the working of a single-tuned amplifier and draw a gain versus frequency plot. CO5- U (16)