

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 32307

B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2019

Second Semester

Electrical and Electronics Engineering

01UEE207- ELECTRIC CIRCUITS

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks


Answer ALL Questions.

PART A - (10 x 2 = 20 Marks)

1. Define Kirchhoff's law.
2. What is an ideal source?
3. State maximum power transfer theorem.
4. Write some applications of maximum power transfer theorem.
5. Define Q-factor of a coil.
6. Sketch the frequency response of a single tuned circuit.
7. Write the purpose of Laplace transformation in the circuit analysis.
8. A RL series circuit with $R=10\ \Omega$ is excited by a dc voltage source of 30 V by closing the switch at $t = 0$. Determine the current in the circuit at $t = 2\tau$.
9. A star connected load has impedance of $(6 + j8)\ \Omega$ in each phase. Determine the line current when it is connected to 400V, 3 phase, 50 Hz supply.
10. In three phase power measurement using two wattmeters, what is the power factor if one wattmeter reads zero?


PART - B (5 x 16 = 80 Marks)

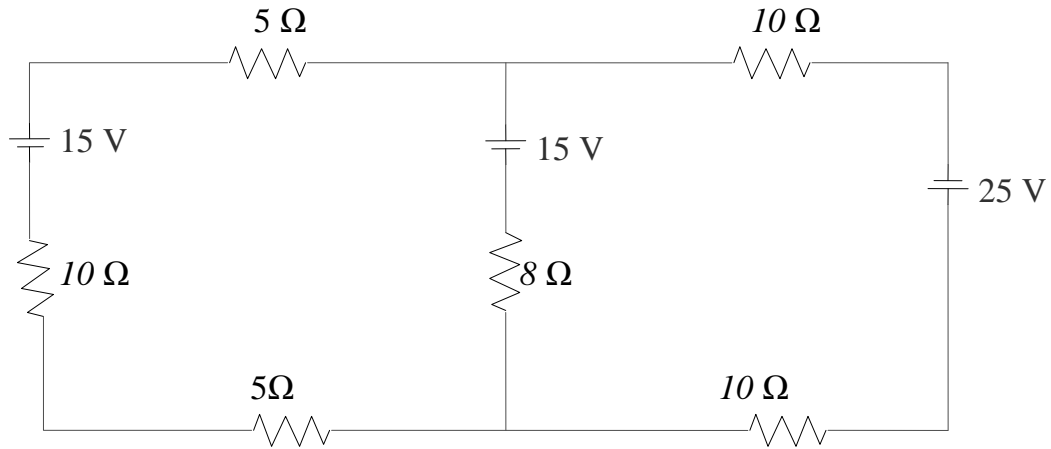11. (a) Use mesh analysis to determine the current in 8Ω resistor as shown in the circuit diagram. (16)



Or

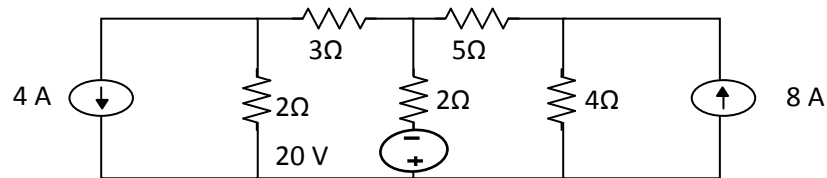- (b) Using nodal analysis, calculate the current through the 5Ω resistor in the circuit shown in figure 2. (16)



12. (a) Find i_o in the network shown in figure 3 using Superposition theorem. (16)


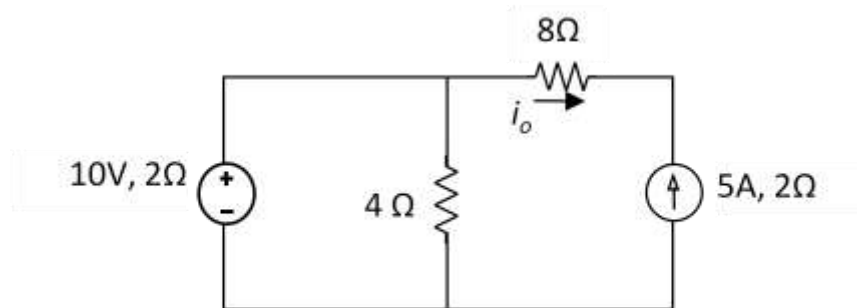


Figure 3

Or

- (b) (i) Explain how three resistances connected in delta can be converted into equivalent star. Derive the relationship. (8)
- (ii) An AC power source $100V, 50Hz$ has an internal impedance of $2 + j5 \Omega$. What will be the maximum power that can be delivered by this source to load? (8)

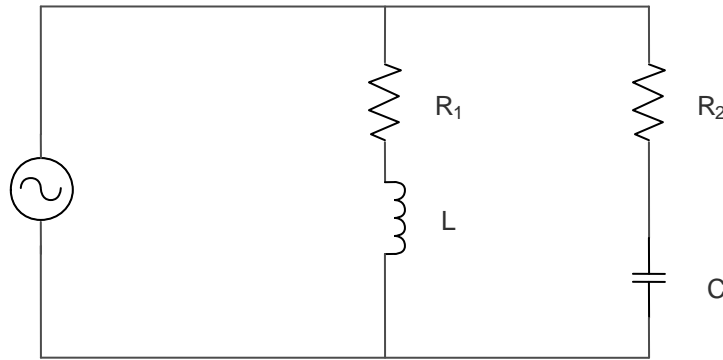13. (a) For the parallel circuit shown in figure, find the Resonance frequency f . (16)



Or

- (b) Two coils connected in series have an equivalent inductance of $0.8 H$ when connected in aiding and an equivalent inductance of $0.4 H$ when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking $k = 0.55$. (16)

14. (a) The switch in the circuit shown in figure is closed on position 1 at $t = 0$ and moved to position 2 after one time constant (τ). Obtain the current for $0 < t < \tau$ and $t > \tau$.

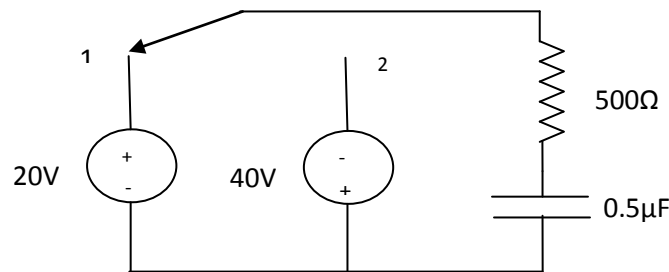


Figure.

(16)

Or

- (b) A capacitor has an initial charge of Q_0 . A resistor R is connected across the capacitor at $t = 0$, to discharge the charge. The power transient of the capacitor $p_c(t) = 800e^{-4000t}$ W. Find the value of R and Q_0 . Take $C = 10 \mu\text{F}$. (16)

15. (a) A three phase balanced supply of 400V (line to line) 50Hz is given to a three phase delta connected load with impedance $20 \angle 45^\circ \Omega$. Obtain the line currents, power and power factor. Also draw the phasor diagram. (16)

Or

- (b) Power is measured in a 3 phase, 400V (Line-Line) system by two wattmeters. If the readings are $W_1 = 3500\text{W}$ and $W_2 = 1500\text{W}$, determine the line currents, power and power factor if reading of W_2 is obtained after reversing its potential coil. (16)
