

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52309

B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2019

Second Semester

Electrical and Electronics Engineering

15UEE209 - ELECTRIC CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Which of the following is not a Active element? CO1- App
(a) Voltage source (b) Current source (c) Generator (d) Vacuum cleaner
- Which of the following condition is satisfy by the Ohm's Law? CO1- R
(a) Constant voltage (b) Constant temperature
(c) Constant current (d) None of the above
- Superposition theorem is only applicable for? CO2- R
(a) Nonlinear system (b) Linear system (c) Both (a) & (b) (d) None of the above
- Maximum power transfer theorem is applicable for? CO2-U
(a) Iron box (b) Grinder (c) Sound system (d) Air conditioner
- Antiresonance is also called as ? CO3- R
(a) Parallel resonance (b) Series resonance
(c) Both (a) & (b) (d) None of the above
- Mutual inductance is ? CO3- R
(a) $K = M \sqrt{(L_1 L_2)}$ (b) $M = K \sqrt{(L_1 L_2)}$ (c) $M = C \sqrt{(L_1 L_2)}$ (d) $M = K \sqrt{(L_1 L_2)}$
- Rising time for overdamped system is ? CO4- R
(a) 0 % to 100 % (b) 0 % to 90 % (c) 0 % to 63.2 % (d) 0 % to 36.8 %


8. Time constant of RC circuit? CO4- R
 (a) 0 % to 63.2 % (b) 0 % to 36.8 % (c) 2T (d) 4T
9. Power factor is not defined as CO5- R
 (a) Angle between voltage and current
 (b) Ratio between Resistance / Impedance
 (c) Real power / Apparent power
 (d) Coil displacement
10. Time period is? CO5- R
 (a) $2\pi / \omega$ (b) $F = 1 / T$
 (c) Time taken for half cycle (d) Time taken for half cycle

PART – B (5 x 2= 10 Marks)

11. What is current? CO1- R
12. State current division rule. CO2- R
13. Define coefficient of coupling. CO3- R
14. What is transient state? CO4-App
15. Define complex power. CO5-Ana


PART – C (5 x 16= 80 Marks)

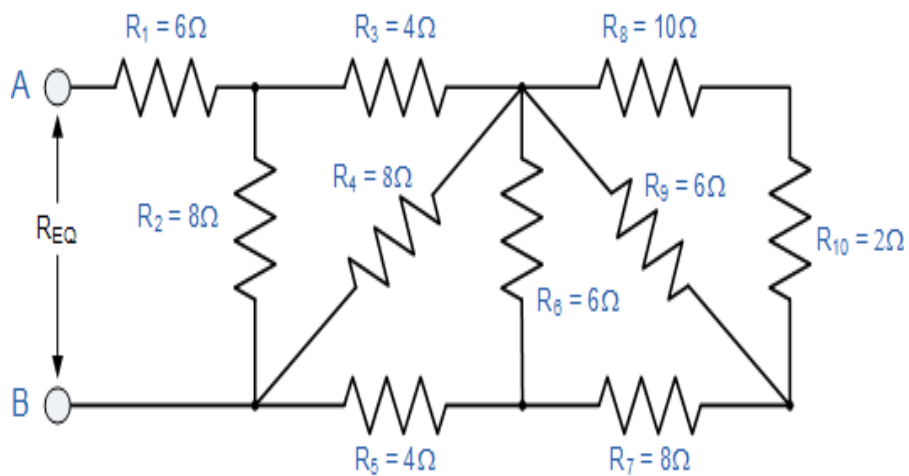16. (a) Determine the total resistance R of the given circuit? CO1- App (16)




Or

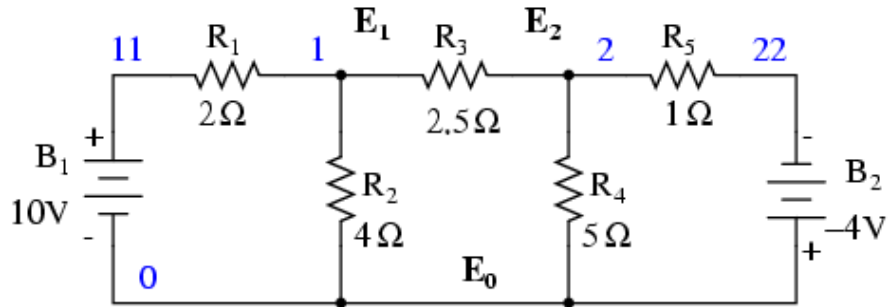- (b) Apply Kirchhoff's voltage law and find the current I_1 and I_2 and I_3 flowing in the given circuit using Cramer rule? CO1- App (16)



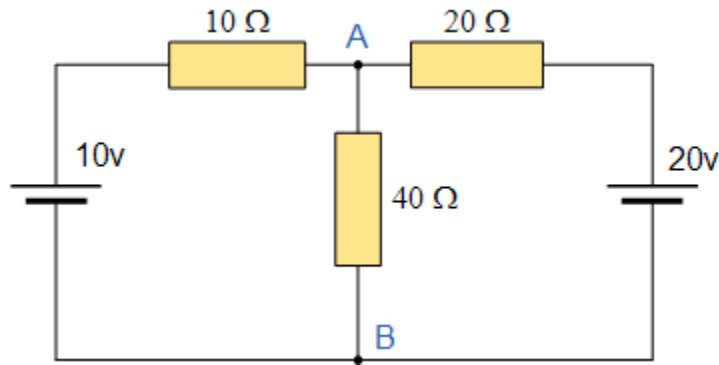17. (a) Using Thevenin's theorem, solve this problem and find the current flow through between Terminal A and Terminal B. CO2- U (16)



Or

- (b) Explain maximum power transfer theorem and derive the expression for maximum power transfer. CO2- U (16)
18. (a) The parameter of a RLC parallel circuit excited by a current source are $R = 40 \text{ Ohm}$, $L = 2 \text{ mH}$, $C = 3 \text{ Microfarad}$. Determine the CO3- Ana (16)
- (i) Resonant frequency
 - (ii) Quality factor
 - (iii) Bandwidth
 - (iv) Cut – off frequencies.

Or

- (b) Two coupled coils with $L_1 = 0.02 \text{ H}$, $L_2 = 0.01 \text{ H}$ and $K = 0.5$ are connected in our different ways, series Aiding, series opposing and Parallel Aiding and Parallel Opposition of the winding sense. What are the four equivalent inductances? CO3- Ana (16)
19. (a) A sinusoidal voltage of $10 \sin 100 t$ is connected in series with a switch and $R = 10 \text{ Ohm}$, $L = 0.1 \text{ H}$. If the switch is closed at $t = 0$, determine the transient current $i(t)$. CO4- U (16)
- Or
- (b) In the series R, L circuit resistance is 50 Ohm , and Inductance is 0.5 H and applied voltage is $e = 100 e^{-50 t}$. Find the
(i) Resulting current
(ii) Initial rate of change of current CO4- U (16)
20. (a) Explain the power and power factor measurements in three phase circuits. CO5- U (16)
- Or
- (b) (i) Mention some advantages of three Phase system over a Single Phase system? CO5- U (8)
(ii) Compare balanced network and unbalanced network CO5- U (8)