A Reg. No. :	
--------------	--

# **Question Paper Code: 56301**

## B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2019

### Sixth Semester

# Electrical and Electronics Engineering

	15UEE60	1- ADAVANCED EI	LECTRICAL AND (	CONTROL	
		(Regulat	ion 2015)		
Dur	ration: Three hours		Ī	Maximum: 100	Marks
		Answer AL	L Questions		
		PART A - (10	x 1 = 10  Marks)		
1.	In electrical drives the source to motor is	component which	is used to modulate	power from	CO1- R
	(a) Control unit	(b) Control comm	and (c) Power mo	odulator (d) S	Sensing unit
2.	The power modulator vDC voltage.	which is used to con	vert fixed DC voltag	ge to variable	CO1- R
	(a) Controlled rectifier		(b) Un-contro	olled rectifier	
3.	(c) Chopper drive is al	so called as Line sha	(d) AC voltage ft drive	ge controller	CO1- R
<i>J</i> .	(a) Individual drive	(b) Group drive	(c) Single drive	(d)Multi mot	or drive
4.	Full form of VVVF con	itrol			CO2- R
	<ul><li>(a) Variable voltage VAR frequency.</li><li>(c) Variable VAR voltage frequency.</li></ul>		` /	voltage variable able voltage fred	•
5.	The slip of an induction motor during DC rheostatic braking is		CO2- R		
	(a) 2-S	(b) S	(c) S-2		(d) 1-S
6.	For an IM to operate in	braking region slip s	hould be always		CO2- R

(b) Greater than 1

(c) is equal to 1

(d) None of these

(a) Less than zero

7.	Speed control by variation of field flux results in				CO2- R		
	(a) Co	(a) Constant power drive		(	(b) Constant torque drive.		
	(c) Va	ariable power driv	e	(	(d) None of the above	ve	
8.	Which	h type of Motor is	best suited for the exc	avator	?		CO3- R
	(a) D0	C Shunt Motor	(b) Differential Motor	(c) ]	DC series Motor (	d) Synchronou	ıs Motor
9.		hable Speed drive ample of	, Open Loop speed dr	ive, clo	osed loop speed driv	es are	CO3- R
	(a) Fix	xed speed Drive	(b) Variable Speed	drive	(c) Servo Drive	(d) Any of the	e above
10.		is the simu	lation language.				CO3- R
	(a) GI	PSS	(b) JAVA		(c) Java script	(d) No	one
			PART – B (5 x	2= 10	Marks)		
11.	Draw	the circuit diag	ram for single phase	semi-	converter fed Sepa	rately	CO1- R
	excite	ed DC motor drive					
12.	Name some power modulators. Also list their functions. CO1-						
13.	6. What is meant by stator voltage control?						CO2- R
14.	What are the three regions in the speed-torque characteristics in the IM? CO2-1						
15. Mention the use of simulation software packages.						CO3- R	
			PART - C (5	x 16=	80 Marks)		
16.	(a)	Derive the fund load dynamics.	lamental torque equat	tions g	soverning DC Moto	r CO1-U	(16)
			Or				
	(b)	-	power circuit the wor	_		1 CO1- U	(16)
17.	(a)	drive with neat	veration of $3\varphi$ fully c waveforms for $\alpha=30$ out the waveforms.				(16)
			Or				
	(b)	-	l with an example, Mun speed-torque plane.	alti-Qu	adrant operation of	a CO1- Ana	(16)

18. (a) Explain the reason behind operating an induction motor with CO2- Ana constant voltage and variable frequency. Draw the appropriate speed-torque characteristics.

Or

- (b) Draw and explain the speed-torque characteristics of the CO2- Ana (16) induction motor.
- 19. (a) Design a circuit and explain the concept of closed loop control of CO2- U (16) 3-phase VSI fed induction motor.

Or

- (b) Explain the speed control scheme employed in industries for CO2-U induction motor drive with stator voltage control and mention the reason for choosing induction motor drive rather than other motor drives.
- 20. (a) Drive the transfer functions of DC motor drive and explain DC CO3-U (16) motor drive in detail.

Or

(b) Explain the operations of armature voltage control and field CO3-U (16) weakening control.