

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 21012

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2014.

Second Semester

Electronics and Instrumentation Engineering

01UEI207 - ELECTRONIC DEVICES AND CIRCUITS

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 2 = 20 Marks)

1. Define Doping.
2. Define cutoff and active region of a transistor.
3. Write Shockley's equation.
4. What is the major difference in construction of the D-MOSFET and the E-MOSFET?
5. Why do we choose Q point at the center of the load line?
6. What is biasing?
7. What is sustained oscillation?
8. What is feedback amplifier?
9. Draw a practical Clamper circuit.
10. What is UJT?

PART - B (5 x 16 = 80 Marks)

11. (a) Explain the operation of forward biased and reverse biased PN junction Diode. (16)

Or

- (b) Draw and explain the input and output characteristics of a transistor in CE configuration. (16)
12. (a) Explain the working of a P channel JFET and draw the V-I characteristics of it. (16)

Or

- (b) Explain the working of a N-channel depletion-mode MOSFET. (16)
13. (a) Design an amplifier with CE configuration and analyze its characteristics. (16)

Or

- (b) Explain complementary symmetry power amplifier with neat circuit diagram. (16)
14. (a) Draw the circuit diagram of a current series feedback amplifier and derive expressions for voltage gain with feedback. (16)

Or

- (b) Explain the working of Colpitt's oscillator and derive an expression for frequency of oscillation for Colpitt's oscillator. (16)
15. (a) With a neat sketch, explain the working of an astable multivibrator. (16)

Or

- (b) Explain the working principle of switched mode power supplies. (16)
-