

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 41352

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2016

Third Semester

Electronics and Instrumentation Engineering

14UEI302 - LINEAR INTEGRATED CIRCUITS AND APPLICATIONS

(Regulation 2014)


Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

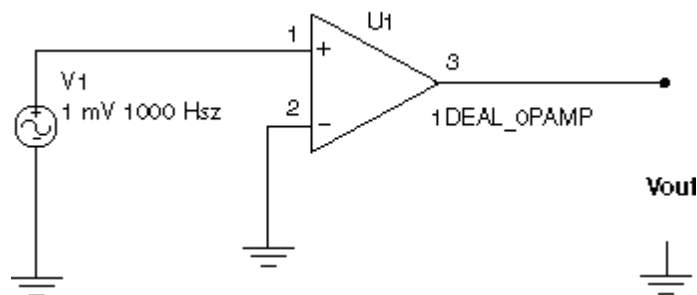PART A - (10 x 1 = 10 Marks)

- An ideal operational amplifier has
 - infinite output impedance
 - zero input impedance
 - infinite bandwidth
 - all of the above
- Input impedance of an inverting amplifier is approximately equal to
 - R_i
 - $R_f + R_i$
 - ∞
 - $R_f - R_i$
- Evaluate the output waveform of the circuit?



- sine wave
- square wave
- sawtooth wave
- triangle wave

PART - C (5 x 16 = 80 Marks)

16. (a) Explain briefly about fabrication process of monolithic ICs. (16)

Or

(b) (i) Sketch the internal circuit of an op-amp. (6)


(ii) Discuss in detail about ideal op-amp characteristics. (10)

17. (a) (i) Illustrate briefly about op-amp summer. (8)

(ii) Prove that op-amp acts as an integrator. (8)

Or

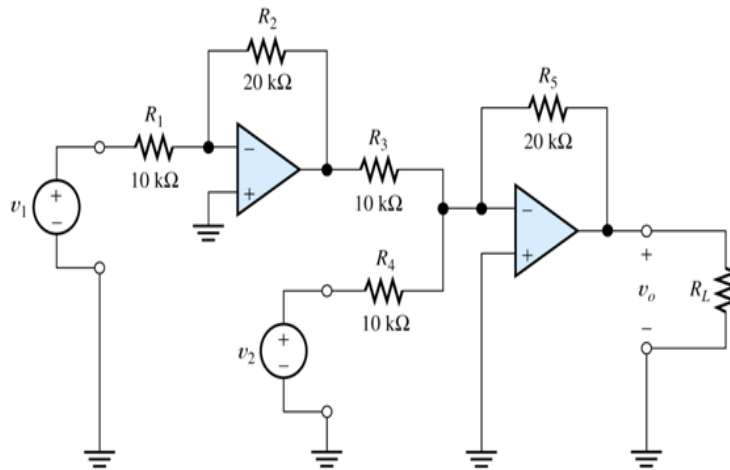(b) (i) Deduce the expression for the output voltage in the amplifier circuit. (10)



(ii) Experiment the methods of improving slew-rate in two-stage Op-amps. (6)

18. (a) (i) With neat circuit diagram explain about instrumentation amplifier. (10)

(ii) Discuss about R-2R ladder network for D/A converters briefly. (6)

Or

(b) (i) Explain the principle of operation of successive approximation ADC. (8)

(ii) Draw and explain about sample and hold circuits. (8)

19. (a) (i) Derive the expression for voltage to frequency conversion factor. (6)

(ii) Describe the application of PLL. (10)

Or

- (b) (i) What is 555 timer? What are the features of 555 timer? Explain the monostable mode in detail? (10)
- (ii) Derive the expression for frequency of oscillation in monostable mode. (6)
20. (a) (i) Design a adjustable voltage regulator using IC 723 to obtain positive low voltage and high voltage. (10)
- (ii) Write short notes on opto couplers? (6)

Or

- (b) (i) Discuss in detail about isolation amplifier. (8)
- (ii) Explain the functional diagram of LM 380 power amplifier. (8)
-