

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 31442

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2016

Fourth Semester

Electronics and Communication Engineering

01UEC402 – ANALOG CIRCUITS

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. What are the essential conditions for maintaining oscillations in a circuit?
2. A certain X-cut quartz crystal resonates at 500 kHz. It has equivalent inductance of 4.2 H and an equivalent capacitance of 0.03 pF. If its equivalent resistance is 500 Ω , calculate the Q-factor.
3. Define duty cycle D.
4. What is a multi-vibrator? How are they classified?
5. List the limitations of integrated circuits.
6. The output voltage of a certain op-amp circuit changes by 20 V in 4 μ s. Find its slew rate.
7. Draw the circuit of a voltage to current converter with floating load.
8. Define capture range, lock-in range and pull-in-time of a PLL.
9. List the various A/D conversion techniques.
10. What are the modes of operation of a timer?

PART - B (5 x 16 = 80 Marks)

11. (a) Draw the circuit of Hartley oscillator and explain its working. Derive the expressions for frequency of oscillation and condition for starting of oscillation. (16)

Or

- (b) Describe the construction of phase shift oscillator and explain its working. (16)

12. (a) Give a detailed account of diode clippers. (16)

Or

- (b) Calculate the component values of a monostable multivibrator developing an output pulse of $140 \mu s$ duration. Assume $h_{FEmin} = 20$, $I_{c(sat)} = 6 mA$, $V_{CC} = 6 V$, $V_{BB} = -1.5 V$. (16)

13. (a) Explain the construction of a monolithic bipolar transistor with neat diagrams. (16)

Or

- (b) (i) Discuss the various operational amplifier stages. (6)
(ii) Explain the open loop op-amp configurations in detail. (10)

14. (a) Discuss the operation of logarithmic amplifiers in detail. (16)

Or

- (b) Write short notes on
(i) Peak detector
(ii) Voltage controlled oscillators. (16)

15. (a) Discuss the various types of DACs in detail. (16)

Or

- (b) Explain the construction and various features of 723 general purpose regulators. (16)
-