

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 31232

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2016

Second Semester

Computer Science and Engineering

01UEE207 - ELECTRIC CIRCUITS

(Common to EEE, ECE, EIE, ICE and IT)

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks


Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. Define Kirchhoff's law.
2. What is an ideal source?
3. State maximum power transfer theorem.
4. Write some applications of maximum power transfer theorem.
5. Define Q-factor of a coil.
6. What is co-efficient of coupling?
7. Define time constant for RL transient circuit.
8. Distinguish steady state and transient state.
9. When a three phase supply system is called balanced supply system?
10. What are the advantages of 3-phase system over 1-phase system?


PART - B (5 x 16 = 80 Marks)

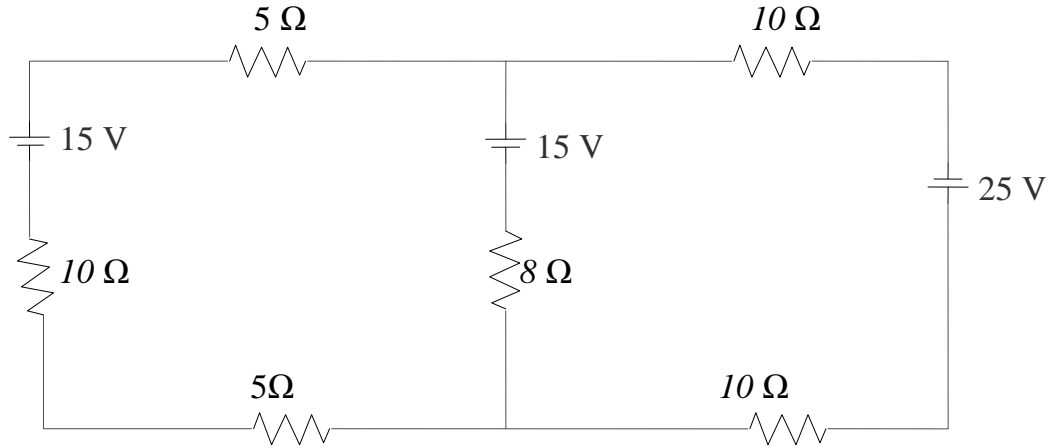11. (a) Use mesh analysis to determine the current in 8Ω resistor as shown in the circuit diagram. (16)




Or

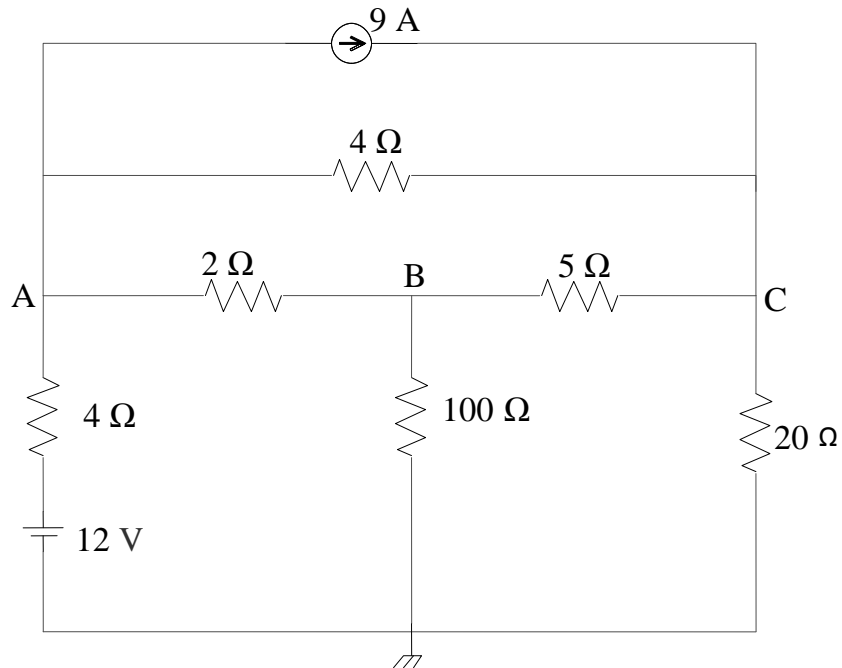- (b) Using nodal analysis determine the voltage across 5Ω resistor and current in $12V$ source of the figure shown below. (16)




12. (a) (i) State and explain Reciprocity and superposition theorems. (8)

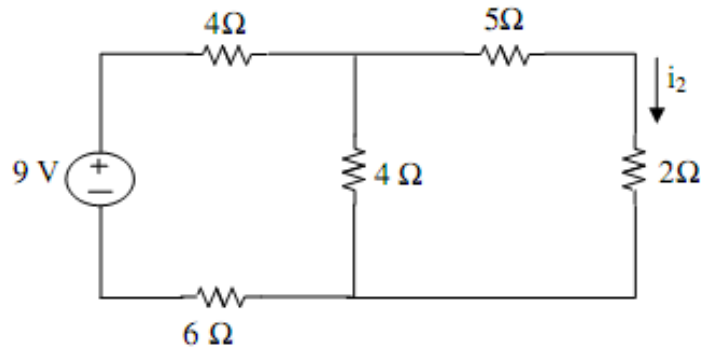- (ii) Use Thevenin's theorem to find the current through the 2Ω resistor in the circuit shown in figure. (8)




Or

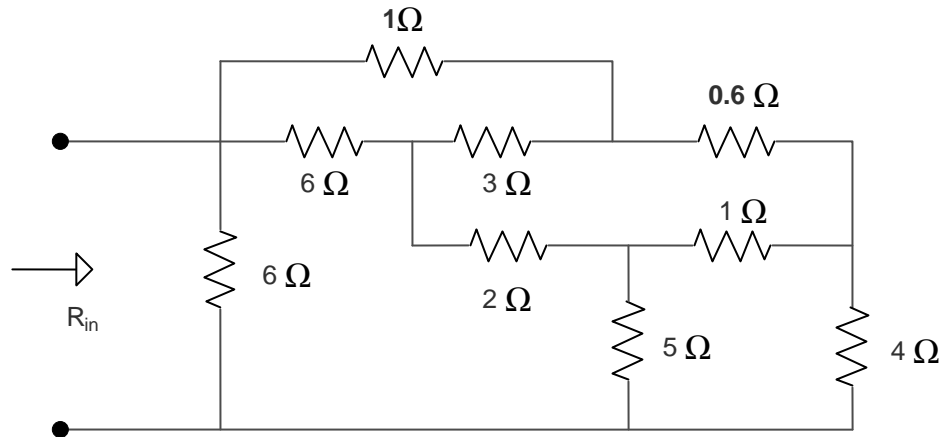- (b) Find R_{in} for the network shown in figure, by using $Y - \Delta$ and $\Delta - Y$ transformations. (16)



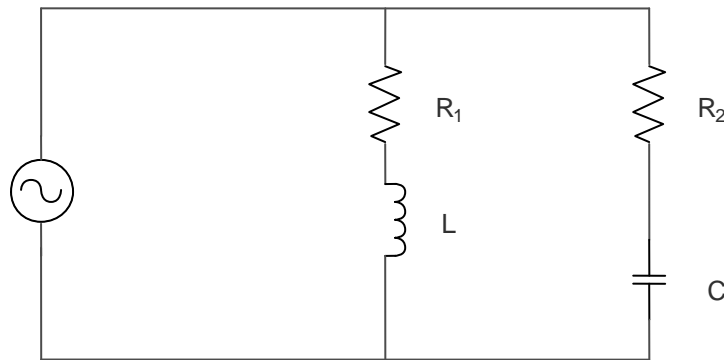13. (a) For the parallel circuit shown in figure, find the Resonance frequency f . (16)




Or

- (b) Discuss about Single tuned and Double tuned circuits. (16)

14. (a) Derive the expression for transient response in series R-L-C circuit for DC excitation. Obtain the solution using Laplace transforms. (16)

Or

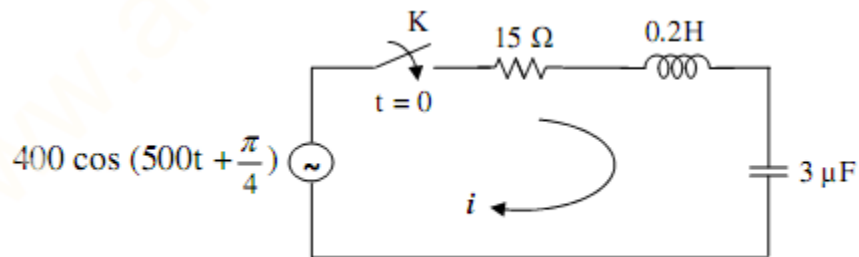- (b) Determine complete solution for current, when switch K is closed at $t = 0$ for applied voltage $v(t) = 400\cos(500t + \pi/4)$. Derive the expression for the current. (16)



15. (a) (i) Derive the formula for total power consumed in unbalanced Y connected load. (8)
- (ii) Explain a method to determine power factor in 3-phase system. (8)

Or

- (b) A balanced three phase system supplies an unbalanced delta connected load made of two resistors of 100Ω and 200Ω and a coil having an inductance of $0.3 H$ with negligible resistance. The line to line voltage is $100 V$ and the supply frequency is $50 Hz$. Calculate
- (i) The total power in the system
- (ii) The total reactive power. (16)