

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 52B08A

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2019

Second Semester

Biomedical Engineering

15UBM208 - ELECTRICAL CIRCUITS ANALYSIS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Resistors are circuit elements that resist the flow of CO1- R
(a) Current (b) Voltage (c) Power (d) Energy
- Mesh analysis is based on CO1- R
(a) Kirchhoff's current law (b) Kirchhoff's voltage law (c) Source (d) Load
- In superposition theorem, the independent current sources must be replaced by CO2- R
(a) Active elements (b) Short circuit
(c) Open circuit (d) Linear bilateral elements
- Maximum power is transferred when load impedance is CO2- R
(a) Equal to source impedance (b) Equal to half of the source impedance
(c) Equal to zero (d) None of the above
- What is the total reactance of a series RLC circuit at resonance? CO3- R
(a) Equal to X_L (b) Equal to X_C (c) Equal to R (d) Zero
- Mutual inductance is a property associated with CO3- R
(a) Only one coil (b) Two or more coils
(c) Two or more coils with magnetic coupling (d) None of the above

7. A network in which branch current and node voltages are not changing with respect to time is said to be CO4- R
- (a) Transition period (b) Transient response
(c) Excitation (d) Steady state
8. The time constant of a series RL circuit is CO4- R
- (a) LR (b) L/R (c) R/L (d) 0
9. Three phase system give _____ output. CO5- R
- (a) DC (b) Constant
(c) Steady (d) Poor
10. Wattmeter deflection in AC circuit is proportional to the CO5- R
- (a) Maximum power in the circuit (b) Instantaneous power in the circuit
(c) Average power in the circuit (d) Half power in the circuit

PART – B (5 x 2= 10 Marks)

11. Name different network elements CO1- R
12. Three equivalent resistances of 3Ω are connected in delta circuit. Obtain the equivalent star connected circuit. CO2- R
13. Define the dot rule for coupled circuits CO3- R
14. Define time constant of RL and RC circuit. CO4- R
15. State the relation between the line and phase quantities of a balanced three-phase wye connected system. CO5- R

PART – C (5 x 16= 80 Marks)

16. (a) (i) Explain the classification of electrical networks CO1-U (8)
(ii) State and explain Kirchhoff's laws CO1-U (8)
- Or
- (b) Using mesh analyses find the three loop current in the circuit given in figure. 16.(b) CO1-App (16)


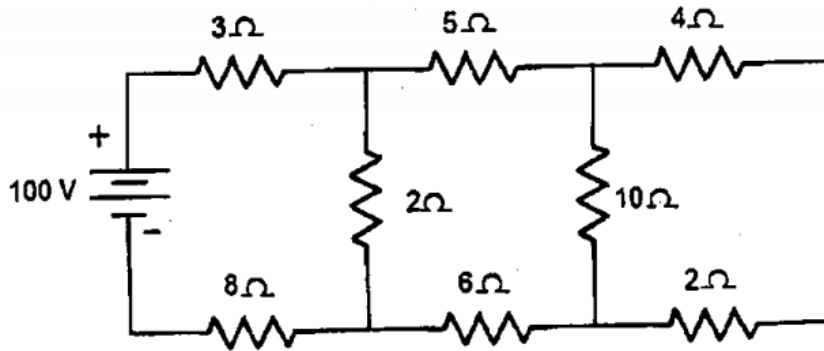


Figure. 16(b).

17. (a) A linear time invariant network when terminated with i) $R = 1\Omega$, the current is $5 \angle -45^\circ$ A ii) $X_C = 1\Omega$, the current is $10 \angle -45^\circ$ A. Find the thevenin's equivalent of the network. What will be the current if it is terminated with $X_L = 1\Omega$.

Or

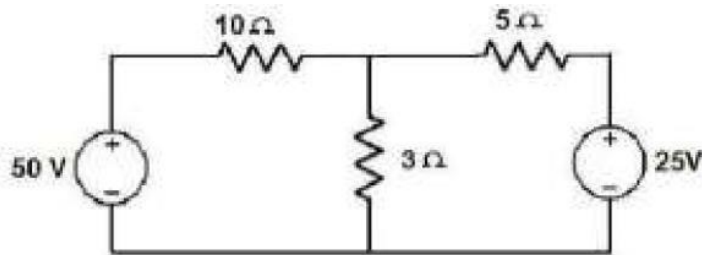- (b) Find the current in each resistor using superposition principle of



18. (a) In series RLC circuit with variable capacitance, the current is at maximum value with capacitance of $20 \mu\text{F}$ and the current reduces to 0.707 times maximum value with capacitance of $30 \mu\text{F}$. Find the values of R and L. What is the bandwidth of circuit if supply voltage is $20 \sin(6.28 \times 10^3 t)$ volts.

Or

- (b) Determine the half power frequencies Bandwidth, the quality factor of a coil for the series circuit consisting of $R=10 \Omega$, $L= 0.1$ H and $C= 10\mu\text{F}$.

19. (a) Derive and determine the DC response of an RL Series circuit and also find the voltage across the resistance and Inductance of the DC response.

Or

- (b) A RC series circuit is connected to a DC source of 100V through a switch. A switch is closed at time $t = 0$. Find the value of voltage and current at $t = 5\text{msec}$. When the value of R and C are 100Ω ohm and 100 mF, respectively. CO4- U (16)
20. (a) A three-phase balanced delta-connected load of $(4+j8)\Omega$ is connected across a 400 V, 3phase balanced supply. Determine the phase currents and line currents. Assume the phase sequence to be RYB. Also, calculate the power drawn by the load. CO5- U (16)
- Or
- (b) Unbalanced four wire star connected load has balanced supply voltage of 400V. The load impedances are $Z_R = (4 + j8)\Omega$, $Z_Y = (4 + j8)\Omega$ and $Z_B = (4 + j8)\Omega$. Calculate the line currents, neutral current and total power. CO5- U (16)