

7. The logic circuit whose output at any instant of time depends only on the present input but also on the past outputs is _____.
- (a) Flip-flops (b) Combinational circuits
(c) Latches (d) Sequential circuits
8. For JK flip Flop with J=1, K=0, the output after clock pulse will be
- (a) 0 (b) 1
(c) high impedance (d) No change
9. Table that is not a part of asynchronous analysis procedure is_____.
- (a) flow table (b) excitation table (c) state table (d) transition table
10. Present states of asynchronous circuits are also called as
- (a) Secondary Variables (b) Primary Variables
(c) Excitation Variables (d) Short term Memories

PART – B (5 x 2= 10Marks)

11. List the number systems CO1-R
12. What is code conversion? CO2-R
13. List basic types of programmable logic devices CO3-U
14. What is the difference between synchronous and asynchronous counter? CO4-R
15. List out the steps for the design of asynchronous sequential circuit CO5-R

PART – C (5 x 16= 80Marks)

16. (a) (i) Explain BCD Code with Examples. CO1-U (10)
(ii) Describe negative and positive logic. CO1-U (6)
- Or
- (b) Minimize the following Boolean expression using Boolean identities $F(A, B, C)=A'B+BC'+BC+AB'C'$. CO1-U (16)
17. (a) Write short notes on: BCD adder, Binary multiplier and Magnitude Comparator CO2-U (16)

Or

- (b) Describe and design a combinational circuit to convert binary code to gray code. CO2-U (16)
18. (a) Implement the combinational circuit with a PLA having 3 inputs, 4 product terms and 2 outputs for the functions $F_1 = \sum m(3, 5, 6, 7)$, $F_2 = \sum m(0, 2, 4, 7)$. CO3-App (16)
- Or
- (b) Design using PLA. CO3-App (16)
- $A(x,y,z) = \sum m(1,2,4,6)$
- $B(x,y,z) = \sum m(0,1,6,7)$
- $C(x,y,z) = \sum m(2,6)$
19. (a) Using JK flip flops, design a parallel counter which counts in the sequence 000,111,101,110,001,010,000& repeats. CO4-App (16)
- Or
- (b) Consider the design of 4-bit BCD counter that counts in the following way: 0000, 0001, 0010... 1001 and back to 0000. Draw the logic diagram of this circuit and describe it. CO4-App (16)
20. (a) Design an asynchronous circuit that has two inputs x_1 and x_2 and one output Z. the circuit is required to give an output whenever the input sequence (0, 0) (0, 1) and (1, 1) received but only in that order. CO5-App (16)
- Or
- (b) For a given Boolean function obtain the hazard free circuit and examine it. $F(A,B,C,D) = \sum m(1,3,6,7,13,15)$ CO5-App (16)

