

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 55402A

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2019

Fifth Semester

Electronics and Communication Engineering

15UEC502 - TRANSMISSION LINES AND WAVEGUIDES

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. One Neper is equal to CO1- R
(a) 9.686 db (b) 8.686 db (c) 7.686 (d) 8.565
2. A line of finite length, terminated in a load equivalent to its CO2-R
characteristic impedance, appears to sending end generator as
(a) Infinite line (b) Finite line
(c) Finite line with fixed value (d) None of the above
3. Give the minimum and maximum value of reflection co-efficient CO3-R
(a) $1 < K < 10.5$ (b) $1 < k < \alpha$ (c) $0 < K < \alpha$ (d) $0 < k < 1$
4. There is no electric field can exist in the direction of the magnetic CO4-R
field such a wave is said to be
(a) TE wave (b) TM wave (c) TEM wave (d) Quasi TM wave
5. The frequency at which the wave motion ceases CO5-R
(a) Flat Line (b) Zero frequency
(c) Attenuation frequency (d) Cut-off frequency

PART – B (5 x 3= 15 Marks)

6. What is symmetrical Network? CO1- U
7. How are practical lines made appear as infinite line? CO2- U
8. Give the name of circles on smith chart. CO3- U
9. What is the use of attenuators? CO4- U

10. What is cavity resonators?.

CO5- U

PART – C (5 x 16= 80Marks)

11. (a) Design an m derived LPF having cut off frequency= 1 KHz. Design impedance of 400Ω and resonant frequency 1100 Hz. CO1- App (16)
- Or
- (b) Explain the properties of symmetrical network with relevant equations CO1- U (16)
12. (a) Explain the concept of transmission line as cascaded T section with mathematical expression. CO2- U (16)
- Or
- (b) Describe input impedance of open and short circuited lines, and plot the variation of input impedance of dissipation line as a function of length for open and short line. CO2- U (16)
13. (a) Derive the expression for voltage and currents on dissipation less line along with line constant for zero dissipation. CO3- U (16)
- Or
- (b) A 50 ohms transmission line is connected to a cellular phone antenna with load impedance $Z_L=25-j50$ ohm. Find the location and length of the short circuited stub required to match with 50 ohms. CO3- U (16)
14. (a) Explain the behavior of electromagnetic waves between parallel planes using maxwell's equation. CO4- U (16)
- Or
- (b) Explain the characteristic impedance of different Modes in Parallel planes CO4- U (16)
15. (a) Derive the expression for TM waves in rectangular waveguides. CO5- U (16)
- Or
- (b) (i) Describe cavity resonator. CO5- U (8)
- (ii) Deduce the expression for resonant frequency of the rectangular cavity resonator for any given mode. CO5- U (8)