

Reg. No. :

|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code: 95T14**

Ph.D. COURSE WORK EXAMINATION, NOV 2019

Elective

Power electronics and Drives

19PPE514 – DIGITAL SIMULATION OF POWER ELECTRONIC SYSTEMS

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

1. (a) Elucidate the theory of computer formulation of digital equations with neat flow chart. CO1- U (20)

Or

- (b) Explain about the various methods of analysis of power electronic systems. Mention the importance of digital simulation. CO1- U (20)

2. (a) Elucidate the theory of formulation of proper tree algorithm with neat diagrams. CO2- U (20)

Or

- (b) Explain with neat diagram the formulation of fundamental cutset matrix. CO2- U (20)

3. (a) Draw the equivalent circuit for three phase induction machine. Also Derive the electromagnetic torque equation. CO3- U (20)

Or

- (b) Explain in detail about State Space Modelling. Derive the State Space Model for Induction machine for Control and Monitoring Purpose. CO3- U (20)

4. (a) Explain the operation of three phase fully controlled bridge rectifier (six pulse converter) with RLE load and draw the necessary wave forms. CO4- U (20)

Or

- (b) Derive the transfer function for the three phase fully controlled bridge converter for simulation using using pspice simulator. CO4- U (20)
5. (a) Draw the power circuit arrangement of three phase variable frequency inverter for the speed control of three phase induction motor and explain its working using DSP Controller. CO5- U (20)

Or

- (b) Simulate the pspice model of Half and Full Wave rectifier using PSPICE Simulator. CO5- U (20)