

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 91T01

M.E. DEGREE EXAMINATION, NOV 2019

First Semester

Power Electronics and Drives

19PPE101– POWER ELECTRONIC CONVERTERS

(Regulation 2019)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART - A (5 x 20 = 100 Marks)

1. (a) Explain the construction, the static and switching characteristics of IGBT with neat diagrams. CO1- U (20)

Or

- (b) Explain the switching characteristics of BJT and give the reason for storage time in power transistors. CO1- U (20)

2. (a) Analyze the performance of single phase half controlled converter with RLE load both in continuous and discontinuous mode of operation. CO2- Ana (20)

Or

- (b) Analyze the performance of three phase half controlled converter with RLE load both in continuous and discontinuous mode of operation. CO2- Ana (20)

3. (a) Dissect the different stages of snubber circuit design for DC-DC converter. CO3- U (20)

Or

- (b) Explain the modes of operation of cuk converter with necessary waveforms. CO3- U (20)

4. (a) Interpret the 180° conduction mode of operation of a three phase inverter with star connected resistive load. CO4- U (20)

Or

(b) Compare multilevel inverters and discuss some applications of multilevel inverter. CO4- U (20)

5. (a) Analyze the working of single-phase bi-directional controllers with R, L and R-L loads. CO5- Ana (20)

Or

(b) Analyze the working of three-phase bi-directional controllers with R, L and R-L loads. CO5- Ana (20)