

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 59501

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Elective

Electronics and Instrumentation Engineering

15UEI901– VLSI SYSTEM DESIGN

(Regulation 2015)

Duration: 1.15 hrs

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

(Answer any six of the following questions)

- Which technology has photo-electronic properties? CO1-R
(a) GaAs (b) BiCMOs (c) CMOS (d) nMOS
- Approximately how many numbers of transistors per chip is available in MSI CO1-R
(a) 10-100 (b) 100-1,000 (c) 1,000-10,000 (d) > 10,000
- In the design rules the implant layer has CO2-R
(a) $2\lambda \times 2\lambda$ (b) $4\lambda \times 4\lambda$ (c) $6\lambda \times 6\lambda$ (d) $8\lambda \times 8\lambda$
- The ratio of pull-up to pull-down for an inverter directly driven by an inverter is CO2-R
(a) 2/1 (b) 3/2 (c) 8/1 (d) 4/1
- Precharge low circuits are slower to pull up than precharge high circuits are to pull down. This statement is _____. CO3-R
(a) True (b) False (c) based on logic (d) based on clock
- Barrel shifter requires _____ control lines. CO3-R
(a) 2N (b) N^2 (c) $2N^2$ (d) N
- The line connecting OR Plane and AND Plane in an NMOS PLA is called CO4-R
(a) Product line (b) Sum line (c) Connector (d) Interconnection

8. PLA contains CO4-R
 (a) AND and OR arrays (b) NAND and OR arrays
 (c) NOT and AND arrays (d) NOR and OR arrays
9. _____ is used for local storage of temporary data, visible only inside a process. CO5-R
 (a) Signal (b) Variable (c) Constant (d) Entity
10. The full form of VHDL is CO5-R
 a) Very High Descriptive Language
 (b) Very High Definition Language
 (c) Variable Definition Language
 (d) None of the Mentioned

PART – B (3 x 8= 24 Marks)

(Answer any three of the following questions)

11. Discuss in detail about the modes of operation of MOS transistor with necessary equations. CO1- U (8)
12. Determine the pull up to pull-down ratio of nMOS Inverter driven by another nMOS Inverter. CO2 -U (8)
13. Design an 4 x 4 Barrel Shifter and explain its operation. CO3- App (8)
14. What is programmable logic devices? Explain the different types of PLD in detail CO4- App (8)
15. Explain in detail about the design procedure of RTL. CO5- U (8)

