

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 56403**

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Sixth Semester

Electronics and Communication Engineering

15UEC603- VLSI DESIGN

(Regulation 2015)

Duration: 1.15 hrs

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

**(Answer any six of the following questions)**

- In continuous assignment left hand side must be CO1-R  
(a) Net                      (b) Reg                      (c) Scalar or vector net                      (d) Scalar or vector reg
- The primary mechanisms for modeling the behavior of a Verilog design needs CO1- R  
(a) Initial statement      (b) Always statement      (c) Both (a) and (b)                      (d) Only (a)
- CMOS technology is used in developing CO2-U  
(a) Microprocessors                      (b) Microcontrollers  
(c) Digital logic circuits                      (d) all of the mentioned
- In CMOS fabrication, the photoresist layer is exposed to CO2- R  
(a) visible light      (b) infra red light                      (c) ultraviolet light                      (d) fluorescent
- In CMOS circuits, which type of power dissipation occurs due to switching of transient current and charging & discharging of load capacitance? CO3-U  
(a) Static dissipation                      (b) Dynamic dissipation  
(c) Both a and b                      (d) None of the above
- The number of pass transistors connected in series can be increased if CO3- R  
(a) Compressor is connected                      (b) Ground is connected  
(c) Voltage regulator is connected                      (d) Buffer is connected

7. Charge leakage and noise margin problems can be addressed by adding \_\_\_\_\_ CO4-U  
 (a) Keeper circuit (b) domino gate (c) pass transistor (d) transmission gate
8. In CMOS NAND gate, p transistors are connected in \_\_\_\_\_ CO4- R  
 (a) Series (b) Parallel (c) Cascade (d) Random
9. The number of test vectors for exhaustive testing is calculated by \_\_\_\_\_ CO5-A  
 (a)  $2^{(m+n)}$  (b)  $2^{((m+n)/2)}$  (c)  $2^{(m-n)}$  (d)  $2^{2(m+n)}$
10. The process of removing equivalent faults is called as \_\_\_\_\_ CO5- R  
 (a) Equivalent removing (b) Fault collapsing  
 (c) Fault reduction (d) Bulk damaging

PART – B (3 x 8= 24 Marks)

**(Answer any three of the following questions)**

11. Write a Verilog program for 2 to 4 decoder in dataflow modeling and behavioral modeling. CO1-U (8)
12. Explain in detail DC transfer characteristic of CMOS inverter CO2-U (8)
13. Analyze the static and dynamic power dissipation in CMOS circuits with necessary diagrams and expressions. CO3-Ana (8)
14. Discuss the comparison of circuit families CO4 -U (8)
15. Describe the scan based approaches and built in self-test to design for testability in detail. CO5- U (8)