

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 33403**

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electronics and Communication Engineering

01UEC303 - CIRCUIT THEORY

(Regulation 2013)

Duration: One hour

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

**(Answer any six of the following questions)**


- The number of independent loops for a network with  $n$  nodes and  $b$  branches is
  - $n-1$
  - $b-n$
  - $b-n+1$
  - independent for the number of nodes
- Mesh analysis makes use of the basic equation
  - $[V] = [Z] [I]$
  - $[I] = [Z] [V]$
  - $[V] = [Y] [I]$
  - $[I] = [Y] [V]$
- Superposition theorem is not applicable to networks containing
  - nonlinear elements
  - dependent voltage source
  - dependent current source
  - transformers
- Maximum power gets transferred to the load when the load impedance is
  - equal to zero
  - equal to one
  - equal to source impedance
  - none of the above
- What is the  $Q$  (Quality factor) of a series circuit that resonates at  $6\text{ kHz}$ , has equal reactance of  $4\text{ kilo-ohms}$  each, and a resistor value of  $50\text{ ohms}$ ?
  - 0.001
  - 50
  - 80
  - 4.0

6. The Q-factor in a series R-LC circuit at resonance is
- (a)  $\frac{1}{R} \sqrt{\frac{C}{L}}$                       (b)  $\frac{1}{L} \sqrt{\frac{C}{R}}$                       (c)  $\frac{1}{R} \sqrt{\frac{L}{C}}$                       (d)  $\frac{1}{R^2} \sqrt{\frac{C}{L}}$
7. Self-inductance of a magnetic coil is proportional to
- (a)  $N$                                       (b)  $1/N$                                       (c)  $N^2$                                       (d)  $1/N^2$
8. In two wattmeter method of power measurement, when the power factor of load is zero leading or lagging the two wattmeter will give\_\_\_\_\_ reading.
- (a) Zero                                      (b) equal  
(c) equal and opposite                      (d) not equal
9. Which parameters are widely used in transmission line theory?
- (a) Z parameters                                      (b) Y parameters  
(c) ABCD parameters                                      (d) h parameters
10. The number of possible combinations generated by four variables taken two at a time in a two port network is
- (a) Four                                      (b) Two                                      (c) Six                                      (d) Zero


PART – B (3 x 8= 24 Marks)

(Answer any three of the following questions)

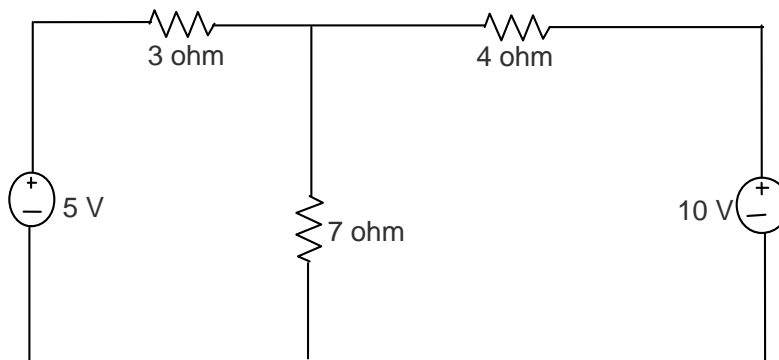11. Draw the dual network of the given circuit. (8)



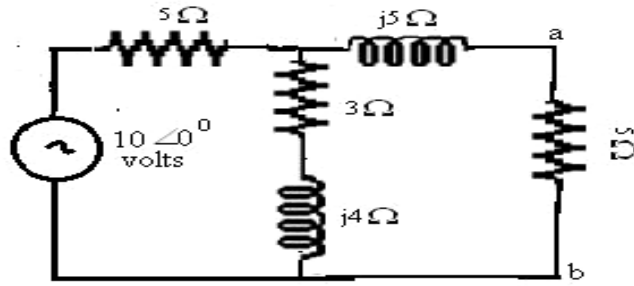12. State the Thevenin's theorem and find the current through branch a-b of the network shown in below figure. (8)



13. A voltage  $v(t) = 10 \sin \omega t$  is applied to a series RLC circuit. At the resonant frequency of the circuit, the maximum voltage across the capacitor is found to be 500V. Moreover the bandwidth is known to be 400 rad/sec and the impedance at resonance is 100Ω. Find the resonant frequency. Also find the values of  $L$  and  $C$  of the circuit. (8)
14. Explain the single tuned circuit with neat diagram and obtain the gain and mutual inductance. (8)
15. Convert the given T-network to a  $\Pi$  network. (8)

