



7. The voltage needed for a TTL IC power supply is  
 (a) 5V dc                      (b) 10 V dc                      (c) 2 V dc                      (d) 20 V dc
8. Which of the following memories in non-volatile memory?  
 (a) ROM                              (b) PROM  
 (c) Ferrite core memory              (d) None of these
9. A circuit which do not operate in synchronous with clock signal is  
 (a) Synchronous sequential circuits              (b) Asynchronous sequential circuits  
 (c) FPGA                              (d) combinational circuits
10. In this mode the inputs and outputs are represented by levels  
 (a) Fundamental mode                              (b) Pulse mode  
 (c) Both (a) and (b)                              (d) None of these

PART – B (3 x 8= 24 Marks)

**(Answer any three of the following questions)**

11. Realize the following function as Multilevel NAND –NAND gate and Multilevel NOR –NOR gate  

$$F = \bar{A} B + B (C + D) + E\bar{F} (\bar{B} + \bar{D}) \quad (8)$$
12. With logic diagram Truth table and explain about 3-to-8 decoder. (8)
13. With neat diagram explain in detail about how the race around condition is avoided in master-slave JK flip-flop. (8)
14. With block diagram explain about PLA and realize the following functions in PLA:  

$$F1 = \bar{A} B \bar{C} + A \bar{B} C + \bar{A} B C \quad (8)$$

$$F2 = A B + AC + \bar{A}BC$$
15. Develop VHDL code for 3 to 8 decoder. (8)