

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 43403

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electronics and Communication Engineering

14UEC303 - CIRCUIT THEORY

(Regulation 2014)

Duration: One hour

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

(Answer any six of the following questions)


- The number of independent loops for a network with n nodes and b branches is
 - $n-1$
 - $b-n$
 - $b-n+1$
 - independent for the number of nodes
- Mesh analysis makes use of the basic equation
 - $[V] = [Z] [I]$
 - $[I] = [Z] [V]$
 - $[V] = [Y] [I]$
 - $[I] = [Y] [V]$
- Superposition theorem is not applicable to networks containing
 - nonlinear elements
 - dependent voltage source
 - dependent current source
 - transformers
- Maximum power gets transferred to the load when the load impedance is
 - equal to zero
 - equal to one
 - equal to source impedance
 - none of the above
- What is the Q (Quality factor) of a series circuit that resonates at 6 kHz , has equal reactance of 4 kilo-ohms each, and a resistor value of 50 ohms ?
 - 0.001
 - 50
 - 80
 - 4.0
- The Q -factor in a series R-LC circuit at resonance is
 - $\frac{1}{R} \sqrt{\frac{C}{L}}$
 - $\frac{1}{L} \sqrt{\frac{C}{R}}$
 - $\frac{1}{R} \sqrt{\frac{L}{C}}$
 - $\frac{1}{R^2} \sqrt{\frac{C}{L}}$

7. Self-inductance of a magnetic coil is proportional to
 (a) N (b) $1/N$ (c) N^2 (d) $1/N^2$
8. In two wattmeter method of power measurement, when the power factor of load is zero leading or lagging the two wattmeter will give _____ reading.
 (a) Zero (b) equal
 (c) equal and opposite (d) not equal
9. Which parameters are widely used in transmission line theory?
 (a) Z parameters (b) Y parameters
 (c) ABCD parameters (d) h parameters
10. The number of possible combinations generated by four variables taken two at a time in a two port network is
 (a) Four (b) Two (c) Six (d) Zero

PART – B (3 x 8= 24 Marks)


(Answer any three of the following questions)

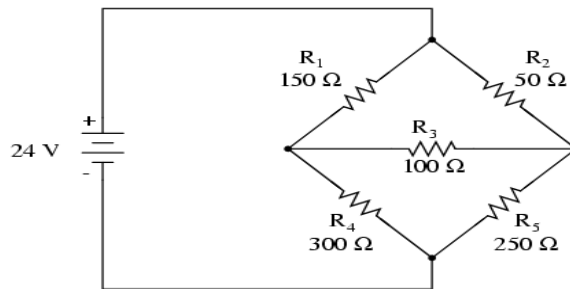11. Find the mesh currents for the following electric circuit shown in Figure (8)



Figure

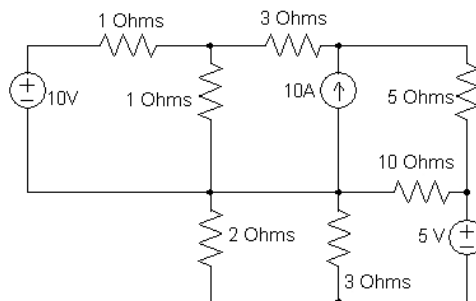12. Determine the current in 2 ohm resistor for the electric circuit shown in Figure using superposition theorem. (8)




Or

13. Obtain the resonant frequency, Q-factor, band width and the voltage across the capacitor at resonance for the series RLC circuit having $R = 7.5\Omega$, $L = 6\mu H$ and $C = 40pF$, with a supply voltage of 0.5 volts. (8)

14. For the circuit shown in figure, $L1 = 4 H$, $L2 = 9H$, $K = 0.5$, $i_1 = 5 \cos(50t-30^\circ)A$, $i_2 = 2 \cos(50t-30^\circ)A$. Find

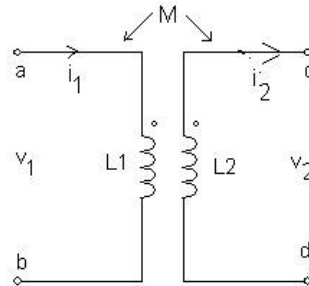(i) V_1 (ii) V_2 (iii) total energy stored in the system at $t = 0$. (8)



15 Find the h parameters for the network shown in figure-6. (8)

