

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53403

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electronics and Communication Engineering

15UEC303 - CIRCUIT THEORY

(Regulation 2015)

Duration: One hour

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

(Answer any six of the following questions)


1. The complementary set of branches of the tree is called the ____ of the graph CO1- R
(a) Co-tree (b) Twigs (c) Links (d) Chords
2. If R_1 and R_2 are connected in parallel then the current through R_1 is CO1- R
(a) $I_2 * [R_2 / (R_1 + R_2)$ (b) $I * [R_1 / (R_1 + R_2)]$ (c) $I * [R_2 / (R_1 + R_2)]$ (d) $I * [(R_1 + R_2) / R_2]$
]
3. Thevenin's equivalent circuit consists of _____ with impedance. CO2- R
(a) Voltage source in parallel (b) Voltage source in series.
(c) Current source in series (d) Current source in parallel
4. The Thevenin's equivalent circuit contains CO2- R
(a) voltage source in series with resistance
(b) voltage source in parallel with resistance
(c) current source in series with resistance
(d) current source in parallel with resistance
5. In a series RLC circuit, the current _____ the applied voltage when $X_L < X_C$ CO3- R
(a) Lag behind (b) Leads (c) In phase with (d) Not related to
6. If $X_L = 23 \Omega$ and the supply frequency is 50 Hz, then inductance L CO3- R
value is
(a) 0.053 H (b) 0.063 H (c) 0.073 H (d) 0.054 H

7. Transmission parameters are also called as _____ CO4- R
 (a) ABCD parameter (b) Y- parameters (c) Z-parameters (d) H-parameters
8. The damped frequency of oscillation β is given by CO4- R
 (a) $\omega_n * \sqrt{(1- \sigma^2)}$ (b) $\omega_n * (1- \sigma^2)$ (c) $\omega_n / (1- \sigma^2)$ (d) $\omega_n * \sigma^2$
9. A tuned amplifier uses _____ load CO5- R
 (a) Resistive (b) Capacitive (c) Inductive (d) LC tank
10. In a star connected circuit the value of power is given by CO5- R
 (a) $\sqrt{3} V_{ph} * I_{ph} * \text{Cos}\phi$ (b) $\sqrt{3} V_L * I_L * \text{Cos}\phi$
 (c) $3 V_L * I_L * \text{Cos}\phi$ (d) $\sqrt{3} V_L * I_L * \text{Sin}\phi$


PART – B (3 x 8= 24 Marks)

(Answer any three of the following questions)

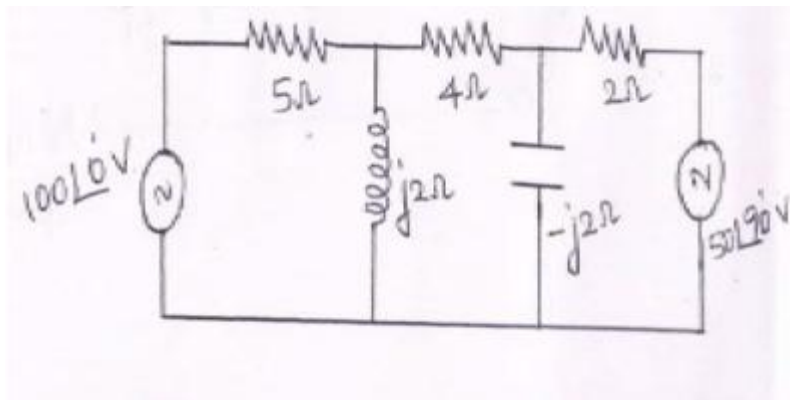11. Calculate loop currents by mesh analysis CO1- App (8)



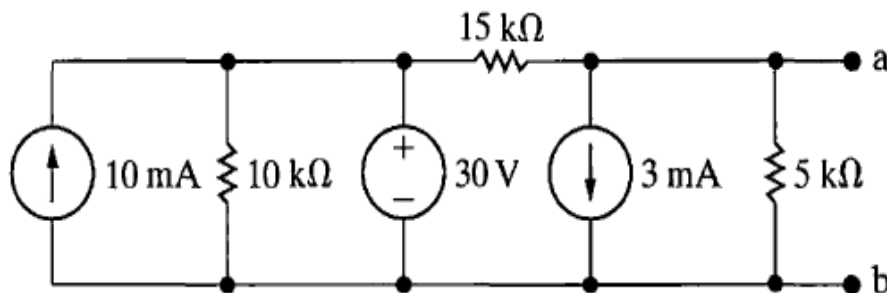12. Obtain the Norton's equivalent across the terminal ab. CO2- App (8)




13. For the series resonant circuit with $R=2 \Omega$, $X_L=X_C=10\Omega$ and $E=10V$. find I , V_R , V_L and V_C at resonance. Also, if resonant frequency is 5000Hz, determine bandwidth, Q factor, half power frequencies and power dissipated in the circuit at resonance and at the half power frequencies. Derive the expression for resonant CO3- Ana (8)

frequency.

14. Find Z parameters for the following network.

CO4- App (8)

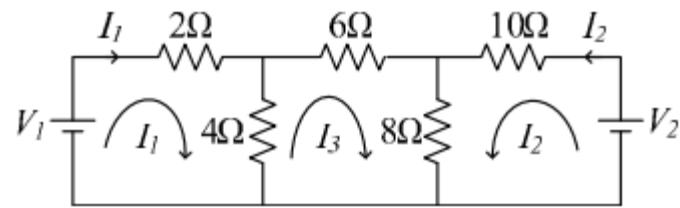

15. Derive the mutual inductance and the coupling coefficient of the transformer with necessary illustration

CO5- U (8)