

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 93405

B.E./B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electronics and Communication Engineering

19UEC305- ANALOG CIRCUITS

(Regulation 2015)


Duration: One hour

Maximum: 30 Marks

PART A - (6 x 1 = 6 Marks)

(Answer any six of the following questions)

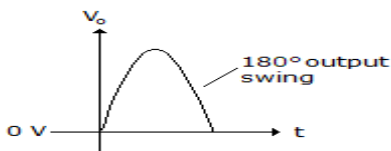1. The cut in voltage or V_{BE} of silicon diode or transistor is ---- CO1- R
(a) 0.7v (b) 0.3v (c) 0.4v (d) none of the above
2. In microphone amplifiers which configuration is used CO1- R
(a) CB (b) CE (c) CC (d) none of the above
3. In a FET amplifier , the source follower is a ----- CO2-App
(a) CS amplifier (b) CG amplifier (c) CD amplifier (d) none of the above
4. The voltage gain of an decreases at 20dB/octave above 100KHz. If the mid frequency gain is 80dB. What is the value of voltage gain at 2MHz CO2-App
(a) 60dB (b) 52dB (c) 54dB (d) 64dB
5. This is an example of the output swing for a class-----amplifier. CO4- R



- (a) A (b) AB (c) C (d) B
6. In class B amplifier, $V_{CE(\min)}=2V$ and supply voltage $V_{cc}=15V$. Find the collector circuits efficiency. CO4- U
(a) 68.06% (b) 45% (c) 68.06% (d) sine wave signals

7. When voltage feedback (negative) is applied to an amplifier, its input impedance CO5- U
 (a) Is decreased (b) Is increased (c) Remains the same (d) None of the above
8. Negative feedback is employed in CO5- U
 (a) Oscillators (b) Rectifiers (c) Amplifiers (d) None of the above
9. The feedback signal in a(n)-----oscillator is derived from an inductive voltage divider in the LC circuit CO6- R
 (a) Hartley (b) Armstrong (c) colpitts (d) wien bridge
10. For a phase shift oscillator, the gain of the amplifier stage must be greater than----- CO6- R
 (a) 19 (b) 29 (c) 30 (d) 1

PART – B (3 x 8= 24 Marks)

(Answer any three of the following questions)

11. Consider the self bias circuit where $V_{cc}=15V, R_c=3K\Omega, R_2=10K\Omega, R_1=90K\Omega,$ CO1- Ana (8)
 $h_{fe}=55(\beta), V_{BE}=0.6V.$ The transistor operates in active region. Determine (i) operating point (ii) stability factor (iii) D.C load line Analyze and suggest , whether the circuit is suitable to get faithful amplification
12. Design an amplifier for the following specifications: Mid band gain(A_v) CO3- Ana (8)
 should be 20 & base voltage should be 2v . Given: $h_{ie}=1100 \Omega ,$
 $h_{re}=10 \times 10^{-4}, h_{fe}=100 ,$ and $h_{oe}=4 \times 10^{-4} \text{ mho}$
13. Design and explain the power amplifier circuit using power transistor to use as CO4-Ana (8)
 final stage in receiver for AF application.
14. Design an feedback amplifiers to use as local negative feedback to increase CO5- Ana (8)
 input resistance, linearize the transfer curve, and stabilize bias. Assume necessary data
15. Design a LC oscillator for the frequency of 10KHz in which tank circuit has CO5- Ana (8)
 two inductive reactance's and one capacitive reactance and derive the expression for frequency of oscillation and condition for oscillation.