

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 93302

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electrical and Electronics Engineering

19UEE302 – ELECTRICAL CIRCUIT ANALYSIS

(Regulation 2019)


Duration: One hour

Maximum: 30Marks

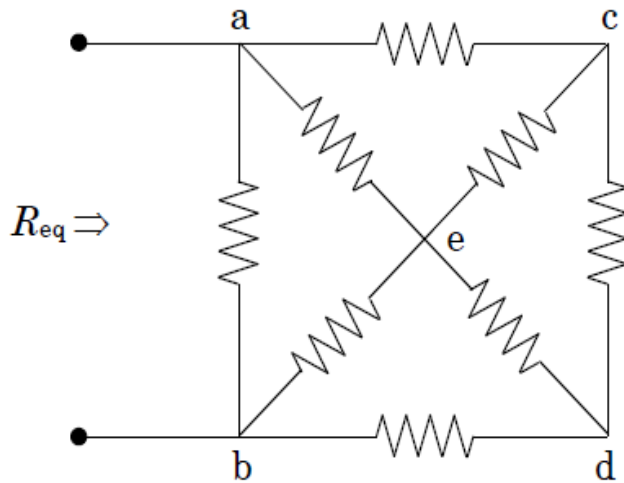
PART A - (6 x 1 = 6 Marks)

(Answer any six of the following questions)


- Which of the following combinations of components represents an impedance of $(110 + j 314) \Omega$ at a frequency of 100 Hz? CO1- App
 - A resistor of 314Ω in series with an inductor of 5 mH.
 - A resistor of 110Ω in series with a capacitor of 5 μF .
 - A resistor of 110Ω in series with a capacitor of 5 μF .
 - An inductor of 50 mH in series with a capacitor of 5 μF
- In a series parallel circuit with 6 resistances if there are three in one parallel bank, these three resistances must have CO1- App
 - The same current as in the voltage source
 - The same current
 - The same IR drop
 - An IR drop equal to the applied voltage
- An amplifier has an output impedance Z_0 of $(70 + j35) \Omega$. What value of load impedance will permit maximum power transfer? CO2-R
 - $(70 + j35)\Omega$
 - $(-70 + j35)\Omega$
 - $(70 - j35)\Omega$
 - $(-70 - j35)\Omega$
- A 12Ω resistor, a $40 \mu\text{F}$ capacitor, and an 8 mH coil are in series across an ac source. The resonant frequency is CO3- App
 - 28.1 Hz
 - 281 Hz
 - 2810 Hz
 - 10 KHz
- If two winding having self-inductances L_1 and L_2 , and a mutual inductance m are connected in series will opposite, then the total inductance of series combination will be CO3- U
 - $L_1 + L_2 - 2M$
 - $L_1 + L_2 + 2M$
 - $L_1 - L_2 + 2M$
 - $L_1 + L_2 - M$



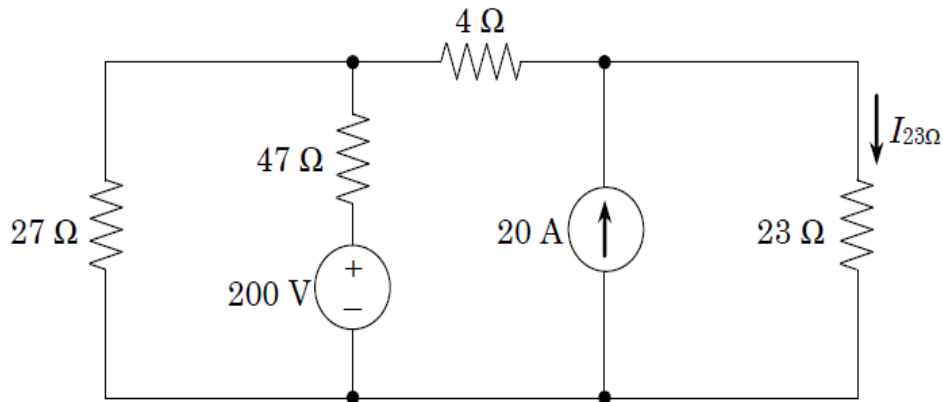
12. Compute the current in the $23\ \Omega$ resistor of the figure shown below by CO2- App (8) applying superposition principle.



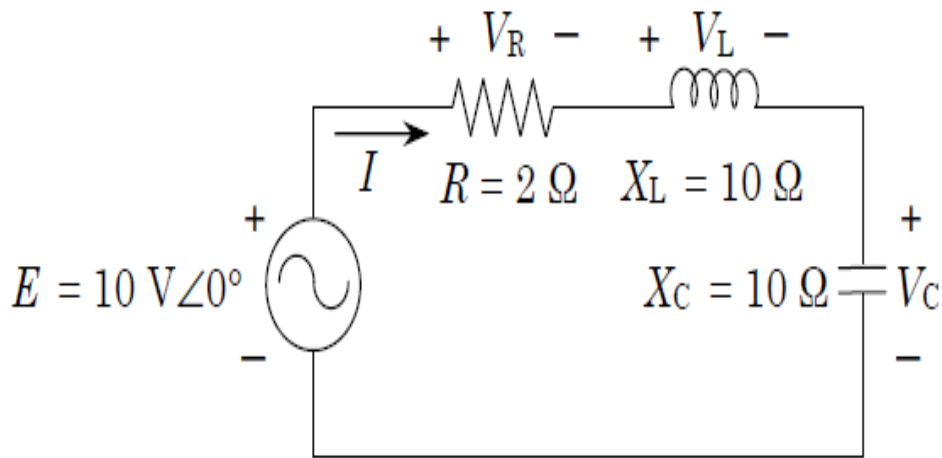13. For the series resonant of Fig, Find I ; V_R ; V_L and V_C at resonance. Also, CO3- App (8) if resonant frequency is 5000 Hz, determine bandwidth, Q factor, half power frequencies, and power dissipated in the circuit at resonance and at the half power frequencies. Derive the expression for resonant frequency.



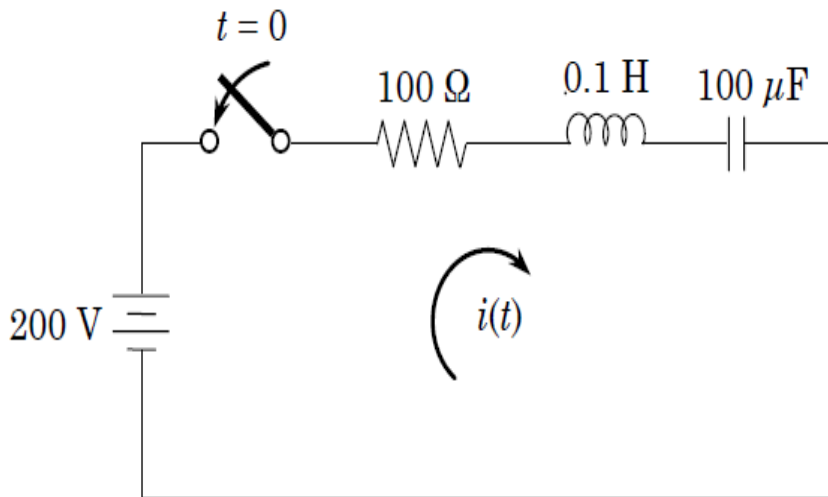14. A series RLC circuit with $R = 100 \Omega$, $L = 0.1 \text{ H}$, and $C = 100 \mu\text{F}$ has a DC voltage of 200 V applied to it at $t=0$ through a switch. Find the expression for the transient current. Assume initially relaxed circuit condition. CO4- App (8)



15. Three equal impedances, each of $(8 + j10) \Omega$ are connected in star. This is further connected to a 440 V , 50 Hz , three phase supply. Calculate the active and reactive power and line and phase currents. CO5- E (8)