

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 93304**

B.E. / B.Tech. DEGREE EXAMINATION, DEC 2020

Third Semester

Electrical and Electronics Engineering

19UEE304 – ANALOG ELECTRONICS

(Regulation 2019)

Duration: One hour

Maximum: 30Marks

PART A - (6 x 1 = 6 Marks)

**(Answer any six of the following questions)**

1. The number of pn junctions in a BJT is/are CO1- R  
(a) 1 (b) 2 (c) 3 (d) 4
2. Which of the following is true for the saturation region? CO1- R  
(a)  $V_{DG} \leq |V_{tp}|$  (b)  $V_{SD} \leq |V_{OV}|$  (c)  $V_{DG} < |V_{tp}|$  (d)  $V_{SD} < |V_{OV}|$
3. In CE configuration, if the voltage drop across  $5k\Omega$  resistor connected in the collector circuit is  $5V$ . Find the value of  $I_B$  when  $\beta=50$ . CO2-R  
(a)  $0.01mA$  (b)  $0.25mA$  (c)  $0.03mA$  (d)  $0.02mA$
4. The correct expression relating the emitter current  $I_e$  to the collector current  $I_c$  is CO2-R  
(a)  $I_e = \alpha I_c$  (b)  $I_c = \alpha I_e$  (c)  $I_e = \beta I_c$  (d)  $I_c = \beta I_e$
5. The expression for the differentiator time constant is CO4- U  
(a)  $CR$  (b)  $1/CR$  (c)  $R/C$  (d)  $C/R$
6. What are the units of slew rate? CO4- R  
(a) Second/Volt (b) Volt/second (c) It is a ratio, no units (d) Ohm/second
7. Calculate the frequency of oscillation for RC phase shift oscillator having the CO4- U  
value of R and C as  $35\Omega$  and  $3.7\mu F$  respectively.  
(a)  $1230\text{ Hz}$  (b)  $204\text{ Hz}$  (c)  $502\text{ Hz}$  (d)  $673\text{ Hz}$
8. What is Barkhausen criterion for oscillation? CO4- R  
(a)  $A\beta > 1$  (b)  $A\beta < 1$  (c)  $A\beta = 1$  (d)  $A\beta \neq 1$
9. A monostable multivibrator has  $R = 120k\Omega$  and the time delay  $T = 1000ms$ , CO5- U  
calculate the value of C?  
(a)  $0.9\mu F$  (b)  $1.32\mu F$  (c)  $7.5\mu F$  (d)  $2.49\mu F$

10. Free running frequency of Astable multivibrator?

CO5- R

(a)  $f=1.45/(R_A+2R_B)C$

(b)  $f=1.45(R_A+2R_B)C$

(c)  $f=1.45C/(R_A+2R_B)$

(d)  $f=1.45 R_A/( R_A+R_B)$

PART – B (3 x 8= 24 Marks)

(Answer any three of the following questions)


11. Explain drain and transfer characteristic of JFET.

CO1- U (8)

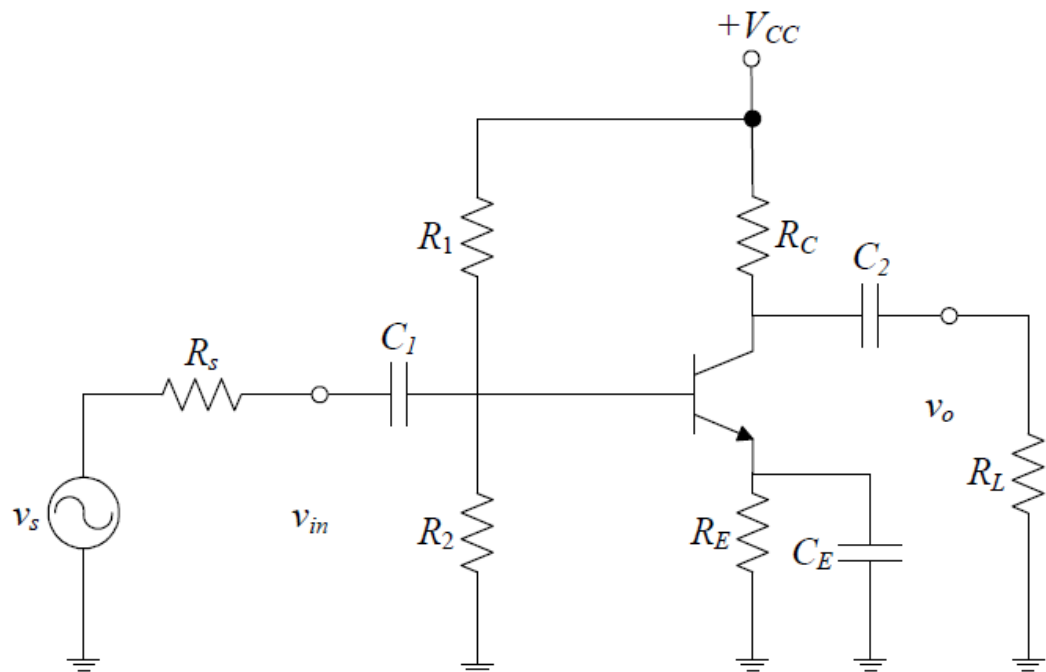12. Consider the common-emitter BJT amplifier circuit shown in Figure.


CO2- App (8)

Assume  $V_{CC} = 15 \text{ V}$ ,  $\beta = 150$ ,  $V_{BE} = 0.7 \text{ V}$ ,  $R_E = 2.7 \text{ k}\Omega$ ,  $R_C = 4.7 \text{ k}\Omega$ ,  $R_1 = 47 \text{ k}\Omega$ ,  $R_2 = 10 \text{ k}\Omega$ ,  $R_L = 47 \text{ k}\Omega$ ,  $R_s = 100 \Omega$ . Determine the Q-point.



13. A non-inverting summer such as the one shown in figure below is used to combine three signals.  $V_1 = 1 \text{ V DC}$ ,  $V_2 = -0.2 \text{ V DC}$ , and  $V_3$  is a  $2 \text{ V}$  peak  $100 \text{ Hz}$  sine wave. Determine the output voltage if  $R_1=R_2=R_3=R_f = 20 \text{ k}\Omega$  and  $R_i = 5 \text{ k}\Omega$ .

CO3- App (8)

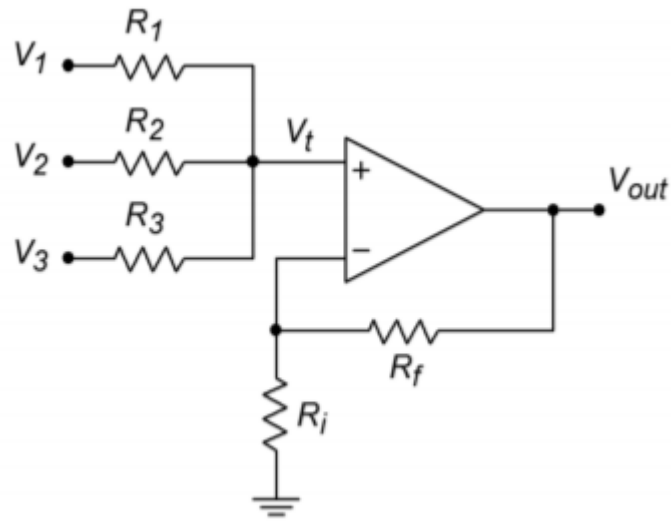

14. Design a square wave oscillator for  $f=1\text{kHz}$ . The op-amp is 741 with supply  $\pm 15\text{V}$ . CO4- App (8)
15. Design a symmetrical square waveform generator of  $10\text{kHz}$  using 555 timer. CO5- C (8)