

6. Which amplifiers have the highest overall efficiency?
- (a) Class A (b) class B or AB
(c) class C (d) class D
7. In a feedback amplifier, if the feedback fraction β is positive, then the feedback
- (a) Degenerative (b) regenerative
(c) negative (d) reverse
8. In the colpitts oscillator, the elements X_1 and X_2 are _____ and X_3 is a(n)
- (a) Inductors, capacitor (b) capacitors, inductor
(c) Capacitors, resistor (d) inductors, resistor
9. An op-amp clamper circuit is also referred as
- (a) DC cutter (b) DC inserter (c) DC lifter (d) DC leveller
10. The _____ is(are) an adjustable voltage regulator.
- (a) Series 7800 ICs (b) series 7900 ICs
(c) LM317 (d) none of these

PART - B (5 x 2 = 10 Marks)

11. Show the VI characteristics of a tunnel diode.
12. Draw the transistor equivalent circuit of SCR.
13. What is an R-C coupled amplifier?
14. What is Barkhausen criterion?
15. List the important characteristics of a voltage regulator.

PART - C (5 x 16 = 80 Marks)

16. (a) (i) Explain the working of transistor as an amplifier. (10)
(ii) Derive the stability factor for a base bias circuit. (6)

Or

- (b) (i) Describe the operation of the p-n junction diode with V-I characteristics. (10)

- (ii) Explain briefly the Schottky diode. (6)
17. (a) (i) Explain the construction and working of UJT. (8)
- (ii) Draw the drain and transfer characteristics of a JFET and Explain. (8)

Or

- (b) Explain the structure, working and characteristics of N channel enhancement type MOSFET. (16)
18. (a) Draw the h-parameter equivalent circuit for a typical common emitter amplifier and derive the expression for A_i , R_i , A_v and R_o . (16)

Or

- (b) Prove that the maximum efficiency of class B amplifier is 78.5% and that of class A type is 50%. (16)
19. (a) Explain the working of Wein bridge oscillator with neat diagram. Also derive the expression for oscillator frequency. (16)

Or

- (b) Explain RC phase oscillator and derive its frequency of oscillation. (16)
20. (a) Explain the working and waveforms of monostable multivibrator. (16)

Or

- (b) Explain the working of a Schmitt trigger with a neat sketch. (16)
-

