

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 41536**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2016

Third Semester

Electronics and Instrumentation Engineering

14UEI306 – DIGITAL ELECTRONICS

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 1 = 10 Marks)

- Find the hexadecimal equivalent of the octal number 153.4.  
(a) B6.8                      (b) 68.8                      (c) 6B.8                      (d) 6B.6
- \_\_\_\_\_ gates are called as the universal gates  
(a) AND and OR                      (b) NAND and NOR  
(c) NOT and NOT                      (d) NAND and OR
- A device that converts from octal to binary number is called  
(a) Decoder                      (b) Multiplexer                      (c) Encoder                      (d) De-multiplexer
- A comparator is a special combinational circuit designed primarily to compare the relative magnitude of \_\_\_\_\_ numbers .  
(a) two decimal                      (b) three decimal                      (c) two binary                      (d) three binary
- \_\_\_\_\_ is used for the purpose of detecting errors during transmission of binary information  
(a) Message bit                      (b) Carry bit                      (c) Parity bit                      (d) Selection bit

6. D flip-flop during the occurrence of clock pulse if \_\_\_\_\_, the output \_\_\_\_\_ and if \_\_\_\_\_, the output is reset.
- (a)  $D = 0, Q = 0$ , D is set (b)  $D = 1, Q = 1$ ,  $D = 0$   
(c)  $D = 1, Q$  is set,  $D = 0$  (d) None of these
7. State assignments are used to avoid .....
- (a) Static – 0 hazard (b) Races  
(c) Static – 1 hazard (d) Dynamic hazards
8. \_\_\_\_\_ consists of a set of fixed AND gates connected to a decoder and a programmable OR array.
- (a) EPROM (b) EEPROM (c) PROM (d) EAPROM
9. Flash memories are similar to
- (a) ROM (b) PROM (c) RAM (d) EEPROM
10. \_\_\_\_\_ is the minimum time required to maintain a constant voltage levels at the excitation inputs of the flip-flop device.
- (a) Rise time (b) Fall time  
(c) Setup time (d) None of these

PART - B (5 x 2 = 10 Marks)

11. Obtain the canonical SOP form of the function  $Y=AB+ACD$ .
12. Define Multiplexer and draw its block diagram.
13. List out the applications of Flip Flops.
14. Define Glitch.
15. What is meant by PLA?

PART - C (5 x 16 = 80 Marks)

16. (a) Use Quine McClusky method to obtain the minimal sum for the following function.  
 $F(X_1 X_2 X_3 X_4) = \sum (0, 1, 3, 6, 7, 14, 15)$ . (16)
- Or
- (b) (i) Give a brief note on Weighted codes. (8)
- (ii) If  $\bar{A}B + C\bar{D} = 0$  then. Prove that  $AB + \bar{C}(\bar{A} + \bar{D}) = AB + BD + \bar{B}\bar{D} + \bar{A}\bar{C}D$ . (8)

17. (a) (i) Compare the characteristics of different Logic families. (8)  
(ii) Design a 4-bit Parallel Adder/Subtractor using logic gates. (8)

Or

- (b) (i) Discuss the 4-bit Magnitude comparator with its logic diagram. (8)  
(ii) Write the truth table of a three - to - eight lines decoder and construct the circuit for 3 - to - 8 lines decoder. (8)

18. (a) Explain the operation universal shift register with logic diagram. (16)

Or

- (b) Define Counter. Design a Synchronous decade counter using JK flip flop. (16)

19. (a) What do meant by hazards? Describe hazards in combinational and sequential circuits with suitable examples. (16)

Or

- (b) Write short notes on: (i) Races (ii) Hazards. (16)

20. (a) What is RAM. Explain in detail about the types of RAM with necessary logic diagrams. (16)

Or

- (b) (i) With a neat sketch, explain the block diagram of PLA. (8)  
(ii) Draw the logic diagram of a  $4 \times 4$  RAM. (8)

