

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 31432

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2016

Third Semester

Electronics and Communication Engineering

01UEC302 - DIGITAL ELECTRONICS AND DESIGN

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. State De Morgan's theorem.
2. Determine canonical SOP form of the function $Y=AB+ACD$.
3. Write down design procedure for combinational circuits.
4. Why multiplexer is called as data selector.
5. What do you mean by triggering of flip flop?
6. What is a shift register? And its types.?
7. What is RAM?
8. Draw the basic configuration of PLA.
9. Distinguish between synchronous sequential circuit and asynchronous sequential circuit.
10. Define hazards.

PART - B (5 x 16 = 80 Marks)

11. (a) Minimize the given switching function using Quine-Mcclusky method

$$f(x_1, x_2, x_3, x_4) = \Sigma(0, 5, 7, 8, 9, 10, 11, 14, 15).$$

(16)

Or

- (b) Simplify the given Boolean function into (i) Sum of products form (ii) Product of sum form and implement it using basic gates. $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$. (16)

12. (a) Design a 4-bit parallel adder/subtractor and draw the logic diagram. (16)

Or

- (b) Design a 4-bit magnitude comparator. (16)

13. (a) Discuss in detail about JK flip flop with its truth table, state diagram and characteristics equation. (16)

Or

- (b) Design a MOD-10 synchronous counter using J-K flip flops. Write the excitation table and state table. (16)

14. (a) With neat diagram explain the RAM organization. (16)

Or

- (b) Implement the given function using PAL.

$$A = \text{Em}(0, 2, 6, 7, 8, 9, 12, 13),$$

$$B = \text{Em}(0, 2, 6, 7, 8, 9, 12, 13, 14),$$

$$C = \text{Em}(1, 3, 4, 6, 10, 12, 13),$$

$$D = \text{Em}(1, 3, 4, 6, 9, 12, 14). \quad (16)$$

15. (a) (i) Explain the design procedure involved in synchronous sequential logic circuits. (8)

- (ii) Write short notes on (a) State table, (b) State diagram and (c) State equation. (8)

Or

- (b) Define races and explain its types and hazards that occur in asynchronous circuits. Discuss a method used for race free assignment with example. (16)