

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 31327**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2016

Second Semester

Electrical and Electronics Engineering

01UEE207- ELECTRIC CIRCUITS

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 2 = 20 Marks)

1. Draw the VI characteristics of ideal and practical voltage sources.
2. A fluorescent tube choke is connected across 230V, 50Hz AC supply. If the resistance and reactance of the choke are  $100\Omega$ ,  $1H$  respectively, determine the current through the choke.
3. Write the resistance of each arm of star connected load in terms of delta connected load.
4. Two resistors  $10\Omega$  and  $20\Omega$  are connected in parallel. If the total current is 3A, what will be the current through each resistor?
5. Determine the resonance frequency of a RLC series circuit with  $R = 5\Omega$ ,  $L = 0.02 H$  and  $C = 5\mu f$ .
6. An R,L,C series circuit is supplied with 230V AC of variable frequency. If  $R=10\Omega$ ,  $L=10mH$  and  $C=10\mu F$ , determine the maximum current through the circuit.

7. A RL series circuit with  $R=10\ \Omega$  is excited by a dc voltage source of 30 V by closing the switch at  $t = 0$ . Determine the current in the circuit at  $t = 2\tau$ .
8. Give the condition for Critical Damping of an RLC series circuit.
9. A star connected load has impedance of  $(6 + j8)\ \Omega$  in each phase. Determine the line current when it is connected to 400 V, 3 $\phi$ , 50 Hz supply.
10. In three phase power measurement using two wattmeter, what is the power factor if one wattmeter reads zero?

PART - B (5 x 16 = 80 Marks)

11. (a) Calculate (i) the equivalent resistance across the terminals of the supply (ii) total current supplied by the source and (iii) power delivered to 16  $\Omega$  resistors in the circuit shown in figure 1.

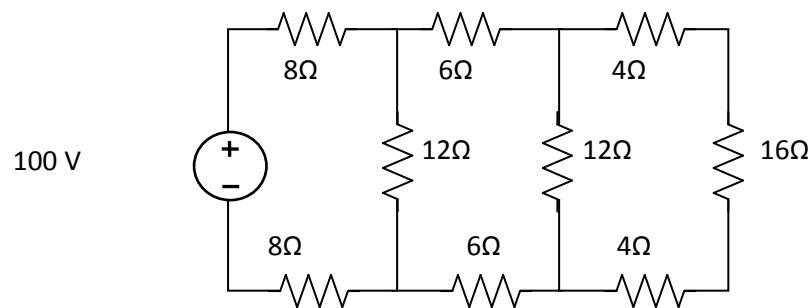


Figure 1

(16)

Or

- (b) Using nodal analysis, calculate the current through the 5  $\Omega$  resistor in the circuit shown in figure 2.

(16)

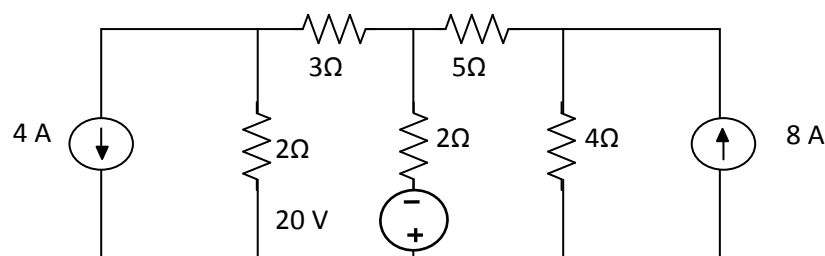


Figure 2

12. (a) (i) In the circuit shown in figure 3, obtain the current in each resistor using Network reduction method. (8)

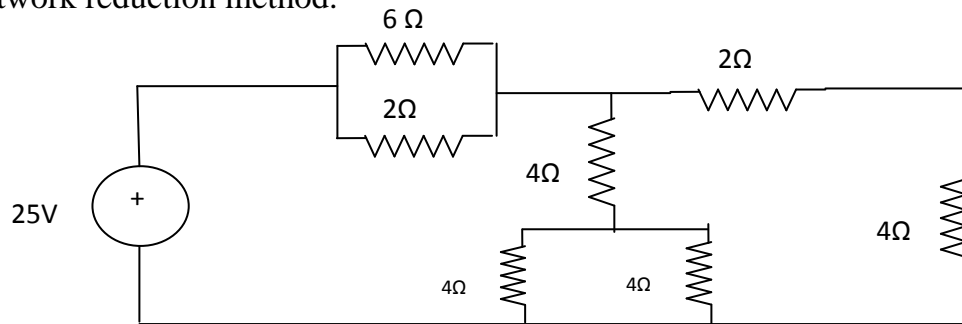


Figure 3

- (ii) Using Superposition theorem, find current  $I$  in figure 4. (8)

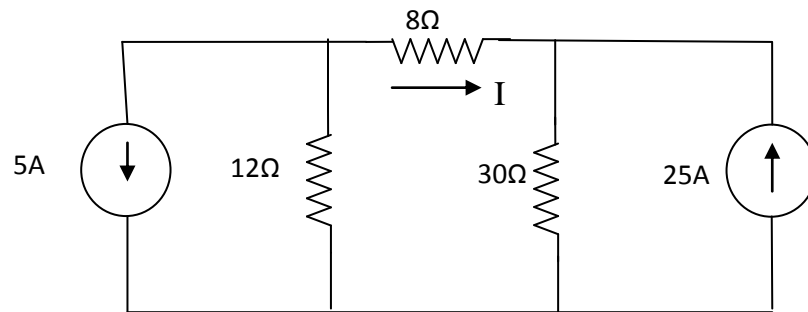


Figure. 4

Or

- (b) (i) Explain how three resistances connected in delta can be converted into equivalent star. Derive the relationship. (8)
- (ii) An AC power source  $100V$ ,  $50Hz$  has an internal impedance of  $2 + j5 \Omega$ . What will be the maximum power that can be delivered by this source to load? (8)
13. (a) A series RLC circuit consists of  $R = 16 \Omega$ ,  $L = 5 mH$  and  $C = 2 \mu F$ . Calculate the quality factor, bandwidth and half power frequencies. (16)

Or

- (b) Two coils connected in series have an equivalent inductance of  $0.8 H$  when connected in aiding and an equivalent inductance of  $0.4 H$  when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking  $k = 0.55$ . (16)

14. (a) A RL series circuit is excited by a sinusoidal source  $e(t) = 10 \sin 100t$  volts, by closing the switch at  $t = 0$ . Take  $R = 10 \Omega$  and  $L = 0.1 H$ . Determine the current  $i(t)$  flowing through the RL circuit. (16)

Or

- (b) (i) Derive the expression for transient current and voltage drop across resistance of an RL series circuit supplied by a constant voltage source at  $t = 0$ . (8)
- (ii) A series RL circuit has a constant voltage  $V$  applied at  $t = 0$ . At what time does voltage drop across R is equal to voltage drop across L? (8)
15. (a) A three phase balanced supply of 400V (line to line) 50Hz is given to a three phase delta connected load with impedance  $20 \angle 45^\circ \Omega$ . Obtain the line currents, power and power factor. Also draw the phasor diagram. (16)

Or

- (b) A 500 V, three phase motor has an output of 3.73 kW and operates at a power factor of 0.85, with an efficiency of 90%. Calculate the reading of each of the two watt meter connected to measure the input. (16)
-