

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 51336

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2016

Third Semester

Electrical and Electronics Engineering

15UEE306 - DIGITAL LOGIC CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- In standard TTL the 'totem pole' stage refers to the
 - multi-emitter input stage
 - phase splitter
 - output buffer
 - open collector output stage
- What is the gray code for 1000?
 - 1010
 - 1000
 - 1011
 - 1100
- The digital multiplexer is basically a combination logic circuit to perform the operation of
 - AND-AND
 - OR-OR
 - AND-OR
 - OR-AND
- A combinational circuit that performs the addition of two bits is called
 - Full adder
 - Full subtractor
 - Half subtractor
 - Half adder
- The output Q_n of a J-K flip-flop is zero. It change to one when a clock pulse is applied. The input J_n and K_n are respectively
 - 1 and X
 - 0 and X
 - X and 0
 - X and 1

6. A flip-flop output transition serves as clock to next flip-flop is called
 (a) ripple counter (b) parallel counter
 (c) shift register (d) none of the above
7. An unwanted switching transients occurs at the output of a circuit are
 (a) races (b) cycles (c) hazards (d) harmonics
8. A PLA can be used
 (a) as a microprocessor (b) as a dynamic memory
 (c) to realize a sequential logic (d) to realize a combinational logic
9. Which one is unary operator in VHDL?
 (a) +(sign) (b) not (c) mod (d) rol
10. Which is used to verify the design function?
 (a) packages (b) libraries (c) test bench (d) subprogram

PART - B (5 x 2 = 10 Marks)

11. Define fan-in and fan-out.
12. Give the application of demultiplexer.
13. Distinguish between synchronous sequential circuits and asynchronous sequential circuit.
14. Define race in asynchronous sequential circuit.
15. What is test bench in VHDL.

PART - C (5 x 16 = 80 Marks)

16. (a) (i) Write a brief notes about error detection and correction codes. (8)
 (ii) Explain the operation and characteristics of DTL circuit. (8)

Or

- (b) (i) Explain the operation of TTL with neat circuit diagram for 2 input NAND gate with Tottem pole output. (12)
 (ii) Write short notes on CMOS NOR gate. (4)

17. (a) Reduce the following using K-map

(i) $F(w, x, y, z) = \sum m(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$ (4)

(ii) $g(w, x, y, z) = \sum m(1, 3, 4, 6, 11) + \sum d(0, 8, 10, 12, 13)$ (4)

(iii) $Y(A, B, C, D) = \prod M(0, 2, 8, 9, 12, 13, 15)$ (4)

(iv) $Y(A, B, C, D) = \prod M(1, 2, 3, 8, 9, 10, 11, 14) + d(7, 15)$. (4)

Or

(b) (i) Implement Excess 3 to BCD code converter circuit. (8)

(ii) Implement the given boolean function using 4:1 Multiplexer,


$F(A, B, C, D) = \sum m(0, 1, 2, 4, 6, 9, 12, 14)$. (8)

18. (a) (i) Design a 4-bit synchronous up-counter using JK flip flop. (8)

(ii) Using D-flip flop, design a synchronous counter which counts in the sequence 000, 001, 010, 011, 100, 101, 110, 111, 000. (8)

Or

 (b) Design a sequential circuit with JK flip-flop. (16)



19. (a) Discuss the different types of hazards that occurs in asynchronous sequential circuits and combinational circuits. (16)

Or

(b) Explain with a suitable example the procedure for analyzing synchronous sequential circuit. (16)

20. (a) (i) Write a VHDL code for a full adder. (8)
- (ii) Explain the operation of RTL data path design with suitable diagram. (8)

Or

- (b) Write a VHDL code for SR flip flop and D flip flop. (16)
-