

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 54B01**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Fourth Semester

Biomedical Engineering

15UBM401-ANALOG AND DIGITAL INTEGRATED CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. If  $A_{DM} = 3500$  and  $A_{CM} = 0.35$ , the CMRR is ..... CO1 -R  
(a) 1 (b) 0 (c)  $\infty$  (d) 1.5
2. Which one of the following features suited for Instrumentation Amplifier. CO1 -R  
(a) High CMRR (b) High DC offset (c) Low Gain Accuracy (d) High Output
3. A multivibrator is an electronic circuit used to implement CO2 -R  
(a) Oscillator (b) Timer  
(c) Flip-flop (d) All of the Mentioned
4. The \_\_\_\_\_ Filter controls the capture range and lock range of PLL CO2 -R  
(a) Low Pass (b) High Pass (c) Band Pass (d) Band Reject
5. What is the formula for finding the time period in Monostable operation? CO3- R  
(a)  $T = 1.1 RC$  (b)  $T = 1.5 RC$  (c)  $T = 2.1 RC$  (d)  $T = 2.5 RC$
6. The operating voltage range for NE/SE 565 PLL. CO3 -R  
(a)  $\pm 6V$  to  $\pm 12V$  (b)  $\pm 12V$  to  $\pm 18V$  (c)  $\pm 4V$  to  $\pm 12V$  (d)  $\pm 7V$  to  $\pm 12V$
7. The output of an AND gate with three inputs, A, B, and C, is HIGH when \_\_\_\_\_. CO4 -U  
(a)  $A = 1, B = 1, C = 0$  (b)  $A = 0, B = 0, C = 0$   
(c)  $A = 1, B = 1, C = 1$  (d)  $A = 1, B = 0, C = 1$

8. Applying DeMorgan's theorem to the expression  $\overline{ABC}$ , we get \_\_\_\_\_ CO4 -U
- (a)  $\overline{A} + \overline{B} + \overline{C}$  (b)  $\overline{A + B + C}$  (c)  $A + \overline{B} + \overline{C}$  (d)  $A(B + C)$
9. How many flip-flops are in the 7475 IC? CO5 -R
- (a) 1 (b) 2 (c) 4 (d) 8
10. The flip-flop is only activated by CO5- R
- (a) Positive edge trigger (b) Negative edge trigger
- (c) Either positive or Negative edge trigger (d) None of the Mentioned

PART – B (5 x 2= 10Marks)

11. List out the characteristics of OP-Amp Circuits. CO1- R
12. List the types of comparators CO2 -R
13. Calculate output frequency  $f_0$ , Lock range  $\Delta f_C$  of a 565 PLL if  $R_T = 10k\Omega$ ,  $C_T = 0.01 \mu F$  and  $C = 10 \mu F$ . CO3 -U
14. What is priority Encoder? CO4- U
15. Classify the different types of PLD. CO5 -R

PART – C (5 x 16= 80Marks)

16. (a) Describe the AC Characteristics of the Operational Amplifier circuits with suitable example. CO1- U (16)
- Or
- (b) Describe the DC Characteristics of the Operational Amplifier circuits. CO1- U (16)
17. (a) How the square wave is generated when it switches from one state to other state and explain it. CO2 -U (16)
- Or
- (b) Draw and explain the types of D/A Converters with suitable waveforms. CO2 -U (16)
18. (a) Describe the operation of Monostable Multivibrator circuit with suitable waveforms. CO3 -U (16)
- Or
- (b) Draw the block diagram of VCO. Explain the working principle of the VCO with suitable waveforms. CO3- U (16)

19. (a) Draw the logic diagram of the full Adder and explain its operation. CO4- U (16)

Or

(b) Simplify the following using tabulation method CO4 -App (16)

$$Y(w,x,y,z)=\Sigma m(1,2,3,5,9,12,14,15)+\Sigma d(4,8,11)$$

20. (a) What is RAM? Explain the different types of RAM in detail. CO5- U (16)

Or

(b) Sketch the transition table and state stable for an asynchronous sequential circuit described by the following Boolean expressions CO5 -U (16)

$$Y1=xy1+x'y2', Y2=xy1'+x'y2$$

