

B

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53B05

B.E./B.Tech. DEGREE EXAMINATION, NOV 2018

Third Semester

Biomedical Engineering

15UBM305- SEMICONDUCTOR DEVICES AND CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. Diode is used as _____ CO1-R
(a) Current source (b) Voltage source (c) Photo diode (d) Rectifier
2. If $I_B = 1$ mA, $\beta = 50$ for a transistor, I_E is _____ CO1-App
(a) 51 mA (b) 50 mA (c) 101 mA (d) 49 mA
3. JFET acts as a current source when it is operating _____ CO2-U
(a) Along the horizontal part of drain curve (b) At $V_{GS} = 0$
(c) Along linear part of drain curve (d) At $V_{GS} < 0$
4. g_m of MOSFET is controlled by _____ CO2- R
(a) Drain-source voltage (b) Gate-source voltage (c) Drain current (d) Gate current
5. The approximate current gain of CE transistor amplifier is _____. CO3- R
(a) h_{ie} (b) $-h_{ie}$ (c) $-h_{fe}$ (d) h_{fe}
6. Hybrid equivalent circuit of a transistor amplifier is valid at _____ frequencies. CO3- U
(a) Low (b) High (c) Very low (d) Very high
7. Oscillator is similar to _____ CO4- R
(a) Rectifier (b) Amplifier (c) D.C source (d) A.C source

8. The phase shift required by RC phase network in a transistor oscillator is _____ CO4- R
 (a) 90° (b) 180° (c) 360° (d) 0°
9. Bistable multivibrator is _____ in any state. CO5- R
 (a) Stable (b) Unstable (c) Saturated (d) Independent
10. Output of an integrator producing waveforms of unequal rise and fall time are called _____ CO5- U
 (a) Triangular waveform (b) Sawtooth waveform
 (c) Pulsating waveform (d) Spiked waveform

PART – B (5 x 3= 15Marks) (5 Out of 7)

11. Define Peak Inverse Voltage of diode. CO1- R
12. BJT as a current controlled device – Justify CO1- E
13. JFET as a Variable Voltage Resistor – Justify CO2- E
14. Compare the operations of Class A and Class B amplifiers. CO3- Ana
15. Point out the advantages of negative feedback. CO4- Ana
16. State and explain Barkhausen criterion for oscillation. CO4- U
17. Differentiate between Astable and Monostable multivibrators. CO5- Ana

PART – C (5 x 15= 75 Marks)

18. (a) (i) Illustrate the principle of operation of PN junction diode. CO1- U (8)
 (ii) Derive an expression for transition and diffusion capacitance of PN junction diode. CO1- U (7)
- Or
- (b) Compare the operation of voltage divider bias circuits, base bias circuits and Emitter bias circuits. CO1- Ana (15)
19. (a) Summarize the working of JFET and draw it's drain and transfer characteristics. CO2-U (15)
- Or
- (b) Explain the construction, working of n channel enhancement MOSFET and also draw their characteristics. CO2-U (15)

20. (a) Determine the h-parameters from transistor characteristics. CO3- App (15)
Or
(b) Analyze of single stage transistor amplifier using parameters voltage gain, current gain, input impedance and output admittance. CO3- Ana (15)
21. (a) Interpret the principle of operation and derive the expression for frequency of oscillation for RC phase shift Oscillator. CO4-U (15)
Or
(b) Draw the circuit of Hartley oscillator and explain its working. Also derive the expressions for frequency of oscillation for starting of oscillation. CO4-U (15)
22. (a) With neat sketch, explain the operation and characteristics of Astable multivibrator. CO5-U (15)
Or
(b) Illustrate the construction, equivalent circuit and operation of UJT and also explain the characteristics of UJT. CO5-U (15)

