

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 59501

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Elective

Electronics and Instrumentation Engineering

15UEI901– VLSI SYSTEM DESIGN

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Which technology has photo-electronic properties?. CO1- R
(a) GaAs (b) BiCMOS (c) CMOS (d) nMOS
- The photoresist layer is exposed to CO1- R
(a) Visible Light (b) Infra Red Light (c) Ultraviolet Light (d) LED
- In the design rules the implant layer has CO2- R
(a) $2\lambda \times 2\lambda$ (b) $4\lambda \times 4\lambda$ (c) $6\lambda \times 6\lambda$ (d) $8\lambda \times 8\lambda$
- The transistors used in BiCMOS are: CO2- R
(a) BJT (b) MOSFET (c) Both BJT and MOSFETs (d) JFET
- Identify the circuit constructed with pair of inverters ganged together to perform function CO3- R
(a) Symmetric (b) Non symmetric (c) SFPL (d) CVPL
- Multipliers are built using CO3- R
(a) Binary Adders (b) Binary Subtractors (c) Dividers (d) Multiplexers
- PLA contains CO4- R
(a) AND and OR arrays (b) NAND and OR arrays
(c) NOT and AND arrays (d) NOR and OR arrays

8. Which type of device FPGA are? CO4- R
 (a) SLD (b) SRAM (c) EPROM (d) PLD
9. The members function of VHDL modules declared between CO5- R
 (a) BEGIN – END (b) { - }
 (c) { - } (d) (-)
10. Which clause is used to declare the packages? CO5- R
 (a) Use (b) Entity (c) Architecture (d) Components

PART – B (5 x 2= 10Marks)

11. What is the difference between enhancement and depletion mode MOS device CO1- U
12. What is transmission gate? CO2- R
13. What is bubble pushing? CO3- R
14. What are pre diffused array? CO4 -R
15. Write the difference between Exit and Wait statement. CO5- U

PART – C (5 x 16= 80Marks)

16. (a) Discuss in detail about the modes of operation of MOS transistor with necessary equations. CO1- U (16)
 Or
 (b) Explain the different steps involved in the fabrication of NMOS with a neat diagram. CO1- U (16)
17. (a) Discuss the mathematical equation that can be used to mode the drain current diffusion capacitance of MOS transistors.. CO2- App (16)
 Or
 (b) Discuss the principles of constant field and lateral scaling. .Write the effects of the above scaling methods on the device characteristics. CO2- Ana (16)
18. (a) Explain the domino and dual rail domino logic families with neat diagram. CO3- U (16)
 Or
 (b) (i) Explain the domino and dual rail domino families with neat diagrams. CO3- Ana (8)
 (ii) Describe the different methods of reducing static and dynamic power dissipation in CMOS circuits CO3- Ana (8)

19. (a) What is semi custom design ASIC? Explain standard cell based design in detail. CO4- U (16)
- Or
- (b) Explain about building block architecture of FPGA. CO4- U (16)
20. (a) Write the VHDL program to design the multiplexer and demultiplexer circuits. CO5- U (16)
- Or
- (b) (i) Construct a VHDL code for JK Flip flop. CO5- App (8)
- (ii) Develop a VHDL program for 4:1 MUX CO5- App (8)

