

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53504

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Third Semester

Electronics and Instrumentation Engineering

15UEI304 - DIGITAL ELECTRONICS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Which of the following is minimum error code?
(a) Octal code (b) Grey code
(c) Binary code (d) Excess 3 code
- Which of the following expressions is in the sum-of-products (SOP) form?
(a) $AB + CD$ (b) $AB(CD)$ (c) $(A + B)(C + D)$ (d) $(A)B(CD)$
- How many bits are required to store one BCD digit?
(a) 1 (b) 2 (c) 3 (d) 4
- The number of full and half-adders required to add 16-bit numbers is
(a) 8 half-adders, 8 full-adders (b) 1 half-adder, 15 full-adders
(c) 16 half-adders, 0 full-adders (d) 4 half-adders, 12 full-adders
- For which of the following flip-flops, the output is clearly defined for all combinations of two inputs
(a) Q type flip-flop (b) R-S flip-flop (c) J-K flip-flop (d) D flip-flop
- What is the difference between a ring shift counter and a Johnson shift counter?
(a) there is no difference (b) a ring is faster
(c) the feedback is reversed (d) the Johnson is faster

7. Which hazard is overcome by properly designed two level AND-OR or OR-AND circuit
- (a) dynamic hazard (b) static-0 hazard
(c) static-1 hazard (d) none of the above
8. Table that is not a part of asynchronous analysis procedure.
- (a) transition table (b) state table
(c) flow table (d) excitation table
9. Which of the memory is volatile memory?
- (a) ROM (b) RAM (c) PROM (d) EEPROM
10. Which of the following memories uses one transistor and one capacitor as basic memory unit?
- (a) SRAM (b) DRAM
(c) Both SRAM and DRAM (d) None of these

PART - B (5 x 2 = 10 Marks)

11. Define De-morgan's theorem.
12. Draw $Y = A + BCD'$ using NAND only.
13. Write down the characteristic equation for JK flip flop.
14. Differentiate fundamental mode and pulse mode asynchronous circuits.
15. Draw the logic diagram of bipolar RAM cell.

PART - C (5 x 16 = 80 Marks)

16. (a) Minimize the given switching function using Quine-Mcclusky method.
 $f(x_1, x_2, x_3, x_4) = \Sigma(0, 5, 7, 8, 9, 10, 11, 14, 15)$. (16)

Or

- (b) Simplify the following expression using K-map
- (i) $Y = \sum_m (7, 9, 10, 11, 12, 13, 14, 15)$
- (ii) $Y = m_1 + m_5 + m_{10} + m_{11} + m_{12} + m_{13} + m_{15}$ (16)

17. (a) Design a BCD adder and explain its working with necessary logic diagram. (16)

Or

- (b) (i) Give the CMOS logic circuit for NOR gate and explain its operation. (8)
(ii) Explain the TTL circuit output connections. (8)
18. (a) Design and explain a ring counters with suitable example. (16)
- Or
- (b) Explain the operation of universal shift register with logic diagram. (16)
19. (a) (i) Define races and explain its types. (8)
(ii) Explain how hazards that occur in asynchronous circuits (8)
- Or
- (b) What are hazards? When does the hazard occur in combinational circuits and quote an example? Name the types of hazards and how they are avoided. (16)
20. (a) Explain ROM, ROM architecture, types of ROM and its application. (16)
- Or
- (b) (i) Draw the block diagram of a PLA and explain its IC 7575-PLA. (16)
-

