

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 43403**

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Third Semester

Electronics and Communication Engineering

14UEC303 - CIRCUIT THEORY

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- Ohm's law is given by
  - $V = ZI$
  - $I = GV$
  - both (a) and (b)
  - none of these
- Mesh analysis makes use of the basic equation
  - $[V] = [Z] [I]$
  - $[I] = [Z] [V]$
  - $[V] = [Y] [I]$
  - $[I] = [Y] [V]$
- A circuit has 7 nodes and 5 independent loops. The number of branches in the network is
  - 2
  - 11
  - 12
  - 10
- Maximum power is transferred when load impedance is
  - Equal to source resistance
  - Equal to half of the source resistance
  - Equal to zero
  - Equal to double of the source resistance
- What is the  $Q$  (Quality factor) of a series circuit that resonates at 6 kHz, has equal reactance of 4 kilo-ohms each, and a resistor value of 50 ohms?
  - 0.001
  - 50
  - 80
  - 4.0
- Transient behavior occurs
  - Only in resistive circuits
  - Only in inductive circuits
  - Only in capacitive circuits
  - Both inductive and capacitive circuits

7. Dot convention in coupled circuits is used
- To measure the mutual inductance
  - To determine the polarity of the mutually induced voltage in coils
  - To determine the polarity of the self-induced voltage in coils
  - To measure the self-inductance
8. In two wattmeter method of power measurement, when the power factor of load is zero leading or lagging the two wattmeter will give\_\_\_\_\_ reading.
- Zero
  - equal
  - equal and opposite
  - not equal
9. For a two port network to be reciprocal
- $Z_{11}=Z_{22}$
  - $y_{21}=y_{22}$
  - $h_{21}= - h_{12}$
  - $AD-BC=0$
10. An ideal filter should have
- Zero attenuation in the pass band
  - Infinite attenuation in the pass band
  - Zero attenuation in the attenuation band
  - Infinite attenuation in the attenuation band

PART - B (5 x 2 = 10 Marks)

- State Kirchhoff's laws for electric circuits.
- State Norton's theorem.
- Give the expressions for series and parallel resonance frequency.
- Write the symmetrical components of three phase system.
- Write the expression of Y parameters in terms of ABCD parameters.

PART - C (5 x 16 = 80 Marks)

16. (a) Find the mesh currents for the following electric circuit shown in Figure -1. (16)


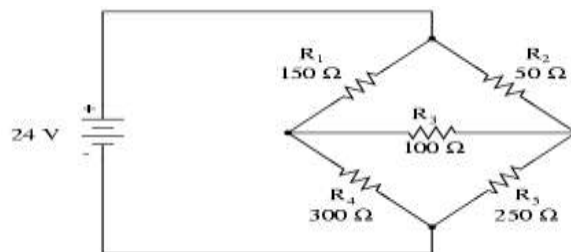


Figure 1

Or

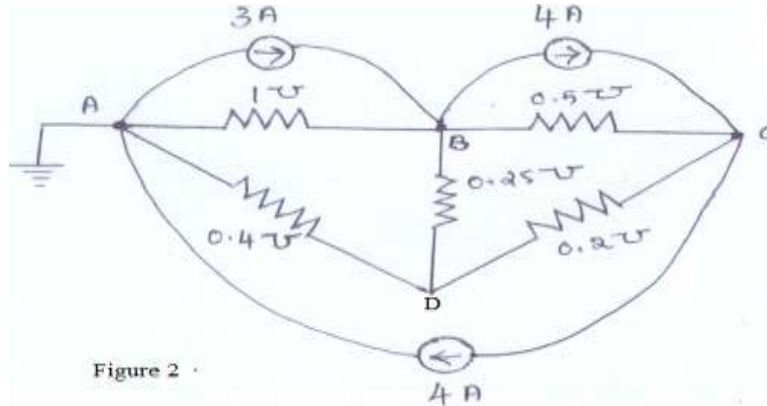- (b) (i) Find  $V_{BD}$  by nodal analysis for the circuit shown in the figure 2 (10)



- (ii) Obtain the expression for star-delta transformation. (6)

17. (a) Determine the current in the  $10\text{-}\Omega$  resistor for the circuit shown in Figure 4 by using superposition theorem. (16)

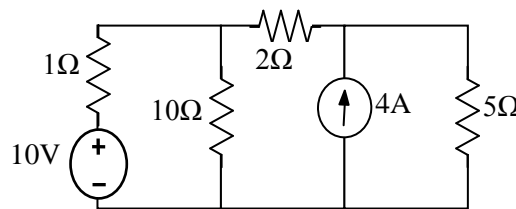


Figure 4

Or

- (b) (i) Using Thevenin's theorems find  $V$  and  $I$  for the circuit shown in figure 4 (14)

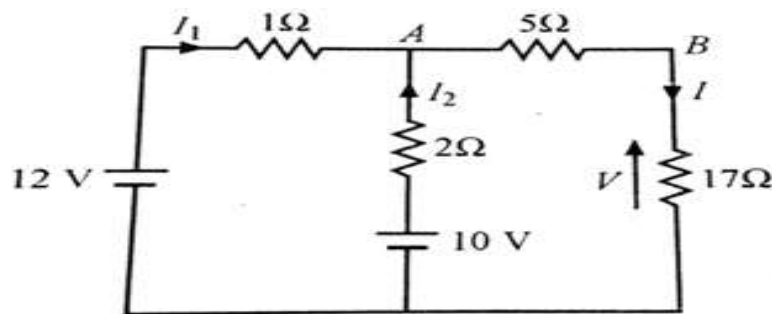


Figure 4

- (ii) State reciprocity theorem. (2)

18. (a) A RLC series circuit consists of  $R = 16\ \Omega$ ,  $L = 5\text{ mH}$  and  $C = 2\ \mu\text{F}$ . Calculate the quality factor, bandwidth and half-power frequencies. (16)

Or

- (b) (i) Derive the equation for transient response of RLC circuit for DC input. (12)  
(ii) Draw the pole –zero diagram of the given network function

$$I(s) = \frac{5s}{(s+1)(s^2+4s+8)} \quad (4)$$

19. (a) Two coils connected in series have an equivalent inductance of  $0.8 H$  when connected in aiding and an equivalent inductance of  $0.4 H$  when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking  $k = 0.55$ . (16)

Or

- (b) (i) Discuss in detail the relation between phase current, line current in a star and delta connected three phase system. (6)  
(ii) Three pure resistances value  $200 \Omega$  each are connected to a 3 phase,  $440 V$ ,  $50 Hz$  supply. Determine the line, phase values of current, voltage and active power in both star and delta connections. (10)
20. (a) The current  $I_1$  and  $I_2$  at the input port and output port respectively of a two port network are given by

$$I_1 = 6V_1 - V_2 \text{ and } I_2 = -V_1 + 2 V_2$$

Find the equivalent pie-network and the input impedance when a load of  $(4+j7) \Omega$  is connected across the output port. (16)

Or

- (b) (i) Design a low pass filter having cut – off frequency of  $2 KHz$ , to operate with a terminal load resistance of  $500 \Omega$ . (8)  
(ii) Design a high pass filter having a cut-off frequency of  $1 KHz$  with a load resistance of  $600 \Omega$ . (8)