

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53403

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Third Semester

Electronics and Communication Engineering

15UEC303 - CIRCUIT THEORY

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks


Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

1. A resistor is connected across a 50 V source. What is the current in the resistor if the color code is red, orange, orange, silver? CO1- R

(a) 2 mA (b) 2.2 mA (c) 214 mA (d) 21.4 mA

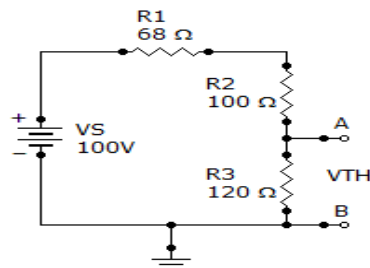2. Find the Thevenin equivalent (V_{TH} and R_{TH}) between terminals A and B of the circuit given below. CO2- U



(a) 4.16 V, 120 Ω (b) 41.6 V, 120 Ω (c) 4.16 V, 70 Ω (d) 41.67 V, 70 Ω

3. In a series RLC circuit that is operating above the resonant frequency, the current CO3-U

(a) Lags the applied voltage (b) leads the applied voltage
(c) is in phase with the applied voltage (d) is zero

4. To increase the current in a series RL circuit, the frequency CO4-R

(a) Should be increased (b) Should be decreased
(c) Should be constant (d) Cannot be determined without values

5. In a Y-connected circuit, the magnitude of each line current is CO5-R


(a) One-third the phase current (b) Three times the corresponding phase current
(c) Equal to the corresponding phase current (d) Zero

PART – B (5 x 3= 15Marks)

6. State Kirchoff's circuital laws. CO1- R
7. State Compensation theorem. CO2- R
8. Define bandwidth. CO3- U
9. In a series RLC circuit $L=2H$, and $C=5\mu f$. Determine the value of R to give critical damping. CO4- App
10. What is meant by coupling coefficient? CO5- R


PART – C (5 x 16= 80 Marks)

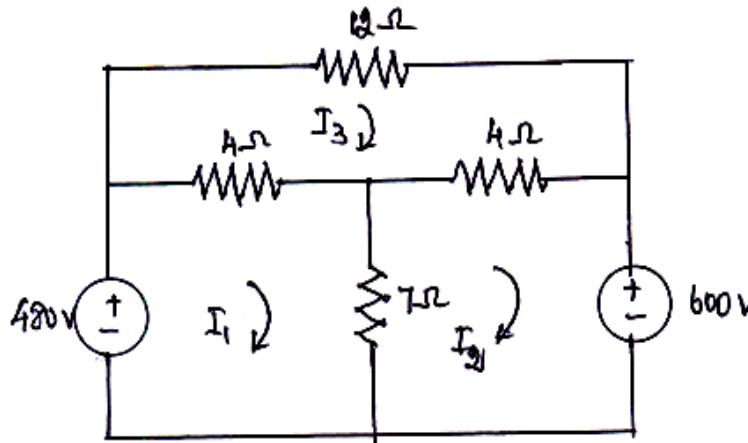11. (a) Write the mesh equations for the circuit shown in the figure and solve for the current in the 12 ohm resistor. CO1-App (16)




Or

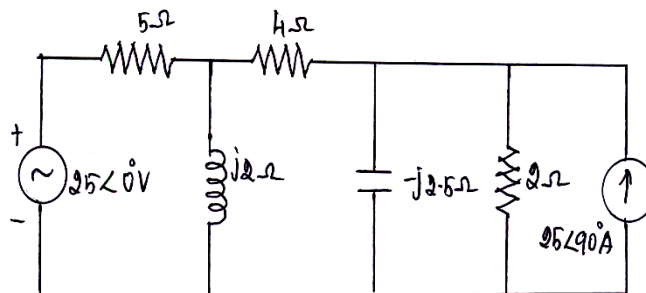- (b) Using nodal analysis, find the current through the 4 ohm resistor in the circuit shown in figure. CO1-App (16)




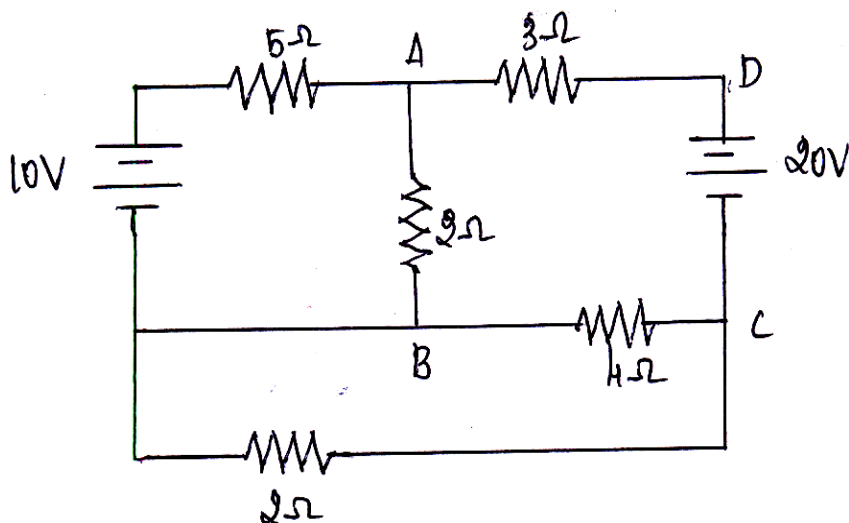12. (a) Find the current in the 2 ohm resistor between A and B for CO2- App (16)
the network using superposition theorem.



Or

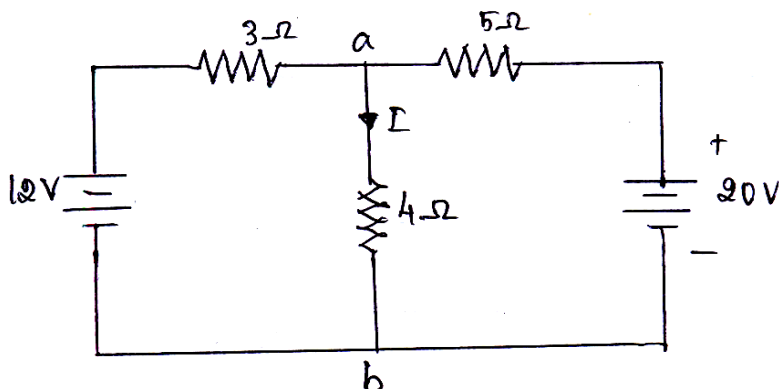- (b) Calculate the current I in 4 ohm resistor in the figure using CO2- App (16)
Millman's theorem.



13. (a) (i) Derive the expression for resonant frequency of a series RLC CO3- U (10)
circuit.

- (ii) A series RLC circuit with $Q=250$ is resonant at 1.5MHz. Find CO3- App (6)
the frequencies at half power points and also band width.

Or

- (b) (i) Derive the expression for resonant frequency of a parallel RLC CO3- U (10)
circuit.

- (ii) A current source is applied to a parallel combination of R,L CO3- App (6)
and C, where $R=10\Omega$, $L=1H$ and $C=1\mu f$.

(a) Compute the resonant frequency.


(b) Find the quality factor.

(c) Calculate the value of the bandwidth.

14. (a) A resistance R and a $2\mu\text{f}$ capacitor are connected in series across a 200V direct supply. Across the capacitor is a neon lamp that strikes at 120V . Calculate R to make the lamp strike 5 sec after the switch has been closed. If $R=5\text{M}\Omega$, how long will it take the lamp to strike? CO4 E (16)

Or

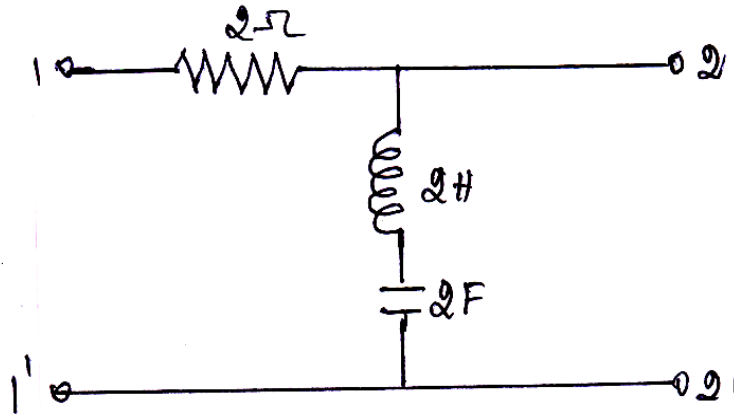- (b) Determine the admittance parameters of the two port network shown. CO4-App (16)



15. (a) Explain the single tuned and double tuned circuit. CO5- U (16)

Or

- (b) (i) A balanced star connected load of $(8+j6)\ \Omega$ /phase is connected to a 3 phase, 230V , and 50Hz supply. Determine the line currents, power factor, power, reactive volt amperes and total volt amperes. CO5- App (10)

- (ii) A wye load with $Z_A = (3+j0)\ \Omega$, $Z_B = (2+j3)\ \Omega$ and $Z_C = (2-j1)\ \Omega$ is connected to a 3phase 4 wire, 100volts , CBA system. Find the currents in all four lines. CO5- App (6)