

C

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code : 53404

B.E./B.Tech. DEGREE EXAMINATION, NOV 2018

Third Semester

Electronics and Communication Engineering

15UEC304-ELECTRONIC CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (5 x 1 = 5 Marks)

- Both the collector-base and base-emitter junctions are forward-biased in CO1- R
(a) Active region (b) Cutoff region (c) Saturation region (d) All the above
- A differential amplifier with differential gain of 300 and common mode gain of 0.2 will have CMRR of CO2- App
(a) 63.52 dB (b) 52.63dB (c) 20dB (d) 40dB
- The cutoff frequency that occurs when the common emitter current gain value drops to 0.707 of its low frequency value is called as CO3- U
(a) Alpha frequency (b) Beta frequency (c) Gamma frequency (d) Bandwidth
- The output stage of a multistage amplifier usually employs CO4-R
(a) Push-pull amplifier (b) Preamplifier (c) Class A amplifier (d) All the above
- Negative feedback is employed in CO5- R
(a) Oscillators (b) Rectifiers (c) Amplifier (d) None of these

PART – B (5 x 3= 15Marks)

- Define Thermal Runaway? CO1-R
- Why CE configuration is preferred for amplification? CO2-U
- Find the unity gain bandwidth of MOSFET whose $g_m = 6 \text{ mA/V}$, $C_{gs} = 8 \text{ pF}$, CO3-App

$C_{gd} = 4 \text{ pF}$ and $C_{ds} = 1 \text{ pF}$.

- 9. Compare the efficiencies of all the power amplifiers.
- 10. Mention the applications of class C tuned amplifier.

CO4-Ana


CO5- R

PART – C (5 x 16= 80Marks)

- 11. (a) For the circuit shown in figure, let $h_{fe} = 100$.

CO1-App (16)

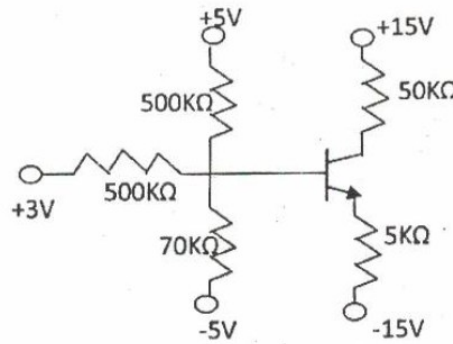- (i) Find V_{TH} and R_{TH} for the base circuit.
- (ii) Determine I_{CQ} and V_{CEQ} .
- (iii) Draw the DC load line.



Or

- (b) With necessary diagrams, explain the methods used in biasing the FET and MOSFET. CO1- U (16)
- 12. (a) Draw and explain Darlington pair using BJT and derive the expressions for Voltage gain, Current gain, input and output impedance. CO2- U (16)

Or

- (b) Explain the operation of an emitter coupled differential amplifier with constant current source to improve stability and derive its CMRR. CO2- U (16)
- 13. (a) With neat sketch, explain hybrid- π equivalent circuit of CE amplifier. Derive the expression for various components in terms of 'h' parameters. CO3-U (16)

Or

- (b) Find the Midband gain A_m and upper 3dB frequency f_h of CS amplifier fed with a signal source having an internal resistance $R_{sig}=100\text{ K}\Omega$. The amplifier has $R_G=4.7\text{ M}\Omega$, $R_D=R_L=15\text{ K}\Omega$, $g_m=1\text{ mA/V}$, $r_0=150\text{ K}\Omega$, $C_{gs}=1\text{ pF}$ and $C_{gd}=0.4\text{ pF}$. CO3-App (16)
14. (a) Explain the working of a transformer – coupled class A power amplifier circuit and derive the expression for its efficiency. CO4 U (16)
- Or
- (b) Draw the circuit diagram and explain the operation of class B push pull amplifier. Also discuss its merits. CO4 U (16)
15. (a) With a neat diagram, derive the expression for R_{if} , R_{of} , A_v and A_{vf} for the following CO5- U (8)
- (i) Voltage series feedback amplifier
- (ii) Current shunt feedback amplifier CO5- U (8)
- Or
- (b) Discuss Nyquist criterion for stability of feedback amplifier, with the help of Nyquist plot. CO5- U (16)

