| Reg. No. : | | | | | | | | | | | |
|------------|--|--|--|--|--|--|--|--|--|--|--|
|------------|--|--|--|--|--|--|--|--|--|--|--|

Question Paper Code: 36401

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Sixth Semester

Electrical and Electronics Engineering

01UEE601 - ELECTRIC DRIVES AND CONTROL

(Regulation 2013)

Duration: Three hours Maximum: 100 Marks

Answer ALL Questions

PART A - $(10 \times 2 = 20 \text{ Marks})$

- 1. What are the three modes of operation of an electrical drive?
- 2. Drive the equations governing motor load dynamics.
- 3. Write down the speed torque relation for single phase fully controlled converter fed DC motor in continuous conduction mode.
- 4. What is time ratio control?
- 5. List out the different methods of speed control of 3 phase induction motors.
- 6. What is the significance of field weakening mode control in induction motor drive system?
- 7. What is meant by power factor control?
- 8. Explain power factor control of synchronous motor with relevant vector diagram.
- 9. What is field weakening mode control in dc drives?
- 10. Name any two simulation packages used for drive systems.

PART - B (5 x 16 = 80 Marks)

| 11. | (a) | Explain the multi-quadrant operation of the electric drive with the help of Load. | Hoist (16) |
|-----|-----|---|----------------|
| | | Or | |
| | (b) | (i) Classify the electrical loads according to the speed-torque characteristics explain with examples. | and (8) |
| | | (ii) Explain the multi-quadrant operation of the electric drive with the help of I Load. | Hoist (8) |
| 12. | (a) | With neat sketches explain about the 3phase controlled rectifier fed DC drives. | (16) |
| | | Or | |
| | (b) | Explain the operation of four quadrant chopper control in dc drives. | (16) |
| 13. | (a) | Explain about VSI induction motor drives and also closed loop control for induct motor drives. | ion (16) |
| | | Or | |
| | (b) | Explain about V/F control in Induction motor. | (16) |
| 14. | (a) | Explain static scherbius drive operation in detail with necessary diagram equations. | and (16) |
| | | Or | |
| | (b) | With necessary diagrams explain the vector control of induction motor drives. | (16) |
| 15. | (a) | Derive the transfer function of DC motor-load system. | (16) |
| | | Or | |
| | (b) | Discuss the current controller design using (i) P controller and (ii) PI controller separately excited DC motor drive system. | er for (16) |
| | | | |
| | | | |