

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 45604

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2018

Fifth Semester

Instrumentation and Control Engineering

14UIC504 - POWER ELECTRONICS AND APPLICATIONS

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- _____ diodes have relatively large reverse recovery times of the about $25\mu s$.
(a) General purpose (b) Fast recovery
(c) Schottky (d) None of the above
- _____ is not available in high voltage and high current ratings.
(a) TRIAC (b) DIAC (c) SCR (d) MOSFET
- Reactive loading of supply lines by a converter is directly dependent on
(a) Displacement angle only (b) Displacement angle and distortion factor
(c) Back emf in the load circuit (d) Circuit configuration
- A Converter which can operate in both 3-pulse and 6-pulse modes is a
(a) 1-phase full converter (b) 3-phase half-wave converter
(c) 3-phase semi converter (d) 3-phase full converter
- Average output voltage for step down chopper with input voltage $V_s=150V$ with duty cycle as 60% is $V_o=$
(a) 90V (b) 200V (c) 85V (d) 110V

6. A step – up chopper has V_s as the source voltage and α as the duty cycle. The output voltage for this chopper is given by
- (a) $V_s (1 + \alpha)$ (b) $V_s / (1 - \alpha)$
(c) $V_s (1 - \alpha)$ (d) $V_s / (1 + \alpha)$
7. In Single-Pulse modulation of PWM inverters, third harmonic can be eliminated if pulse width is equal to
- (a) 30° (b) 60° (c) 120° (d) 150°
8. A Single phase CSI has capacitor C as the load. For a constant source current, the voltage across the capacitor is
- (a) Square Wave (b) Triangular Wave
(c) Step Function (d) Pulsed Wave
9. _____ is used for speed control of high power ac drives.
- (a) Chopper (b) Inverters
(c) Cycloconverters (d) Voltage controllers
10. The inverter of _____ mode would experience a direct short circuit through SCRs.
- (a) 120° (b) 240° (c) 180° (d) none of these

PART - B (5 x 2 = 10 Marks)

11. Comment on forced commutation.
12. Define phase angle control.
13. What is meant by step-up and step-down chopper?
14. Define total harmonic distortion.
15. List the application of cycloconverters

PART - C (5 x 16 = 80 Marks)

16. (a) Explain the constructions and switches characteristics of power MOSFET. (16)
- Or
- (b) Describe the working of an IGBT. How does latch – up occur in an IGBT. (16)
17. (a) (i) List the classification of converters with circuit symbol. (8)
(ii) Elaborate the working principle of half wave rectifier with RL load. (8)

- (b) Explain the operation of dual converter with a neat circuit diagram. (16)
18. (a) Explain the current limit control and time ratio control as applied to dc chopper. (16)

Or

- (b) Describe the working principle of zero controlled switching converters. (16)
19. (a) Discuss the principle of working of a three-phase bridge inverter with an appropriate circuit diagram. Draw phase and line voltage waveforms on the assumption that each thyristor conducts for 180° and the resistive load is star connected. The sequence of firing of various SCRs should also be indicated in the diagram. (16)

Or

- (b) Discuss the working principle of current source inverter of single phase capacitor commutated inverter and auto sequential commutated inverter. (16)
20. (a) Describe the working of a multistage sequence control of voltage controllers. (16)

Or

- (b) Describe the matrix converter. (16)
-

