

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 41343**

B.E. / B.Tech. DEGREE EXAMINATION, NOVEMBER 2015

Third Semester

Electronics and Communication Engineering

14UEC303 - CIRCUIT THEORY

(Regulation 2014)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

- The number of independent loops for a network with  $n$  nodes and  $b$  branches is
  - $n-1$
  - $b-n$
  - $b-n+1$
  - independent for the number of nodes
- The nodal methods of circuit analysis is based on
  - KVL and Ohm's law
  - KCL and Ohm's law
  - KCL and KVL
  - KCL, KVL and Ohm's law
- Superposition theorem is not applicable to networks containing
  - nonlinear elements
  - dependent voltage source
  - dependent current source
  - transformers
- The maximum power that can be transferred to the load  $R_L$  from the voltage source in Fig. 1 is

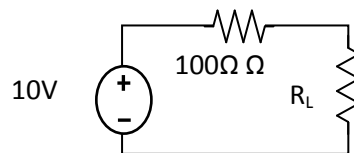


Figure 1

- 1 W
- 10 W
- 0.25 W
- 0.5 W

5. What is the  $Q$  (Quality factor) of a series circuit that resonates at  $6\text{ kHz}$ , has equal reactance of  $4\text{ kilo-ohms}$  each, and a resistor value of  $50\text{ ohms}$ ?
- (a) 0.001                      (b) 50                      (c) 80                      (d) 4.0
6. The step function voltage is applied to an RLC series circuit having  $R = 2\text{ ohm}$ ,  $L = 1\text{ H}$  and  $C = 1$ . The transient current response of the circuit would be
- (a) over damped                      (b) critically damped  
(c) under damped                      (d) none of the above
7. Self-inductance of a magnetic coil is proportional to
- (a)  $N$                       (b)  $1/N$                       (c)  $N^2$                       (d)  $1/N^2$
8. A 3 phase load is balanced if all the three phases have the same
- (a) impedance                      (b) power factor  
(c) impedance and power factor                      (d) none of the above
9. A two - port network is symmetrical if
- (a)  $Z_{11}Z_{22} - Z_{12}Z_{21} = 1$                       (b)  $AD - BC = 1$   
(c)  $h_{11}h_{22} - h_{12}Z_{21} = 1$                       (d)  $Y_{11}Y_{22} - Y_{12}Y_{21} = 1$
10. For a two-port network to be reciprocal
- (a)  $Z_{11} = Z_{22}$                       (b)  $y_{21} = y_{12}$                       (c)  $h_{21} = -h_{12}$                       (d)  $AD-BC = 0$

PART - B (5 x 2 = 10 Marks)

11. A  $10\text{ A}$  current source has a source resistance of  $100\text{ ohm}$ . What will be the equivalent voltage source?
12. Write the expression for Millman's equivalent source of  $n$  number of parallel connected voltage sources.
13. A RC series circuit is excited by a dc voltage source of  $80\text{ V}$  by closing the switch at  $t = 0$ . Determine the voltage across the capacitor in a time of one time constant.
14. Write the symmetrical components of three phase system.
15. Write the expression of Y parameters in terms of ABCD parameters.

PART - C (5 x 16 = 80 Marks)

16. (a) Find the current in the  $5\text{ ohm}$  resistor of the circuit shown in Figure 2 by using mesh analysis. (16)

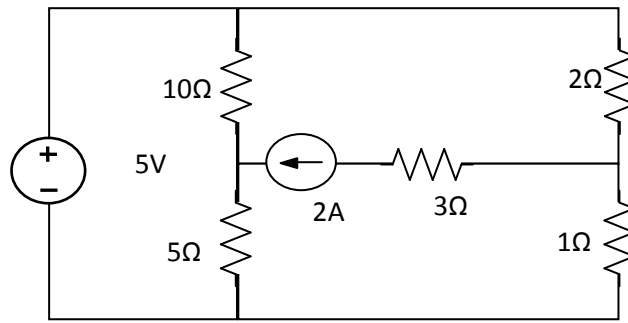


Figure 2

Or

- (b) Find the equivalent resistance between the terminals *A* and *B* for the circuit shown in Figure 3. (16)

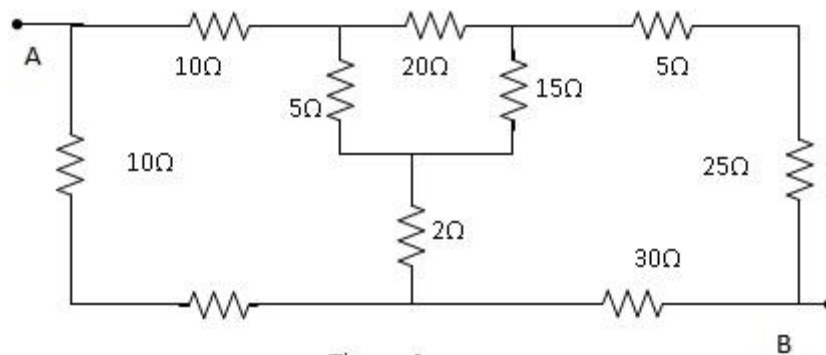


Figure 3

17. (a) Determine the current in the 10-Ω resistor for the circuit shown in Figure 4 by using superposition theorem. (16)


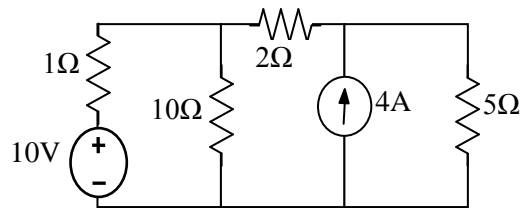


Figure 4

Or

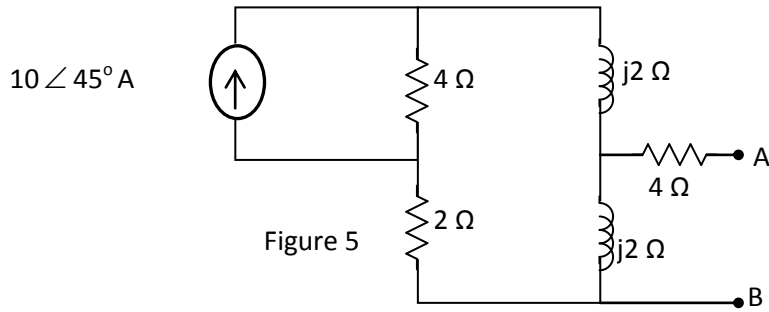- (b) In the circuit of figure 5, determine the impedance that can be connected across the terminals *A* and *B* for the maximum power. Also estimate the maximum power. (16)



18. (a) A RLC series circuit consists of  $R = 16 \Omega$ ,  $L = 5 \text{ mH}$  and  $C = 2 \mu\text{F}$ . Calculate the quality factor, bandwidth and half-power frequencies. (16)

Or

- (b) A capacitor has an initial charge of  $Q_0$ . A resistance  $R$  is connected across the capacitor at  $t = 0$ , to discharge the charge. The power transient of the capacitor  $P_C(t) = 800e^{-4000t} \text{ W}$ . Find the value of  $R$  and  $Q_0$ . Take  $C = 10 \mu\text{F}$ . (16)
19. (a) Two coils connected in series have an equivalent inductance of  $0.8 \text{ H}$  when connected in aiding and an equivalent inductance of  $0.4 \text{ H}$  when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking  $k = 0.55$ . (16)

Or

- (b) Three coils each having a resistance of  $20 \Omega$  and a reactance of  $15 \Omega$  are connected in (i) star and (ii) delta, across a three-phase,  $400 \text{ V}$ ,  $50 \text{ Hz}$  supply. Calculate in each case, the readings on two Watt meters connected to measure the power input. (16)
20. (a) The current  $I_1$  and  $I_2$  at the input port and output port respectively of a two port network are given by

$$I_1 = 6V_1 - V_2 \text{ and } I_2 = -V_1 + 2V_2$$

Find the equivalent pie-network and the input impedance when a load of  $(4+j7) \Omega$  is connected across the output port. (16)

Or

- (b) Currents  $I_1$  and  $I_2$  entering at port 1 and port 2 respectively of a two-port network are given below by the following equations:

$$I_1 = 0.5V_1 - 0.2V_2$$

$$I_2 = -0.2V_1 + V_2$$

Find the Z and ABCD parameters for the network. (16)