

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 31206**

B.E. / B.Tech. DEGREE EXAMINATION, NOVEMBER 2015

Second Semester

Civil Engineering

01UEE206 - BASIC ELECTRICAL AND ELECTRONICS ENGINEERING

(Common to Mechanical Engineering)

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. What are the limitations of ohm's law?
2. What is the use of copper shading band in energy meter?
3. Define back emf in a dc motor.
4. Define transformation ratio.
5. Define peak inverse voltage in a diode.
6. Why transistor is called as current controlled device?
7. Convert the decimal number  $139_{10}$  into its equivalent binary number.
8. What is a synchronous counter?
9. Define demodulation of a signal.
10. What are the basic types of communication systems?

PART - B (5 x 16 = 80 Marks)

11. (a) (i) A line voltage of 400 V is applied to three phase star connected identical impedances each containing of a  $4 \Omega$  resistance in series with  $3 \Omega$  inductive reactance. Find (a) line current (b) total power supplied. (8)

- (ii) Explain the construction details and principle of operation of an attraction type moving iron instrument. (8)

Or

- (b) (i) Find the average value, rms value and form factor of a periodic wave having the following values for equal time intervals changing suddenly from one value to the next. 0, 5, 10, 20, 50, 60, 50, 20, 10, 5, 0, -5, -10, etc. (8)
- (ii) With a neat sketch explain the principle and operation of the instrument which is used to measure the electrical power consumed during a specific period. (8)

12. (a) Draw and explain the constructional details of a dc generator and also derive the emf equation. (16)

Or

- (b) (i) Draw and explain the core type and shell type transformers. (6)
- (ii) Explain the principle of operation of single phase induction motor based on double field revolving theory. (10)

13. (a) (i) What is a Zener diode? Explain the operation of Zener diode and draw its characteristics. (8)
- (ii) Explain the operation of a full wave rectifier with neat diagram. (8)

Or

- (b) (i) Explain with neat diagram, input and output characteristics of a Common Base configuration of a BJT. (8)
- (ii) Explain in detail about small signal CE amplifier. (8)

14. (a) (i) What are universal gates? Explain their principle of working with necessary truth table. (8)
- (ii) Write short notes on RS-flip flop and D-flip flop. (8)

Or

- (b) Write in detail about Analog to Digital converter and Full adder with necessary diagram. (16)

15. (a) Explain the principle of amplitude and frequency modulation. (16)

Or

- (b) (i) With neat diagram, explain the basic components of satellite communication. (8)
- (ii) Explain the block diagram of optical fiber communication systems. (8)