

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 31237**

B.E. / B.Tech. DEGREE EXAMINATION, NOVEMBER 2015

Second Semester

Electrical and Electronics Engineering

01UEE207- ELECTRIC CIRCUITS

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 2 = 20 Marks)

1. Draw the VI characteristics of ideal and practical voltage sources.
2. A fluorescent tube choke is connected across 230V, 50Hz AC supply. If the resistance and reactance of the choke are  $100\Omega$ ,  $1H$  respectively, determine the current through the choke.
3. A 12 V DC source has internal resistance of  $1\Omega$ . The maximum power that can be delivered by the source is \_\_\_\_\_.
4. Two resistors  $10\Omega$  and  $20\Omega$  are connected in parallel. If the total current is 3A, what will be the current through each resistor?
5. Determine the resonance frequency of a RLC series circuit with  $R= 5 \Omega$ ,  $L = 0.02 H$  and  $C= 5 \mu F$ .
6. Two identical coils with  $L = 0.03 H$  have a coupling coefficient  $k = 0.8$ . Find the mutual inductance and the equivalent inductance with the coils connected in series opposing mode.
7. The time constant of an RC circuit with  $R=1k$  and  $C= 100\mu F$  is \_\_\_\_\_.

8. Write the condition for under damping and critical damping in RLC series circuit.
9. The phase voltage of a balanced three phase system is 230V. What will be the line voltage?
10. A star connected balanced load draws a current of 35 A per phase when connected to a 440 V supply. Determine the apparent power.

PART - B (5 x 16 = 80 Marks)

11. (a) Calculate (a) the equivalent resistance across the terminals of the supply (b) total current supplied by the source and (c) power delivered to 16 Ω resistors in the circuit shown in figure 1. (16)

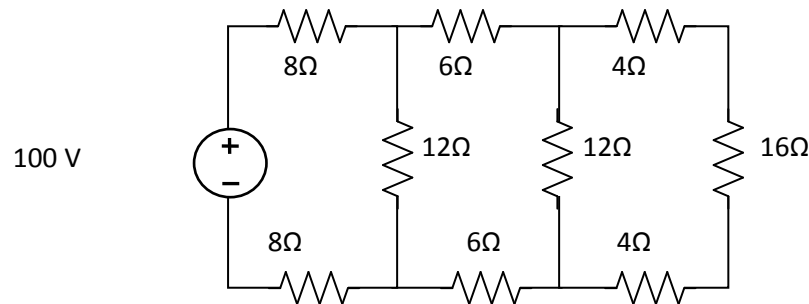


Figure 1

Or

- (b) (i) A series  $RL$  circuit with  $R = 5\Omega$  and  $L = 2mH$  has an applied voltage  $V = 150\sin 5000t$  Volts. Calculate current and power factor. (8)
- (ii) For the circuit shown in figure 2, determine current through various resistors using Nodal Method. (8)

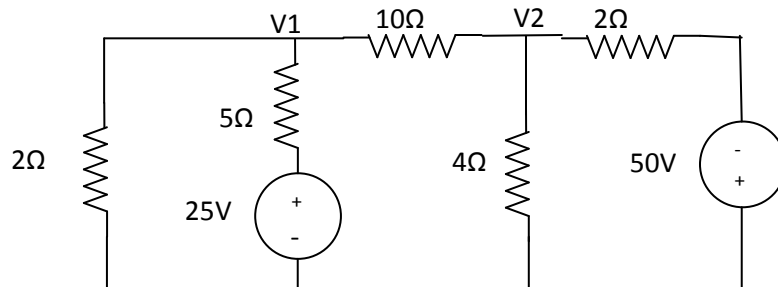


Figure 2

12. (a) (i) In the circuit shown in figure 3, obtain the current in each resistor using Network reduction method. (8)

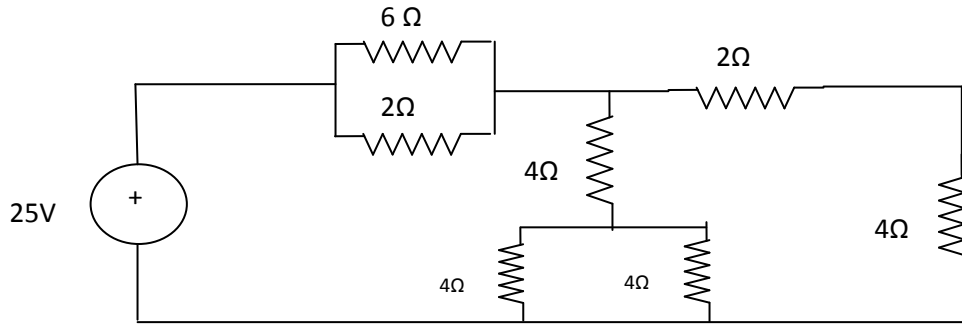


Figure 3

(ii) Using Superposition theorem, find current  $I$  in figure 4. (8)

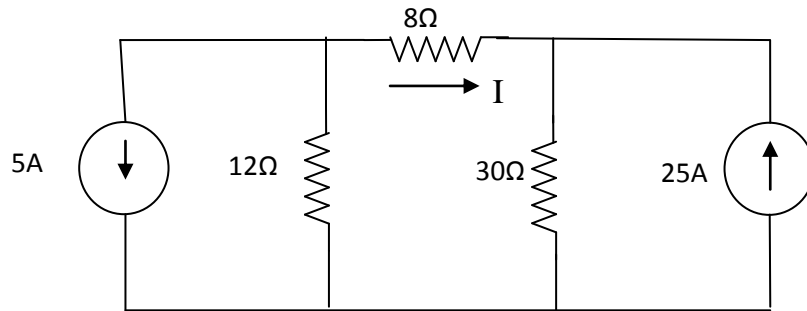


Figure 4

Or

(b) Find the equivalent resistance between  $A$  and  $B$ , in the network shown in figure 5. (16)

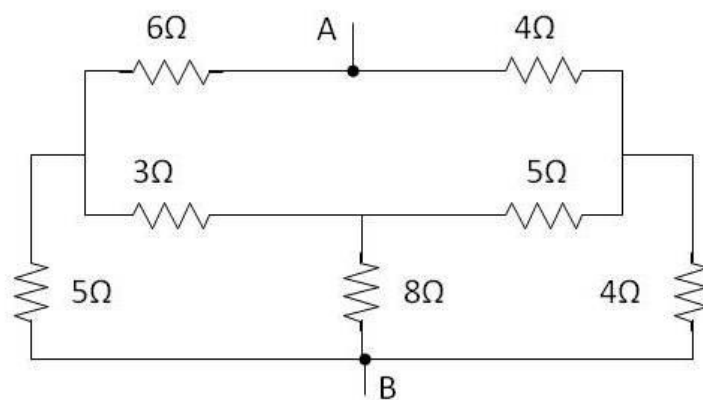


Figure 5

13. (a) (i) Derive the relationship between resonant frequency and Quality factor of an RLC series circuit. (8)
- (ii) Compute the Quality factor of an RLC series circuit with  $R=20\Omega$ ,  $L = 50mH$  and  $C = 1\mu F$ . (8)

Or

- (b) Two coils connected in series have an equivalent inductance of  $0.8 H$  when connected in aiding and an equivalent inductance of  $0.4 H$  when connected in opposing. Determine the mutual inductance. Calculate the self-inductance of the coils, by taking  $k = 0.55$ . (16)
14. (a) The switch in the circuit shown in figure 6. is closed on position 1 at  $t = 0$  and moved to position 2 after one time constant ( $\tau$ ). Obtain the current for  $0 < t < \tau$  and  $t > \tau$ . (16)

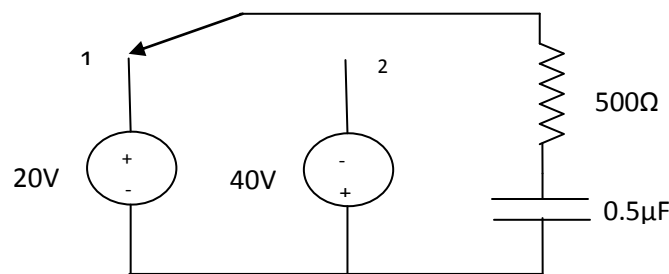


Figure. 6

Or

- (b) A capacitor has an initial charge of  $Q_o$ . A resistor  $R$  is connected across the capacitor at  $t = 0$ , to discharge the charge. The power transient of the capacitor  $p_c(t) = 800e^{-4000t}$  W. Find the value of  $R$  and  $Q_o$ . Take  $C = 10 \mu F$ . (16)
15. (a) A three phase balanced supply of  $400V$  (line to line)  $50Hz$  is given to a three phase delta connected load with impedance  $20 \angle 45^\circ \Omega$ . Obtain the line currents, power and power factor. Also draw the phasor diagram. (16)

Or

- (b) A  $500 V$ , three phase motor has an output of  $3.73 kW$  and operates at a power factor of  $0.85$ , with an efficiency of  $90\%$ . Calculate the reading of each of the two watt meter connected to measure the input. (16)