

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53052

B.E. / B.Tech. DEGREE EXAMINATION, NOV 2017

Third Semester

Electronics and Instrumentation Engineering

15UEI302 - ELECTRICAL AND ELECTRONIC MEASUREMENTS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. Frequency can be measured by
 - (a) Maxwell's bridge
 - (b) Schering bridge
 - (c) Heaviside bridge
 - (d) Wien bridge
2. Low resistance is measured by
 - (a) De Sauty's bridge
 - (b) Maxwell's bridge
 - (c) Kelvin's double bridge
 - (d) Wien bridge
3. The power delivered to a 3-phase load can be measured by the use of 2-wattmeter only when the
 - (a) Load is balanced
 - (b) Load is unbalanced
 - (c) 3-phase load is connected to the source through 3-wires
 - (d) 3-phase load is connected to the source through 4-wires
4. In an electro-dynamometer type of wattmeter
 - (a) the current coil is fixed
 - (b) the pressure coil is fixed
 - (c) any of the two coils
 - (d) both the coils should be movable
5. Current transformers and potential transformers are used to increase the ranges of
 - (a) DC ammeter and DC voltmeter
 - (b) AC ammeter and DC voltmeter
 - (c) AC ammeter and AC voltmeter
 - (d) DC ammeter and AC voltmeter

(b) Elaborate the constructional details and principle of working of single phase induction type energy meter. (16)

18. (a) Distinguish between DC and AC potentiometers, and discuss in detail about student type potentiometer. (16)

Or

(b) Draw the equivalent circuit and phasor diagram of a current transformer. Derive the expression for ratio and phase angle errors. (16)

19. (a) Draw and explain the circuit of a frequency measurement. What are the different methods used for high frequency determination. (16)

Or

(b) List the standard signals that can be generated using function generator and discuss the frequency measurement. (16)

20. (a) Explain about X – Y recorders and describe its applications. (16)

Or

(b) Explain with a neat sketch of Seven Segment display and Data Logger. (16)
