

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--

Question Paper Code : 51496

B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2016

Second Semester

Electrical and Electronics Engineering

EE 2151/EE 25/EE 1151/080280005/10133 EE 205 – CIRCUIT THEORY

(Common to Electronics and Instrumentation Engineering/Instrumentation and Control Engineering)

(Regulations 2008/2010)

Time : Three Hours

Maximum : 100 Marks

Answer ALL questions.

PART – A (10 × 2 = 20 Marks)

1. State Kirchoff's current law and voltage law.
2. Convert the voltage source shown in Fig. 2 into equivalent current source.

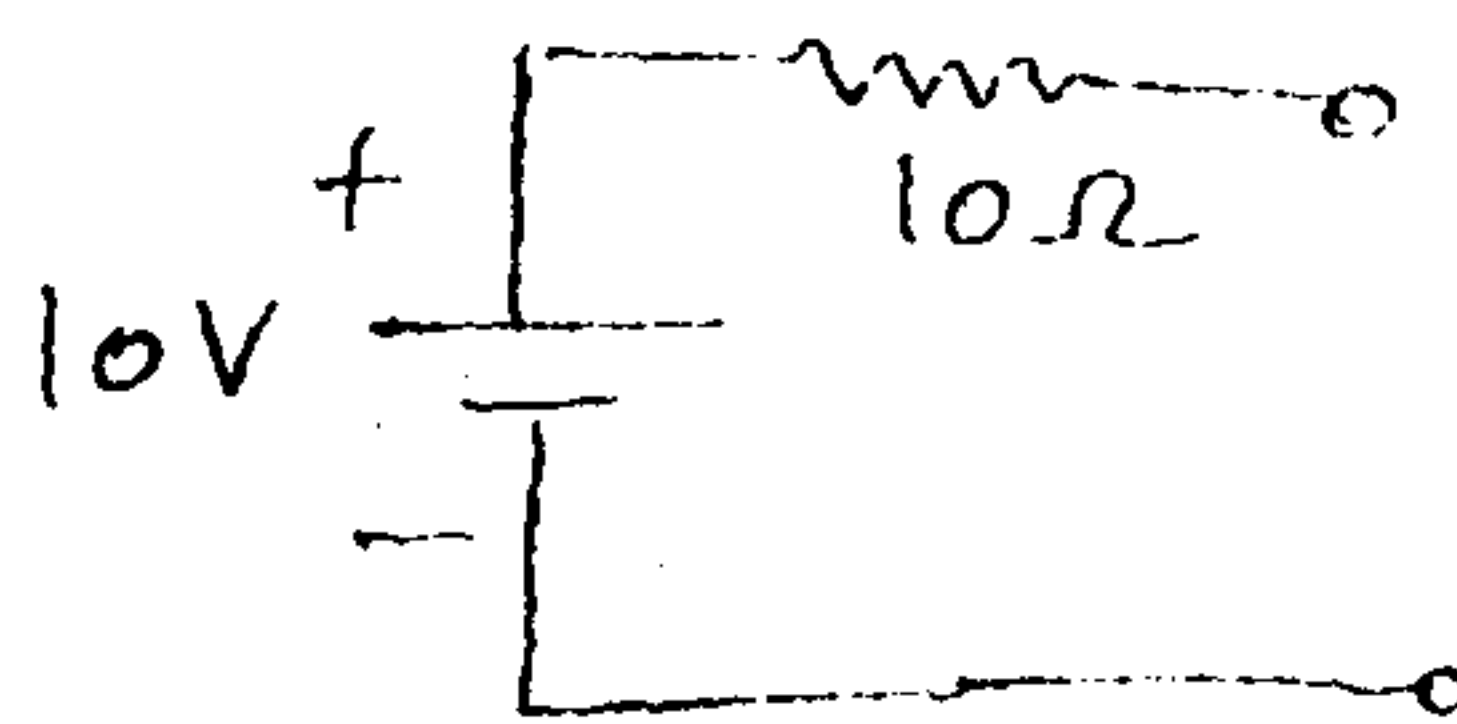


Fig. – 2

3. State the voltage division principle for two resistor in series and the current division principle for two resistors in parallel.
4. State Maximum power transfer theorem.
5. Define quality factor Q of a coil.

6. Sketch the frequency response of double tuned circuit.
7. What is meant by transient time ?
8. Write the purpose of Laplace transformation in the circuit analysis.
9. Draw the circuit diagram for a three phase delta connected source and a star connected load.
10. Write the expression for power for single phase and three phase AC circuit.

PART – B (5 × 16 = 80 marks)

11. (a) In the circuit shown in Fig. 11 (a), find the loop currents and the current through the $10\ \Omega$ and $5\ \Omega$ resistance along with their direction of flow. (16)

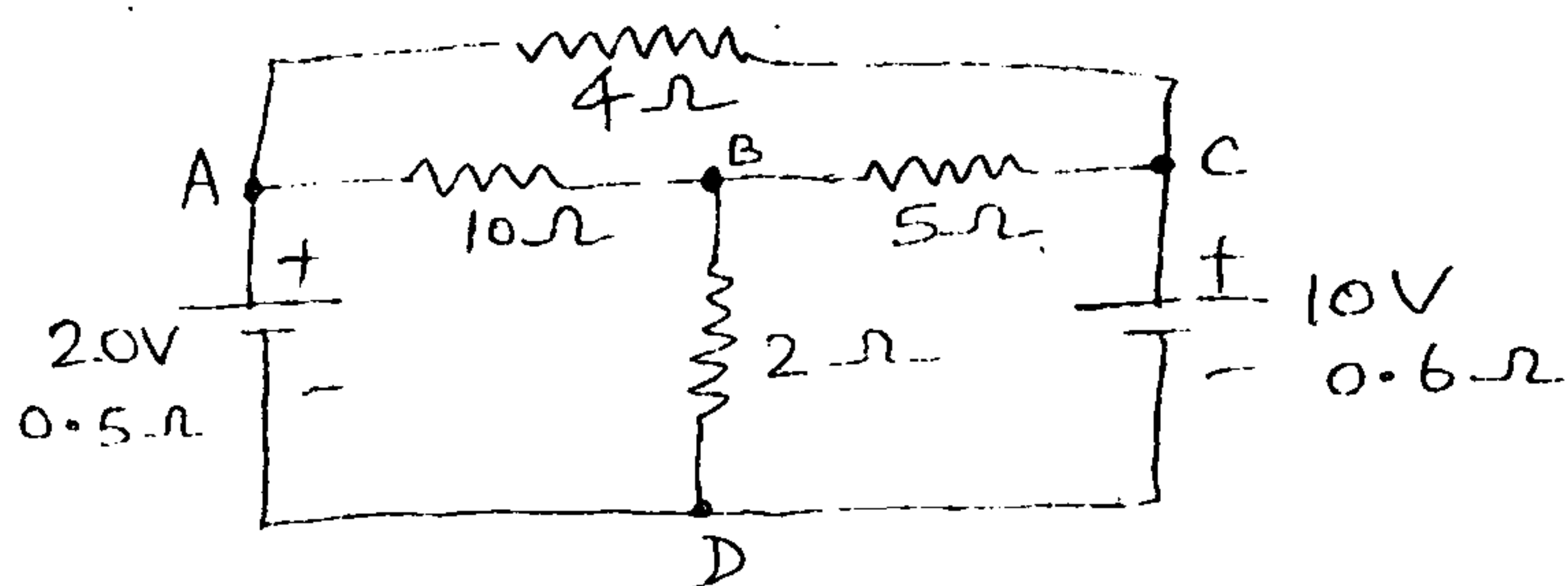


Fig. 11(a)

OR

- (b) In the circuit shown in Fig. 11. (b), find the nodal voltages V_1 , V_2 and V_3 and the current through $1\ \Omega$, $2\ \Omega$ and $3\ \Omega$. (16)

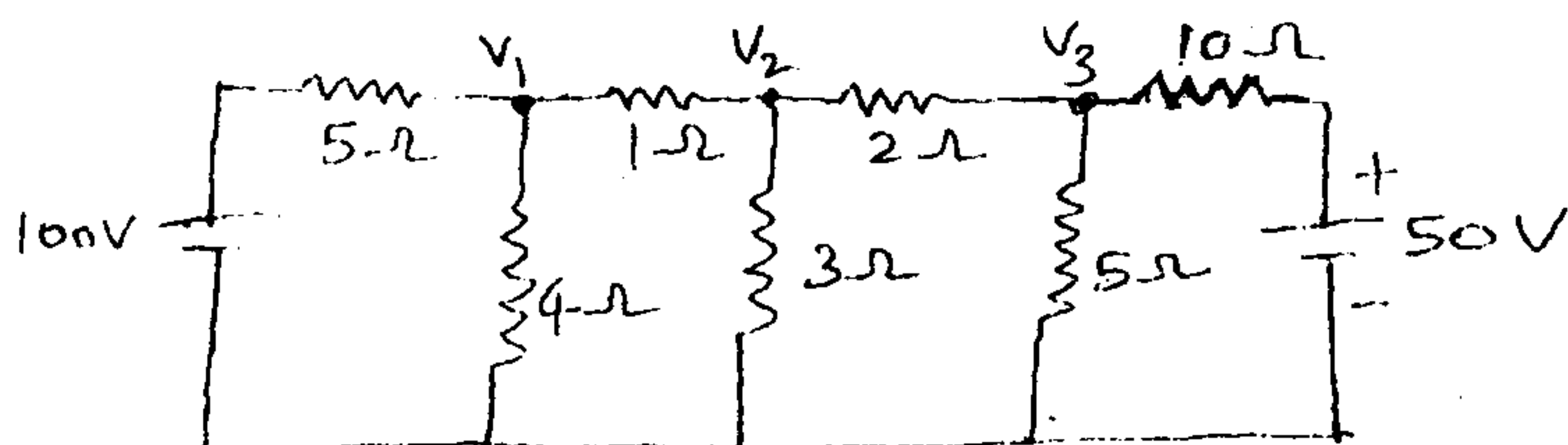


Fig. 11(b)

12. (a) (i) Explain the source transformation technique. (6)
- (ii) Use the superposition theorem to find the current through $4\ \Omega$ resistor in the circuit shown in Fig. Q. 12. (a) (ii). (10)

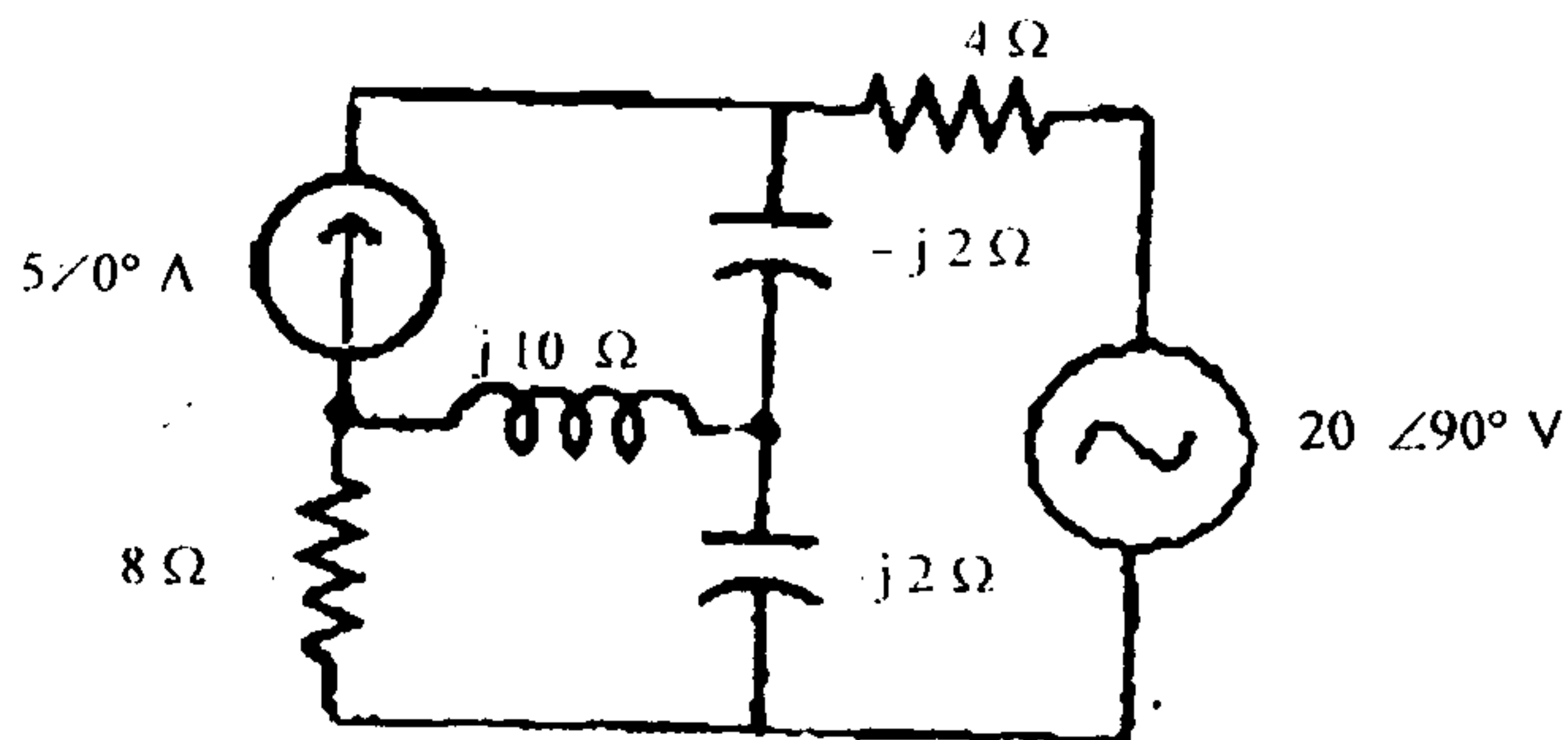


Fig. Q. 12 (a) (ii)

OR

- (b) (i) Derive expression for star connected resistances in terms of delta connected resistances. (8)
- (ii) Find the current through branch a-b of the network shown in Fig. Q. 12. (b) (ii) Using Thevenin's theorem. (8)

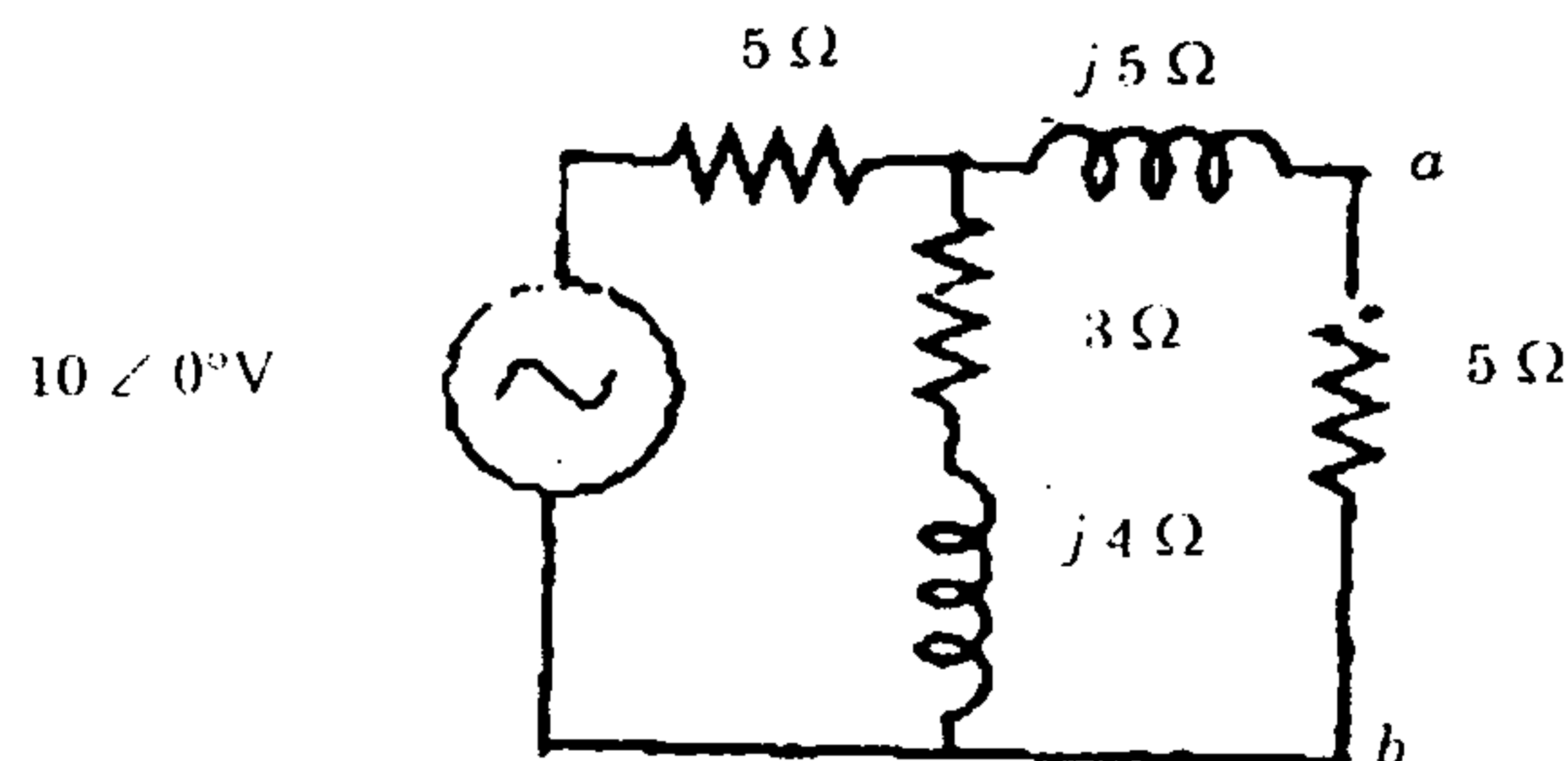


Fig. Q. 12 (b) (ii)

13. (a) A RLC series circuit has $R = 60\ \Omega$, $L = 160\ \text{mH}$ and $C = 160\ \mu\text{f}$. Find the resonant frequency under resonant condition obtain the current, power and the voltage drops across the various elements if the applied voltage is 300 V. (16)

OR

- (b) Illustrate the amplification factor with respect to frequency and coefficient of coupling of a single tuned circuit in detail. (16)

14. (a) A series RLC circuit with $R = 100 \Omega$, $L = 0.1 \text{ H}$ and $C = 100 \mu\text{F}$ has a DC voltage of 200 volts applied to it at $t = 0$ through a switch. Find the expression for the transient current. Assume initially relaxed circuit conditions.

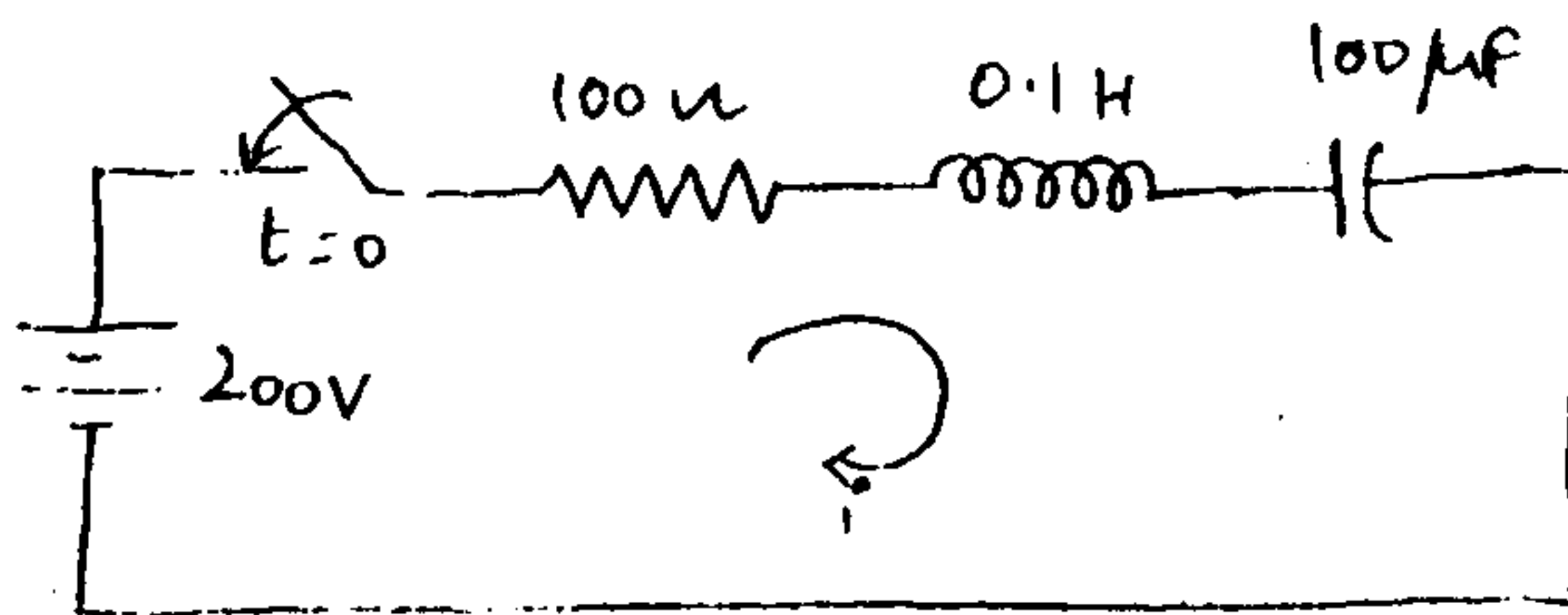


Fig. 14(a)

OR

- (b) (i) Define natural response and transient response. (4)
- (ii) In the circuit shown in figure. Q. 14. (b) (ii) find the time when the voltage across the capacitor becomes 25 V, after the switch is closed at $t = 0$. (12)

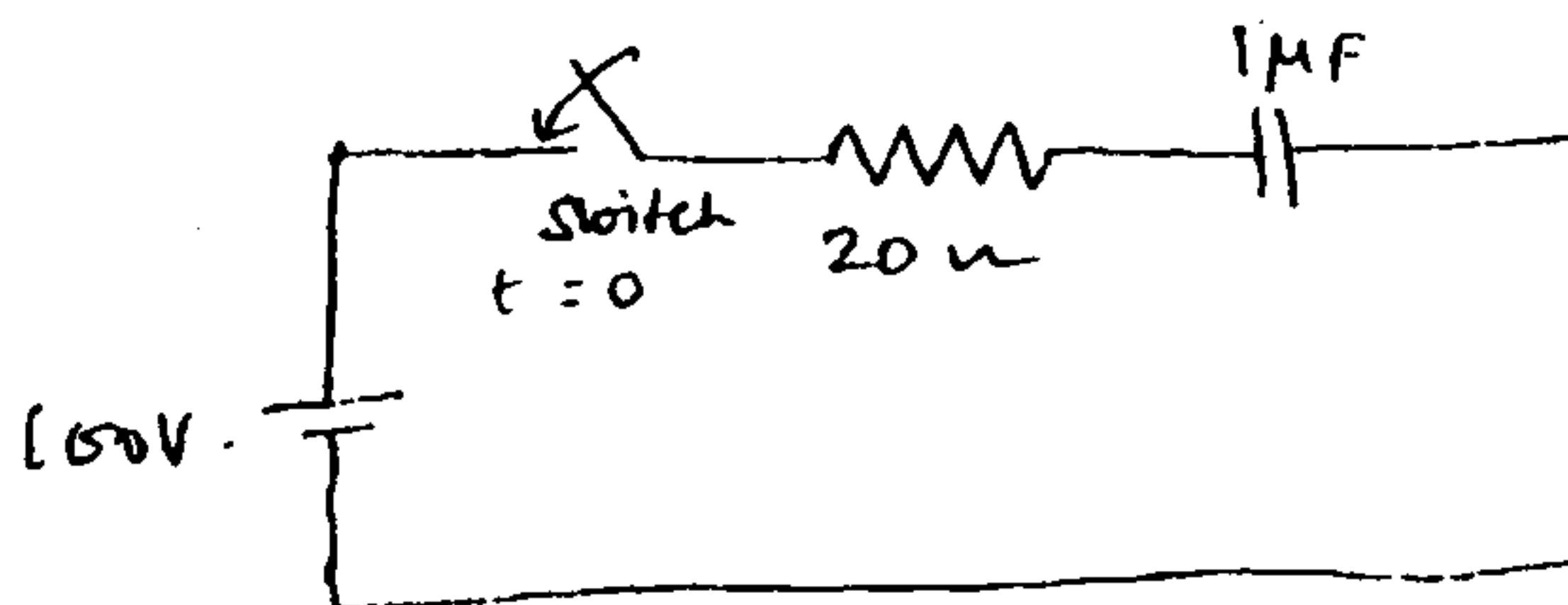


Fig. 14 (b)(ii)

15. (a) In a three phase three wire balanced system supplying power to a balanced three phase delta load find out the currents in all branches and lines. (16)
- OR
- (b) Describe the three phase power measurement by two wattmeter method. (16)