

Reg. No.

|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|
|  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |  |
|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|--|

**Question Paper Code : 51506**

**B.E./B.Tech. DEGREE EXAMINATION, MAY/JUNE 2016**

**Fifth Semester**

**Electrical and Electronics Engineering**

**EE 2301/EE 51/10133 EE504/10144 EE 504 – POWER ELECTRONICS**

**(Common to Instrumentation and Control Engineering)**

**(Regulations 2008/2010)**

**(Common to PTEE 2301/10144 EE 504 – Power Electronics for B.E. (Part-Time)**

**Fourth Semester – Electrical and Electronics Engineering – Regulations 2009/2010)**

**Time : Three Hours**

**Maximum : 100 Marks**

**Answer ALL questions.**

**PART – A (10 × 2 = 20 Marks)**

1. How Triac differs from SCR ?
2. What are the factors associated with switching loss ?
3. Define Harmonic factor.
4. How controlled rectifiers are used in battery charger application ?
5. What is the function of step-up chopper ?
6. What is meant by SMPS ? Mention its applications.
7. What are the advantages of space vector modulation over sinusoidal PWM ?
8. State the need for reduction of harmonics in inverters.
9. Draw the power circuit for single phase AC voltage controller using Triac.
10. What is matrix converter ?

**PART – B (5 × 16 = 80 Marks)**

11. (a) Explain the switching characteristics of IGBT. How it differs from MOSFET ? Also state the relation with switching loss and switching frequency. (16)

**OR**

- (b) Explain the basic structure, V-I characteristics and applications of any two power semiconductor devices in thyristor family. (16)

12. (a) Derive the expressions for performance parameters associated with input current of single phase fully controlled converter. (16)

**OR**

- (b) Draw the basic block diagram of a dual converter operating in circulating current mode and describe the operation with relevant waveforms. (16)

13. (a) Explain the different control strategies used for chopper. Compare its advantages and disadvantages. (16)

**OR**

- (b) Explain the operation of Boost converter with appropriate power circuit and waveforms. Derive the expression for voltage gain,  $L_{min}$  for continuous conduction and the value of capacitance. (16)

14. (a) With appropriate power circuit, discuss the principle of operation of three phase inverter with  $180^\circ$  thyristor conduction mode. Also, prepare a table which shows the sequence of firing of various SCRs. (12 + 4)

**OR**

- (b) Compare the performances of voltage source inverters, PWM inverters and current source inverters. (16)

15. (a) Explain the different configurations of single phase AC voltage controller with its power circuit and derive the expression for output voltage. (16)

**OR**

- (b) Describe the principle of working of single phase to single phase cycloconverter for both continuous and discontinuous conduction. (16)