

Reg. No. :

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 31043**

B.E. / B.Tech. DEGREE EXAMINATION, APRIL 2015.

Third Semester

Electronics and Communication Engineering

01UEC303 - CIRCUIT THEORY

(Regulation 2013)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions.

PART A - (10 x 2 = 20 Marks)

1. For the circuit shown in fig 1 determine the voltage  $V_1$ .

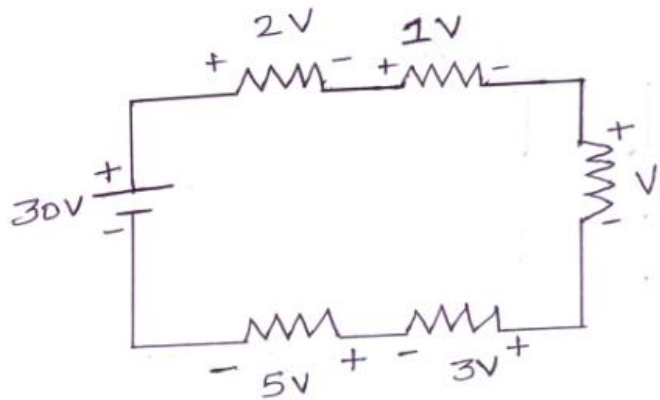


Fig. 1

2. Convert the circuit shown in fig 2 into single current source and resistance.

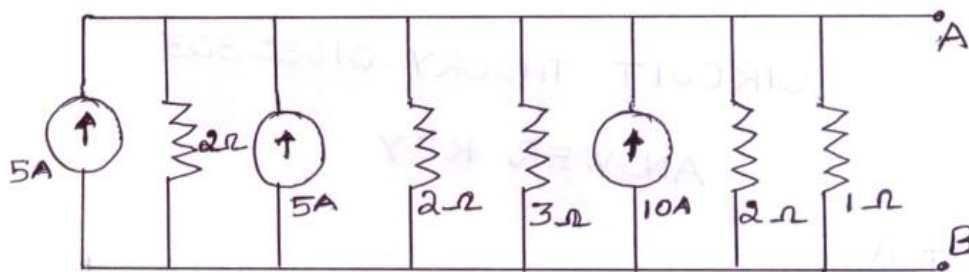


Fig. 2

3. Find the Thevenin's equivalent resistance across  $AB$  fig 3.

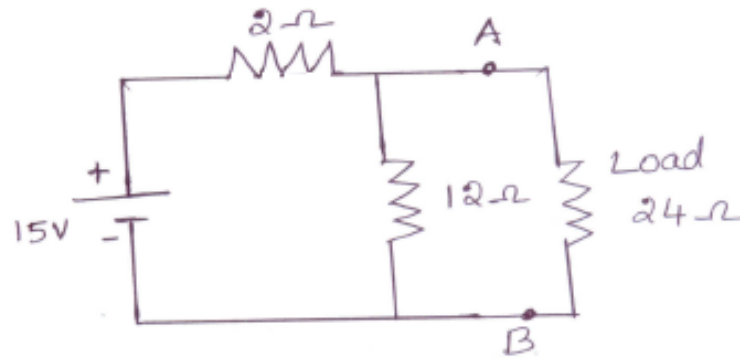


Fig. 3

4. State maximum power transfer theorem and determine the value of load resistance  $R_L$  when it draws maximum power in fig 4.

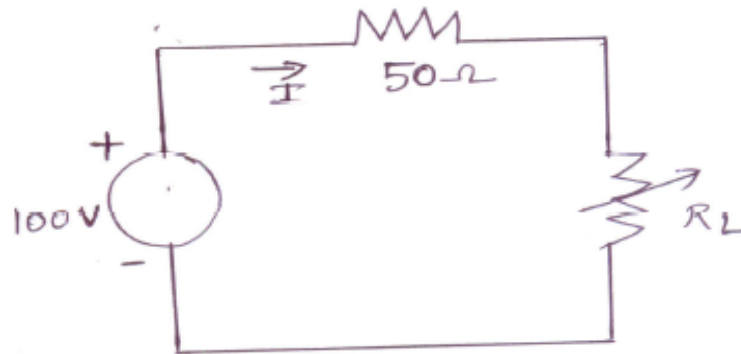


Fig. 4

5. Define resonance. Determine the values of impedance at resonance for circuit shown in fig 5.

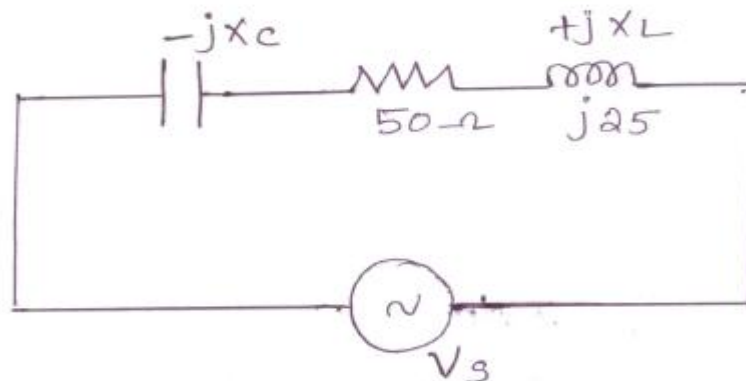


Fig. 5

6. Distinguish between natural and forced response.
7. Two inductively coupled coils have self inductances  $L_1 = 50\text{mH}$  and  $L_2 = 200\text{mH}$ . If the coefficient of coupling is 0.5. Find the value of mutual inductance between the coils.
8. Two wattmeter method is used to measure power in a three phase load. The wattmeter readings are  $400\text{W}$  and  $-35\text{W}$ , Calculate the power factor.
9. Define driving point and transfer point impedances.
10. Express  $Z$  parameters in terms of  $Y$  parameters.

PART - B (5 x 16 = 80 Marks)

11. (a) (i) Find the current  $I$  and voltage across  $30\Omega$  resistor for the circuit shown in fig 6. (8)

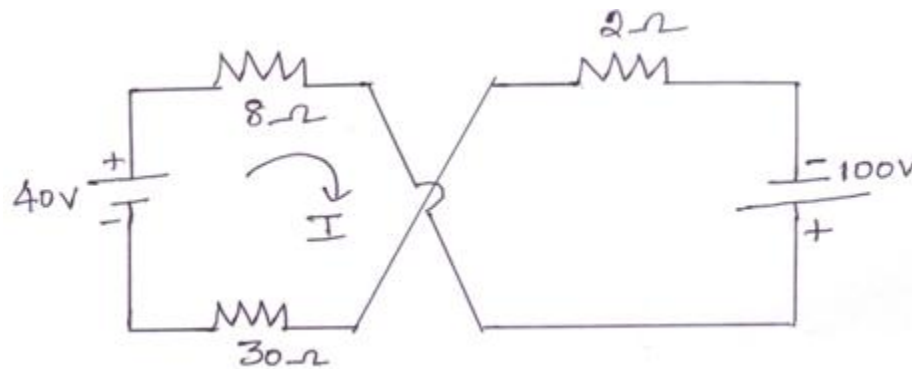


Fig. 6

- (ii) Determine the power dissipation in the  $4\Omega$  resistor of circuit shown in fig 7 using mesh analysis. (8)

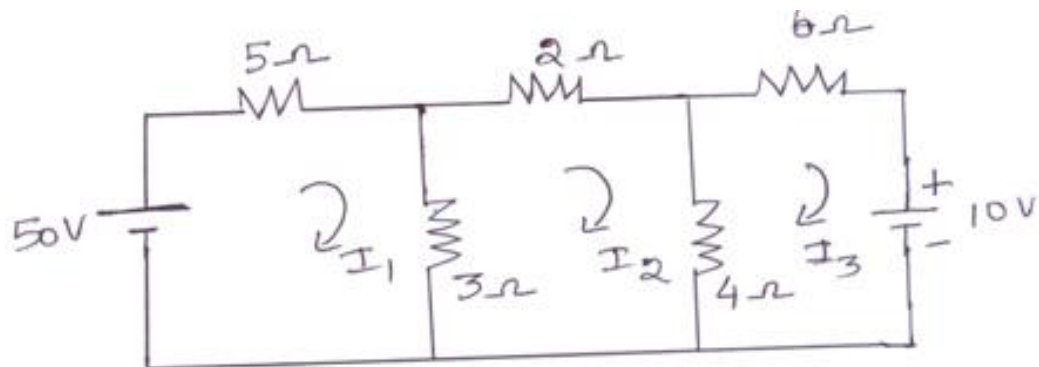


Fig. 7

Or

- (b) (i) Find the voltage  $V$  in the circuit shown in fig 8 which makes the current in the  $10\Omega$  resistor to be zero by using nodal analysis. (12)

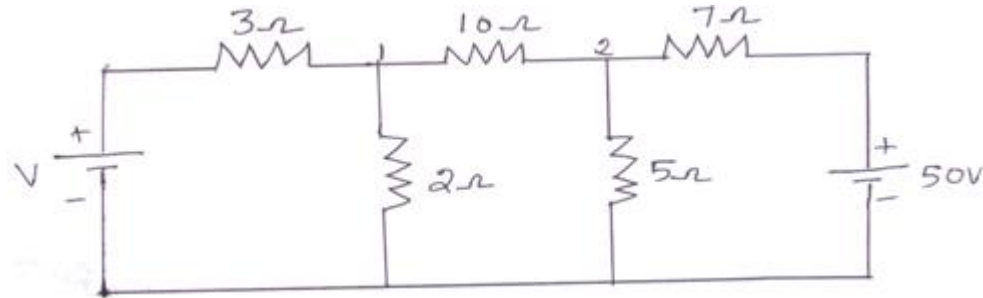


Fig. 8

- (ii) Determine the current in all the resistors of the circuit shown in fig 9. (4)

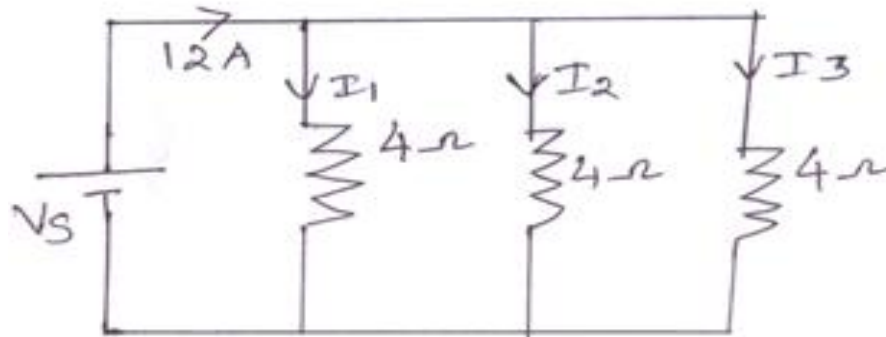


Fig. 9

12. (a) (i) Find the current through  $5\Omega$  resistor by superposition theorem in fig 10. (8)

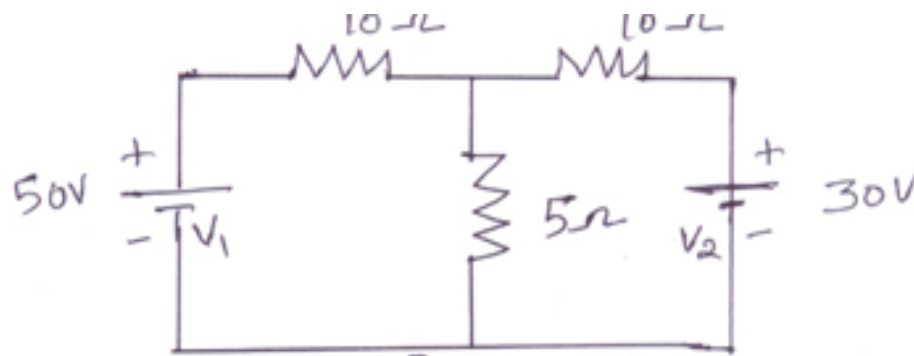


Fig. 10

- (ii) Find the current in  $3\Omega$  resistor using superposition theorem in fig 11. (8)

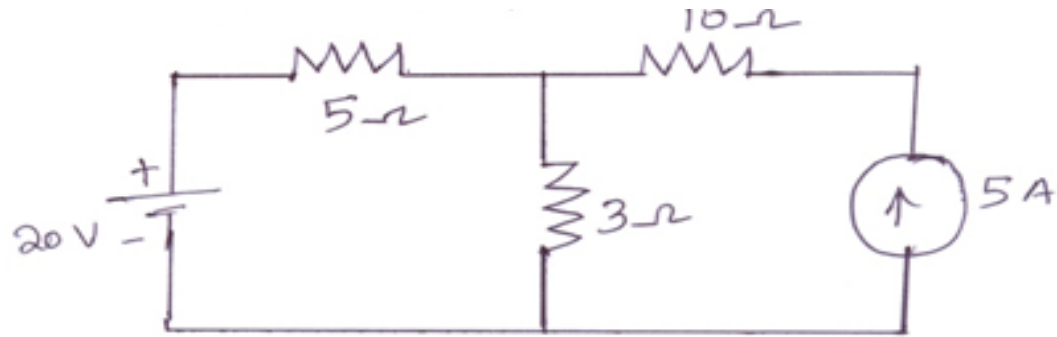


Fig. 11

Or

- (b) (i) Define Thevenin's theorem and Norton's theorem. (4)

- (ii) Determine the Thevenin's equivalent circuit across  $AB$  in fig12. (12)

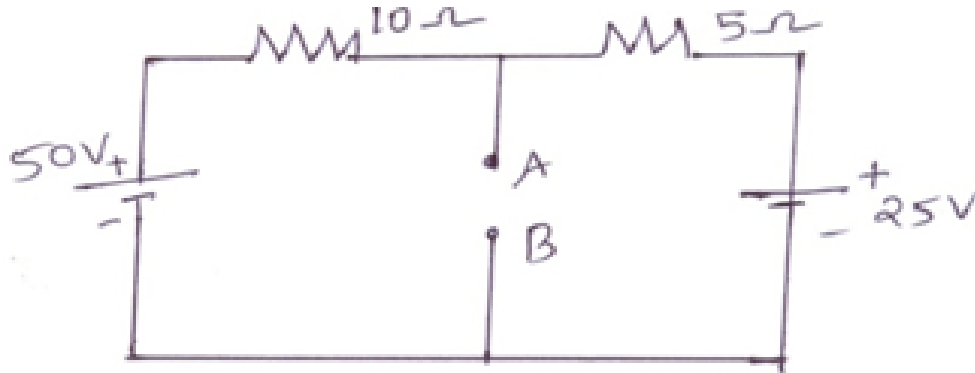


Fig. 12

13. (a) (i) Discuss the quality factor  $Q$  and its effect on bandwidth. Determine the value of  $Q$  at resonance and bandwidth of the circuit shown in fig 13. (8)

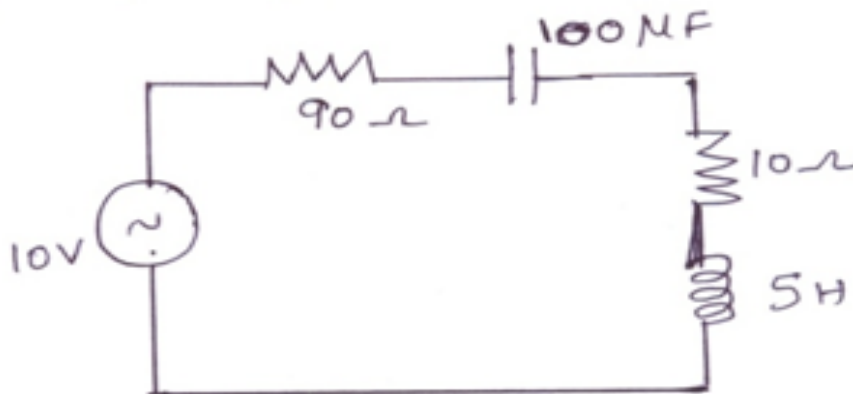


Fig. 13

- (ii) A voltage  $v(t) = 10 \sin \omega t$  is applied to a series RLC circuit. At the resonant frequency of the circuit, the maximum voltage across the capacitor is found to be 500V. Moreover the bandwidth is known to be 400 rad/sec and the impedance at resonance is 100Ω. Find the resonant frequency. Also find the values of  $L$  and  $C$  of the circuit. (8)

Or

- (b) (i) A series  $RL$  circuit with  $R = 30\Omega$  and  $L = 15H$  has a constant voltage  $V = 60V$  applied at  $t = 0$  as shown in fig 14. Determine the current  $i$ , the voltage across resistor and the voltage across inductor. (8)

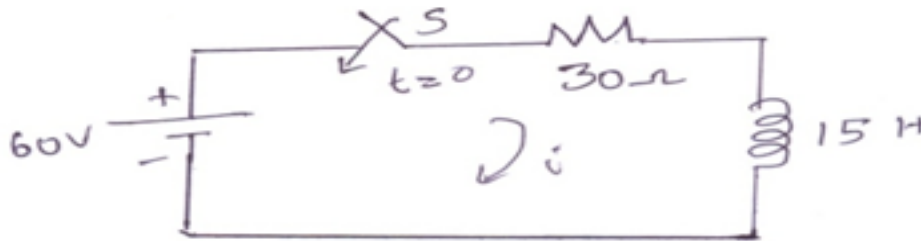


Fig. 14

- (ii) Discuss the response of circuits for non sinusoidal period inputs with an example. (8)

14. (a) Explain in detail about single and double tuned circuits. (16)

Or

- (b) A symmetrical 3 phase 3 wire 440V supply is connected to a star connected load. The impedance in each branch are  $Z_R = 2 + j3$ ,  $Z_Y = 1 - j2$ ,  $Z_B = 3 + j4$ . Find its equivalent delta connected load. The phase sequence is  $RYB$ . (16)

15. (a) Find the transmission parameters for the circuit shown in fig 15. (16)

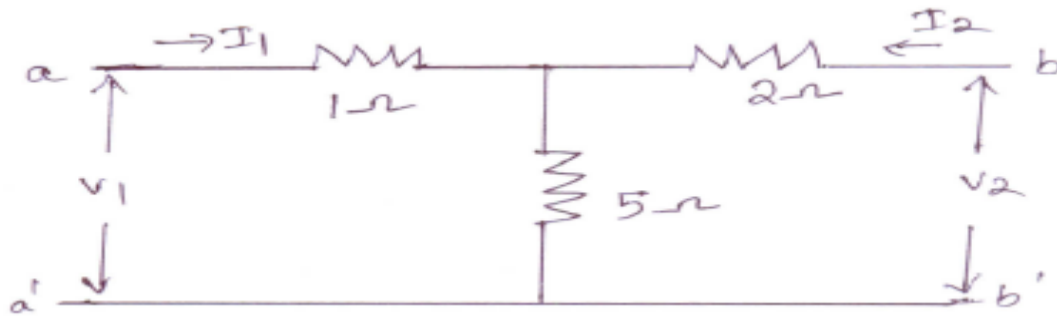


Fig. 15

Or

(b) (i) The impedance parameters of a 2 port network are

$$Z_{11} = 6\Omega, Z_{22} = 4\Omega, Z_{12} = Z_{21} = 3\Omega$$

Compute  $Y$  parameters and  $ABCD$  parameters. (8)

(ii) Explain the characteristics of ideal filter. Define high pass filter and passive filter. (8)

---

