

**A**

**Reg. No. :**

--	--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 52B08**

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2018

Second Semester

Biomedical Engineering

15UBM208 - ELECTRICAL CIRCUITS ANALYSIS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. A circuit contains two un-equal resistances in parallel CO1-R
  - (a) Current is same in both
  - (b) Large current flows in larger resistor
  - (c) Potential difference across each is same
  - (d) Smaller resistance has smaller conductance
2. Ohm's law is not applicable in all the following cases except CO1- R
  - (a) Electrolytes
  - (b) Arc lamps
  - (c) Insulators
  - (d) Vacuum ratio values.
3. Superposition theorem is valid only for CO2- R
  - (a) linear circuits
  - (b) nonlinear circuits
  - (c) both linear and non linear
  - (d) neither of the two
4. Norton's equivalent circuit consists of CO2- R
  - (a) voltage source in parallel with resistance
  - (b) voltage source in series with resistance
  - (c) current source in series with resistance
  - (d) current source in parallel with resistance
5. What is the total reactance of a series RLC circuit at resonance? CO3- R
  - (a) equal to  $X_L$
  - (b) equal to  $X_C$
  - (c) equal to R
  - (d) zero


6. The bandwidth is defined as the band of frequencies between  $f_2$  and  $f_1$ . CO3- R  
 (a)  $f_1 - f_2$  (b)  $f_2 - f_1$  (c)  $f_1 \times f_2$  (d)  $f_1 / f_2$
7. The transient response occurs CO4- R  
 (a) only in resistive circuits (b) only in inductive circuits  
 (c) only in capacitive circuits (d) both in (b) and (c)
8. The transient current in a loss – free LC circuit when excited from an ac source is an \_\_\_\_\_ sine wave. CO4- R  
 (a) undamped (b) over damped (c) under damped (d) critically damped
9. In a three phase unbalanced star connected system, the vector sum of the current in the three lines is CO5- R  
 (a) Zero (b) not zero  
 (c) one (d) three times the current in the each phase
10. Wattmeter deflection in ac circuit is proportional to the CO5-R  
 (a) maximum power in the circuit (b) instantaneous power in the circuit  
 (c) average power in the circuit (d) real power in the circuit

PART – B (5 x 2= 10Marks)

11. What is a node, a junction and a branch? CO1- R
12. List some applications of maximum power transfer theorem. CO2- R
13. Give the relationship between bandwidth and selectivity. CO3- R
14. Define time constant of RC and RLC circuit. CO4- R
15. Write down the line and phase values in star and delta connection. CO5- R

PART – C (5 x 16= 80Marks)

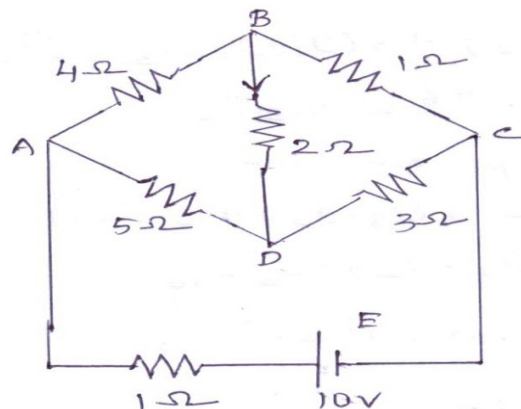16. (a) In the circuit shown, determine the current through the  $2\Omega$  resistor and the total current delivered by the battery. Use Kirchoff's law. CO1- App (16)




Or

(b) Determine voltages at each node for the circuit shown

CO1- App


(16)

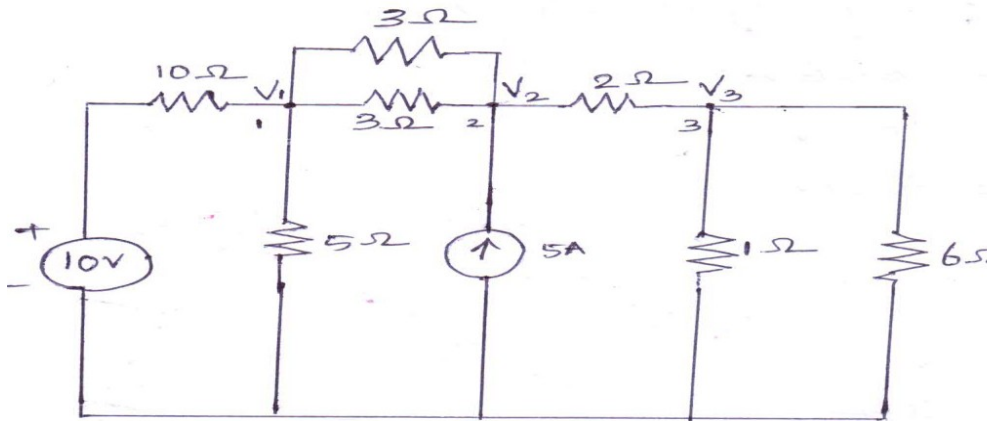

17. (a) Obtain the Norton's equivalent circuit and determine the current flowing through the 5Ω resistor for the circuit shown.

CO2- App

(16)

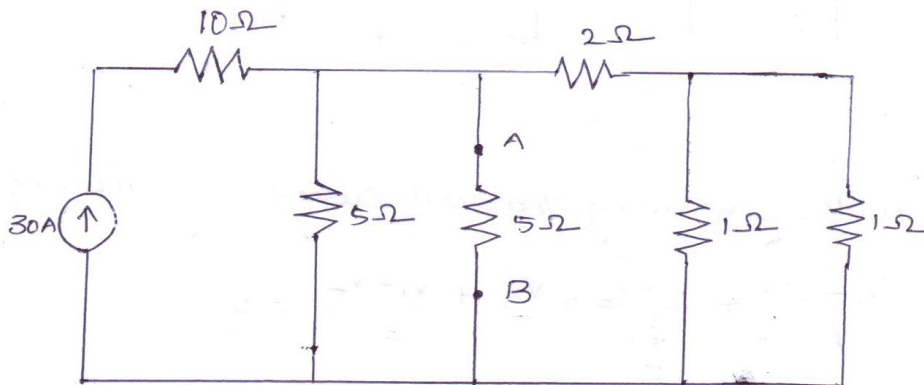


Or

(b) For the circuit shown, verify reciprocity theorem.

CO2-Ana

(16)

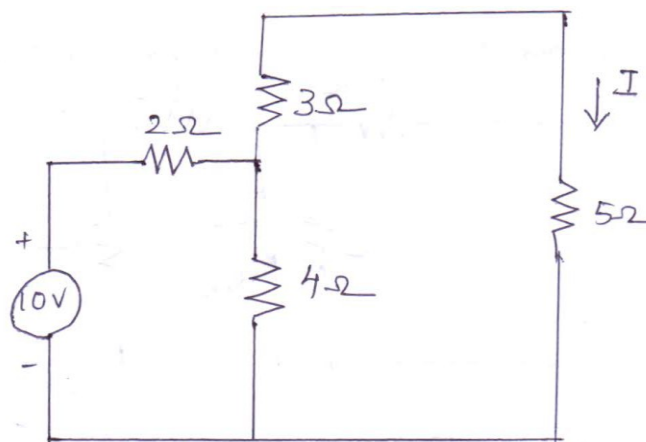

18. (a) Obtain the expression for Q- Factor of parallel resonance of a circuit having R,L and C. CO3- Ana (16)


Or

(b) Explain and derive the relationships for bandwidth and half power frequencies of RLC series circuit. CO3- Ana (16)

19. (a) Derive an expression for the complete solution of current for RC series circuit. CO4-U (16)

Or

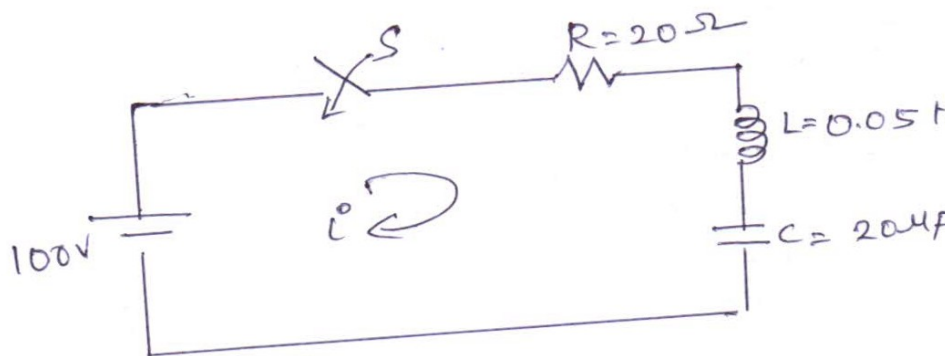(b) The circuit shown consists of resistance, inductance, and capacitance in series with a 100V source when the switch is closed at  $t = 0$ . Find the current transient. CO4- Ana (16)



20. (a) With a neat circuit and phasor diagram, explain the three phase power measurement by two wattmeter method and also derive the expression for Power Factor. CO5- U (16)

Or

(b) (i) Develop the expression for balanced delta connected load and draw the phasor diagram. CO5- U (8)

(ii) A balanced star connected load having an impedance  $(15+j20) \Omega$  is connected to a three phase, 440v; 50Hz supply. Find the line currents and the power absorbed by the load. Assume RYB phase sequence. CO5- U (8)