

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--

Question Paper Code: 53B05

B.E./B.Tech. DEGREE EXAMINATION, MAY 2018

Third Semester

Biomedical Engineering

15UBM305 Semiconductor Devices and Circuits

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer All Questions

PART A - (10x 1 = 10 Marks)

1. At room temperature the current in an intrinsic semiconductor is due to CO1- R
(a) holes (b) electrons (c) ions (d) Holes and Electrons
2. The configuration which provides both high current and voltage gain CO1- R
(a) CE (b) CB (c) CC (d) None
3. Field Effect Transistors (FET) can be used as a variable CO2- R
(a) inductor (b) capacitor (c) resistor (d) voltage source
4. With the E-MOSFET, when gate input voltage is zero, drain current is CO2- R
(a) At Saturation (b) Zero (c) Wide (d) Narrow
5. Astable multivibrator is _____ in any state. CO3- R
(a) Stable (b) Unstable (c) Saturated (d) Both B & C
6. The Hysteresis can be eliminated in Schmitt Trigger by keeping CO3- R
(a) $RC_1=RC_2$ (b) $RC_1>RC_2$
(c) $RC_1<RC_2$ (d) RC_1 and RC_2 has no effect

7. Only the condition = _____ must be satisfied for self-sustained oscillations to result. CO4- U
 (a) 0 (b) -1 (c) 1 (d) none of these
8. The crystal oscillator frequency is very stable due to _____ of the crystal CO4- R
 (a) High Q (b) Low Q (c) Rigidity (d) Vibrations
9. A 180 degree output swing will be in _____ amplifier. CO5- R
 (a) Class A (b) Class B (c) Class AB (d) None
10. What is the maximum efficiency of a class A circuit with a direct or series-fed load connection? CO5- R
 (a) 90% (b) 78.5% (c) 50% (d) 25%

PART – B (5 x 2= 10Marks)

11. Distinguish between avalanche break down and Zener break down. CO1- U
12. State the applications of SCR CO2- U
13. If an astable multivibrator has $C_1=C_2=1000\text{pF}$, and $R_1=R_2=20\text{K}\Omega$, calculate the frequency of oscillation. CO3- U
14. Outline the reason for not preferring LC oscillators to generate low frequency signals? CO4- U
15. Illustrate the reason behind the rejection of Class C mode in Audio frequency power amplifiers. CO5- U

PART – C (5 x 16= 80Marks)

16. (a) Explain the operation of common emitter connection of transistor with its characteristics CO1-U (16)

Or

- (b) Explain the working of Zener diode and draw its V-I characteristics CO1 -Ana (16)
17. (a) Discuss the structure and operation of n Channel JFET with its V-I and Transfer Characteristics. CO2 -U (16)

Or

- (b) (i) Distinguish the D-MOSFET and E MOSFET CO2 -U (6)
(ii) Explain the Construction, operation and characteristics of n Channel E – MOSFET with neat sketches. CO2 -U (10)
18. (a) Explain the operation of Astable multivibrator with Triggering methods. CO3- U (16)

Or

- (b) (i) Evaluate the operation of Zener voltage regulator with Varying input voltage and varying load. CO3- E (10)
(ii) Determine the minimum and maximum values of current limiting resistor, if $V_z=8V$, Source voltage = 30V, load Current = 0-50mA, $P_{zmax}=1W$ in a Zener regulator. CO3- App (6)
19. (a) Explain in detail the Voltage series feedback connection and Current shunt feedback connection of amplifiers. CO4-App (16)

Or

- (b) (i) Draw and Explain the construction of Wien Bridge Oscillator and derive the frequency expression. CO4 -App (10)
(ii) The frequency sensitive arms of the Wien bridge oscillator uses $C_1=C_2=0.001\mu F$ and $R_1=10K\Omega$, R_2 is variable. The frequency is varied from 10KHz to 50 KHz by varying R_2 . Find the minimum and Maximum values CO4 -App (6)
20. (a) Derive the expressions for Voltage gain, Current gain, input and Output impedance for CE amplifier using h parameter analysis. CO5- C (16)

Or

- (b) Explain the operation of a class B amplifier with neat diagram. Derive the expression for its maximum efficiency. Mention its drawback and the methods to overcome it. CO5- C (16)

