

**A**

**Reg. No. :**

--	--	--	--	--	--	--	--	--	--

**Question Paper Code: 59501**

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2018

Elective

Electronics and Instrumentation Engineering

15UEI901– VLSI SYSTEM DESIGN

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

Answer ALL Questions

PART A - (10 x 1 = 10 Marks)

1. In MOS transistors, \_\_\_\_\_ is used for their gates. CO1- R  
(a) Metal                      (b) Polysilicon                      (c) Silicon-di-Oxide                      (d) Gallium
2. The photoresist layer is exposed to CO1- R  
(a) Visible Light                      (b) Infra Red Light                      (c) Ultraviolet Light                      (d) LED
3. Which color is used for n-diffusion? CO2- R  
(a) Red                      (b) Blue                      (c) Yellow                      (d) Green
4. The transistors used in BiCMOS are: CO2- R  
(a) BJT                      (b) MOSFET                      (c) Both BJT and MOSFETs                      (d) JFET
5. In clocked CMOS logic, output is evaluated in CO3- R  
(a) On Period                      (b) Off Period                      (c) Both Periods                      (d) Half of On Period

6. Multipliers are built using CO3- R
- (a) Binary Adders      (b) Binary Subtractors      (c) Dividers      (d) Multiplexers
7. PLA contains CO4- R
- (a) AND and OR arrays      (b) NAND and OR arrays
- (c) NOT and AND arrays      (d) NOR and OR arrays
8. Which type of device FPGA are? CO4- R
- (a) SLD      (b) SRAM      (c) EPROM      (d) PLD
9. The full form of VHDL is CO5- R
- (a) Very High Descriptive Language      (b) Very High Definition Language
- (c) Variable Definition Language      (d) None of the Mentioned
10. A decimal counter has \_\_\_\_\_ states. CO5- R
- (a) 5      (b) 10      (c) 15      (d) 20

PART – B (5 x 2= 10Marks)

11. Define body effect. CO1- U
12. Mention techniques to reduce switching activity. CO2- R
13. What is transmission gate? CO3- R
14. List the steps used for design flow in VLSI. CO4- R
15. What is subprogram? CO5- U

PART – C (5 x 16= 80Marks)

16. (a) Discuss in detail about the modes of operation of MOS transistor with necessary equations. CO1- U      (16)

Or

- (b) Explain the different steps involved in the fabrication of NMOS with a neat diagram. CO1- U (16)
17. (a) Determine the pull up to pull down ratios of NMOS inverter. CO2- App (16)  
Or
- (b) (i) Label the stick diagram for NAND and NOR gate. CO2- Ana (10)  
(ii) Discuss about any three layout design rules. CO2- Ana (6)
18. (a) Explain the domino and dual rail domino logic families with neat diagram. CO3- U (16)  
Or
- (b) Discuss in detail about the concepts of high speed adders. CO3- Ana (16)
19. (a) What is programmable logic devices? Explain the different types of PLD in detail CO4- U (16)  
Or
- (b) Explain about building block architecture of FPGA. CO4- U (16)
20. (a) Explain in detail about the design procedure of RTL. CO5- U (16)  
Or
- (b) (i) Construct a VHDL code for JK Flip flop. CO5- App (8)  
(ii) Develop a VHDL program for 4:1 MUX CO5- App (8)

