

A

Reg. No. :

--	--	--	--	--	--	--	--	--	--	--

Question Paper Code: 54305

B.E. / B.Tech. DEGREE EXAMINATION, MAY 2018

Fourth Semester

Electrical and Electronics Engineering

15UEE405- ANALOG INTEGRATED CIRCUITS

(Regulation 2015)

Duration: Three hours

Maximum: 100 Marks

PART A - (10 x 1 = 10 Marks)

1. Why oxidation process is required in IC fabrication? CO1 -R
 - (a) To protect against contamination
 - (b) To use it for fabrication various components
 - (c) To prevent diffusion of impurities
 - (d) All of the mentioned

2. Which technology is used to get cheap resistors and capacitors? CO1 -R
 - (a) Thick film technology
 - (b) Thin film technology
 - (c) Thin and thick film technology
 - (d) None of the mentioned

3. Which is not the ideal characteristic of an op-amp? CO2- R
 - (a) Input Resistance $\rightarrow 0$
 - (b) Output impedance $\rightarrow 0$
 - (c) Bandwidth $\rightarrow \infty$
 - (d) Open loop voltage gain $\rightarrow \infty$

4. Ideal op-amp has infinite voltage gain because CO2 -R
 - (a) To control the output voltage
 - (b) To obtain finite output voltage
 - (c) To receive zero noise output voltage
 - (d) None of the mentioned

5. Calculate the conversion time of a 12-bit counter type ADC with 1MHz clock frequency to convert a full scale input? CO3- R
- (a) 4.095 μ s (b) 4.095ms
(c) 4.095s (d) None of the mentioned
6. Find out the resolution of 8 bit DAC/ADC? CO3- R
- (a) 562 (b) 625 (c) 256 (d) 256
7. Which characteristic of PLL is defined as the range of frequencies over which PLL can acquire lock with the input signal? CO4- R
- (a) Free-running state (b) Pull-in time
(c) Lock-in range (d) Capture range
8. According to transfer characteristics of PLL, the phase error between VCO output & incoming signal must be maintained between _____ in order to maintain a lock. CO4- R
- (a) 0 & π (b) 0 & $\pi/2$ (c) 0 & 2π (d) π & 2π
9. What is the dropout voltage in a three terminal IC regulator? CO5- R
- (a) $|V_{in}| \geq |V_o| + 2v$ (b) $|V_{in}| < |V_o| - 2v$ (c) $|V_{in}| = |V_o|$ (d) $|V_{in}| \leq |V_o|$
10. Switching regulators are series type regulators, which has _____ power dissipation & _____ efficiency. CO5- R
- (a) increased, increased (b) increased, reduced
(c) reduced, increased (d) reduced, reduced

PART – B (5 x 2= 10Marks)

11. What are the different IC packages? CO1- R
12. Define common mode rejection ratio. CO2- R
13. If the gain of a closed-loop inverting amplifier is 3.9, with an input resistor value of 1.6 kilohms, what value of feedback resistor is necessary? CO3- R
14. Define the resolution of a Digital to Analog converter. CO4- R
15. The timing components for a PLL are 15 kOhms and 220 pF. Calculate the free-running frequency. CO5- R

PART – C (5 x 16= 80Marks)

16. (a) Explain briefly about the logic families of digital IC's. CO1-App (16)
Or
(b) List the basic process used in the silicon planer technology. CO1- App (16)
17. (a) Draw the circuit diagram of op-amp differentiator, integrator and derive an expression for the output in terms of the input. CO2 -App (16)
Or
(b) Explain and derive the condition for DC-characteristics of an operational amplifier. CO2 -Ana (16)
18. (a) Explain the working of an instrumentation amplifier with a circuit. Give its characteristics and applications. CO3- Ana (16)
Or
(b) Explain
(i) R-2R ladder type DAC CO3 -Ana (8)
(ii) Weighted resistor type DAC CO3 -Ana (8)
19. (a) Draw the block diagram of an Astable multivibrator using 555timer and derive an expression for its frequency of oscillation. CO4 -U (16)
Or
(b) Explain working of PLL using block diagram and explain any one application of the same. CO4- Ana (16)
20. (a) Explain in detail about the LM 380 power amplifier. CO5- U (16)
Or
(b) Draw and explain the functional block diagram of a 723 regulator. CO5- U (16)

